



**GATE
PSUs**



MADE EASY
Publications

POSTAL STUDY PACKAGE

COMPUTER SCIENCE & IT

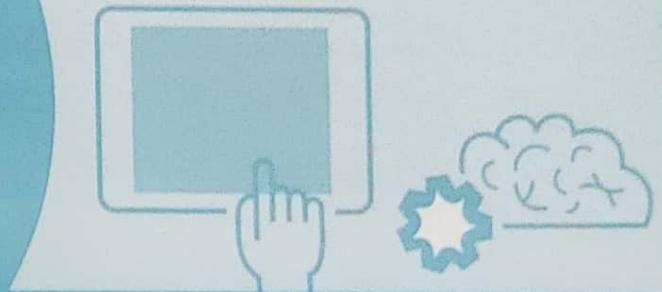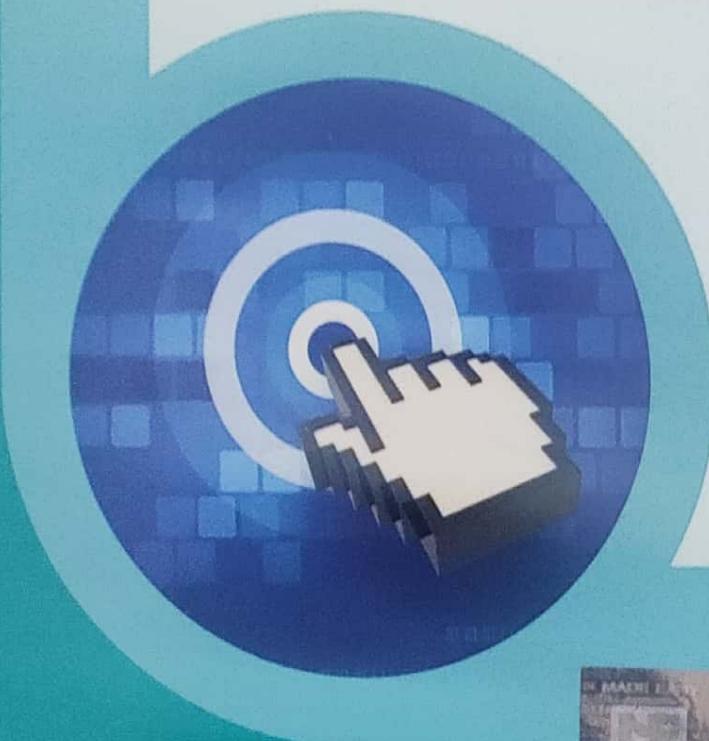

2020



**THEORY
BOOK**

Digital Logic

Well illustrated theory with solved examples

Contents

Digital Logic

Chapter 1

Basics of Digital Logic	1
1.1. Digital Number Systems	2
1.2. Codes	7
1.3. Arithmetic Operations	10
1.4. Signed Number Representation	13
1.5. Over Flow Concept	19
<i>Student Assignments.....</i>	21

Chapter 2

Boolean Algebra & Minimization Techniques	22
2.1 Logic Operations	22
2.2 Laws of Boolean Algebra	23
2.3 Boolean Algebraic Theorems	24
2.4 Minimization of Boolean Functions	27
2.5 Representation of Boolean Functions	27
2.6 Implicants, Prime Implicants and Essential Prime Implicants	37
<i>Student Assignments.....</i>	41

Chapter 3

Logic Gates and Switching Circuits	43
3.1 Basic Gates	43
3.2 Universal Gates	49
3.3 Special Purpose Gate	52
3.4 Realization of Logic Gates Using Universal Gates	57
<i>Student Assignments.....</i>	61

Chapter 4

Combinational Logic Circuits.....	63
4.1 Design Procedure for Combinational Circuit	63
4.2 Arithmetic Circuits	64
4.3 Non-arithmetic Circuit	77
4.4 Hazards	107
<i>Student Assignments.....</i>	110

Chapter 5

Sequential Logic Circuits	113
5.1 Latches and Flip-Flops	114
5.2 Race Around Condition	125
5.3 Conversion of Flip-Flops	127
5.4 Applications of Flip-Flops	130
<i>Student Assignments.....</i>	132

Chapter 6

Registers.....	134
6.1 Shift Register	134
<i>Student Assignments.....</i>	143

Chapter 7

Counters	144
7.1 Asynchronous/Ripple Counters	146
7.2 Synchronous Counters	151
7.3 Synchronous Counter Design	158
7.4 State Diagram and State Table	162
7.5 Finite State Model/Machine	164
<i>Student Assignments.....</i>	166



01

CHAPTER

Basics of Digital Logic

Introduction

Electronic systems are of two types:

- (i) Analog systems
- (ii) Digital systems

Analog systems are those systems in which voltage and current variations are continuous through the given range and they can take any value within the given specified range, whereas a digital system is one in which the voltage level assumes finite number of distinct values. In all modern digital circuits there are just two discrete voltage level.

Digital circuits are often called switching circuits, because the voltage levels in a digital circuit are assumed to be switched from one value to another instantaneously. Digital circuits are also called logic circuits, because every digital circuit obeys a certain set of logical rules.

Digital systems are extensively used in control systems, communication and measurement, computation and data processing, digital audio and video equipments, etc.

Advantages of Digital Systems

Digital systems have number of advantages over analog systems which are summarized below:

1. Ease of Design

The digital circuits having two voltage levels, OFF and ON or LOW and HIGH, are easier to design in comparison with analog circuits in which signals have numerical significance ; so their design is more complicated.

2. Greater Accuracy and Precision

Digital systems are more accurate and precise than analog systems because they can be easily expanded to handle more digits by adding more switching circuits.

3. Information Storage is Easy

There are different types of semiconductor memories having large capacity, which can store digital data.

4. Digital Systems are More Versatile

It is easy to design digital systems whose operation is controlled by a set of stored instructions called program. However in analog systems, the available options for programming is limited.

5. Digital Systems are Less Affected by Noise

The effect of noise in analog system is more. Since in analog systems the exact values of voltages are important. In digital system noise is not critical because only the range of values is important.

6. Digital Systems are More Reliable

As compared to analog systems, digital systems are more reliable.

Limitations of Digital System

- (i) The real world is mainly analog.
- (ii) Human does not understand the digital data.

1.1. Digital Number Systems

Many number systems are used in digital technology. A number system is simply a way to count. The most commonly used number systems are:

- Decimal number system
- Octal number system
- Binary number system
- Hexadecimal number system

A number system with base or radix 'r' will have r number of different digits from $0 \rightarrow (r-1)$ thus, number system is represented by $(N)_b$

where, N = Number ; b = Base or radix

In general a number with an integer part of 'n' bits and a fraction part of 'm' bits can be written as

$$(N)_b = \underbrace{b_{n-1} b_{n-2} \dots b_1 b_0}_{\text{Integer part}} \quad \uparrow \quad \underbrace{b_{-1} b_{-2} \dots b_{-m}}_{\text{Fraction part}}$$

1.1.1 Decimal Number System

- This system has 'base 10'.
- It has 10 distinct symbols (0, 1, 2, 3, 4, 5, 6, 7, 8 and 9).
- This is a positional value system in which the value of a digit depends on its position.
 \Rightarrow Let we have $(453)_{10}$ is a decimal number then,

$$\begin{array}{r} 4 \quad 5 \quad 3 \\ \swarrow \quad \searrow \\ 3 \times 10^0 = 3 \\ 5 \times 10^1 = 50 \\ 4 \times 10^2 = 400 \\ \hline \text{Finally we get, } \quad (453)_{10} \end{array}$$

\therefore We can say "3" is the least significant digit(LSD) and "4" is the most significant digit(MSD).

Example-1.1 A particular number system having base B is given as $(\sqrt{41})_B = 5_{10}$. The value of ' B ' is

- | | |
|-------|-------|
| (a) 5 | (b) 6 |
| (c) 7 | (d) 8 |

Solution: (b)

Squaring both side,

$$(\sqrt{41})_B = (5)_{10}$$

$$\begin{aligned} [\sqrt{(4B+1)}]_B^2 &= [(5)]_{10}^2 \\ (4B+1)_B &= (25)_{10} \\ (4B+1)_{10} &= (25)_{10} \\ B &= 6 \end{aligned}$$

1.1.2 Binary Number System

- It has base '2' i.e. it has two base numbers 0 and 1 and these base numbers are called "Bits".
- In this number system, group of "Four bits" is known as "Nibble" and group of "Eight bits" is known as "Byte".

i.e.

$$4 \text{ bits} = 1 \text{ Nibble}; \quad 8 \text{ bits} = 1 \text{ Byte}$$

Binary to Decimal Conversion

A binary number is converted to decimal equivalent simply by summing together the weights of various positions in the binary number which contains '1'.

Example-1.2

The decimal number representation of 101101.10101 is

Solution:

$$\begin{aligned}(101101.10101)_2 &= 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} \\ &\quad + 0 \times 2^{-2} + 1 \times 2^{-3} + 0 \times 2^{-4} + 1 \times 2^{-5} \\ &= 32 + 0 + 8 + 4 + 0 + 1 + \frac{1}{2} + 0 + \frac{1}{8} + 0 + \frac{1}{32} = (45.65625)_{10}\end{aligned}$$

Decimal to Binary Conversion

The integral decimal number is repeatedly divided by '2' and writing the remainders after each division until a quotient '0' is obtained.

Example-1.3

Convert $(13)_{10}$ to binary.

Solution:

Quotient	Remainder	
13 ÷ 2	6	1 ↑ LSB
6 ÷ 2	3	0
3 ÷ 2	1	1
1 ÷ 2	0	1 MSB

$$(13)_{10} \Rightarrow (1101)_2$$

Remember

To convert Fractional decimal into binary, Multiply the number by '2'. After first multiplication integer digit of the product is the first digit after binary point. Later only fraction part of the first product is multiplied by 2. The integer digit of second multiplication is second digit after binary point, and so on. The multiplication by 2 only on the fraction will continue like this based on conversion accuracy or until fractional part becomes zero.

Example - 1.4

Convert $(0.65625)_{10}$ to an equivalent base-2 number.

Solution:

$$\begin{array}{ccccccccc} 0.65625 & \xrightarrow{\times 2} & 0.31250 & \xrightarrow{\times 2} & 0.62500 & \xrightarrow{\times 2} & 0.25000 & \xrightarrow{\times 2} & 0.50000 \\ \downarrow & & \downarrow & & \downarrow & & \downarrow & & \downarrow \\ 1.31250 & & 0.62500 & & 1.25000 & & 0.50000 & & 1.00000 \\ \downarrow & & \downarrow & & \downarrow & & \downarrow & & \downarrow \\ 1 & & 0 & & 1 & & 0 & & 1 \end{array}$$

Thus,

$$(0.65625)_{10} = (0.10101)_2$$

1.1.3 Octal Number System

- It is very important in digital computer because by using the octal number system, the user can simplify the task of entering or reading computer instructions and thus save time.
- It has a base of '8' and it posses 8 distinct symbols (0,1...7).
- It is a method of grouping binary numbers in group of three bits.

Octal to Decimal Conversion

An octal number can be converted to decimal equivalent by multiplying each octal digit by its positional weightage.

Example-1.5

Convert $(6327.4051)_8$ into its equivalent decimal number.

Solution:

$$\begin{aligned}(6327.4051)_8 &= 6 \times 8^3 + 3 \times 8^2 + 2 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1} + 0 \times 8^{-2} + 5 \times 8^{-3} + 1 \times 8^{-4} \\ &= 3072 + 192 + 16 + 7 + \frac{4}{8} + 0 + \frac{5}{512} + \frac{1}{4096} \\ &= (3287.5100098)_{10}\end{aligned}$$

Thus, $(6327.4051)_8 = (3287.5100098)_{10}$

Decimal to Octal Conversion

- It is similar to decimal to binary conversion.
- For integral decimal, number is repeatedly divided by '8' and for fraction, number is multiplied by '8'.

Example-1.6

Convert $(3287.5100098)_{10}$ into octal.

Solution:

For integral part:

Quotient	Remainder
3287 ÷ 8 410	7
410 ÷ 8 51	2
51 ÷ 8 6	3
6 ÷ 8 0	6

$$\therefore (3287)_{10} = (6327)_8$$

Now for fractional part:

$\begin{array}{r} 0.5100098 \\ \times 8 \\ \hline 4.0800784 \end{array}$	$\begin{array}{r} 0.0800784 \\ \times 8 \\ \hline 0.6406272 \end{array}$	$\begin{array}{r} 0.6406272 \\ \times 8 \\ \hline 5.1250176 \end{array}$	$\begin{array}{r} 0.1250176 \\ \times 8 \\ \hline 1.0001408 \end{array}$
\downarrow 4	\downarrow 0	\downarrow 5	\downarrow 1

Finally,

$$\begin{aligned}(0.5100098)_{10} &= (0.4051)_8 \\ (3287.5100098)_{10} &= (6327.4051)_8\end{aligned}$$

Octal-to-Binary Conversion

This conversion can be done by converting each octal digit into binary individually.



Theory with Solved Examples

Example-1.7 Convert $(472)_8$ into binary**Solution:**

$$\begin{array}{ccc} 4 & 7 & 2 \\ \downarrow & \downarrow & \downarrow \\ \therefore (472)_8 = (100 & 111 & 010)_2 \end{array}$$

Binary-to-Octal Conversion

In this conversion the binary bit stream are grouped into groups of three bits starting at the LSB and then each group is converted into its octal equivalent. After decimal point grouping start from left.

Example-1.8 Convert $(1011011110.11001010011)_2$ into octal.**Solution:**

For left-side of the radix point, we grouped the bits from LSB:

$$\begin{array}{cccc} 0 & 0 & 1 & 0 & 1 & 1 & 0 \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ 1 & 3 & 3 & 6 \end{array}$$

Here two 0's at MSB are added to make a complete group of 3 bits.

For right-side of the radix point, we grouped the bits from MSB:

$$\begin{array}{ccccc} \bullet & 1 & 1 & 0 & 0 \\ \uparrow & \downarrow & \downarrow & \downarrow & \downarrow \\ \text{radix} & 6 & 2 & 4 & 6 \\ \text{point} & & & & \end{array}$$

Here a '0' at LSB is added to make a complete group of 3 bits.

Finally, $(1011011110.11001010011)_2 = (1336.6246)_8$

1.1.4 Hexadecimal Number System

- The base for this system is "16", which requires 16 distinct symbols to represent the numbers.
- It is a method of grouping 4 bits.
- This number system contains numeric digits (0, 1, 2,...,9) and alphabets (A, B, C, D, E and F) both, so this is an "ALPHANUMERIC NUMBER SYSTEM".
- Microprocessor deals with instructions and data that use hexadecimal number system for programming purposes.
- To signify a hexadecimal number, a subscript 16 or letter 'H' is used i.e. $(A7)_{16}$ or $(A7)_H$.

Table-1.1

Hexadecimal	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

Hexadecimal-to-Decimal Conversion**Example - 1.9** Convert $(3A.2F)_{16}$ into decimal system.**Solution:**

$$\begin{aligned}(3A.2F)_{16} &= 3 \times 16^1 + 10 \times 16^0 + 2 \times 16^{-1} + 15 \times 16^{-2} \\ &= 48 + 10 + \frac{2}{16} + \frac{15}{16^2} = (58.1836)_{10}\end{aligned}$$

Decimal-to-Hexadecimal Conversion**Example - 1.10** Convert $(675.625)_{10}$ into Hexadecimal.**Solution:**

For Integral Part:

	Quotient	Remainder
$675 \div 16$	42	3
$42 \div 16$	2	$10 = A$
$2 \div 16$	0	2

$$\therefore (675)_{10} = (2A3)_{16}$$

For Fractional Part:

$$625 \times 16 = 10 = A$$

$$\therefore (0.625)_{10} = (0.A)_{16}$$

$$\text{Finally, } (675.625)_{10} = (2A3.A)_{16}$$

Hexadecimal-to-Binary Conversion

For this conversion replace each hexadecimal digit by its 4 bit binary equivalent.

Example - 1.11 Convert $(2F9A)_{16}$ to Binary System**Solution:**

$$\begin{array}{cccc} 2 & F & 9 & A \\ \downarrow & \downarrow & \downarrow & \downarrow \\ 0010 & 1111 & 1001 & 1010 \\ \therefore (2F9A)_{16} & = (0010\ 1111\ 1001\ 1010)_2 \end{array}$$

Binary-to-Hexadecimal Conversion

For this conversion the binary bit stream is grouped into pairs of four (starting from LSB) and hex number is written for its equivalent binary group.

Example - 1.12 Convert $(10100110101111)_2$ to hexadecimal number system.**Solution:**

$$\begin{array}{cccc} 00\ 10 & 10\ 01 & 10\ 10 & 1111 \\ \underbrace{\quad}_{2} & \underbrace{\quad}_{9} & \underbrace{\quad}_{A} & \underbrace{\quad}_{F} \end{array}$$


Here two 0's at MSB are added to make a complete group of 4 bits.

$$\therefore (10100110101111)_2 = (29AF)_{16}$$

The number systems can also be classified as weighted binary number and unweighted binary number. Where weighted number system is a positional weighted system for example, Binary, Octal, Hexadecimal BCD, 2421 etc. The unweighted number systems are non-positional weightage system for example Gray code, Excess-3 code etc.

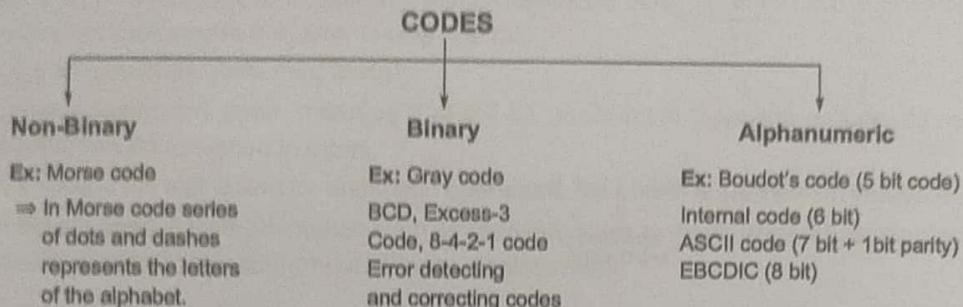1.2 Codes

When numbers, letters or words are represented by a special group of symbols, we say that they are being encoded, and the group of symbols is called "CODE".



1.2.1 Binary Coded Decimal Code (BCD)

- In this code, each digit of a decimal number is represented by binary equivalent.
- It is a 4-bit binary code.
- It is also known as "8-4-2-1 code" or simply "BCD Code".
- It is very useful and convenient code for input and output operations in digital circuits.
- Also, it is a "weighted code system".

For example:

$$\begin{aligned}
 (943)_{\text{decimal}} &\longrightarrow (\dots\dots)_{\text{BCD}} \\
 \Rightarrow & \quad \begin{array}{ccc} 9 & 4 & 3 \\ \downarrow & \downarrow & \downarrow \\ 1001 & 0100 & 0011 \end{array} \\
 \therefore & (943)_10 = (100101000011)_2
 \end{aligned}$$

Advantages of BCD Code

- The main advantage of the BCD code is relative ease of converting to and from decimal.
 - Only 4-bit code groups for the decimal digits "0 through 9" need to be remembered.
 - This case of conversion is especially important from the hardware standpoint.
⇒ In 4-bit binary formats, total number of possible representation = $2^4 = 16$
- Then,
- | |
|-----------------------|
| Valid BCD codes = 10 |
| Invalid BCD codes = 6 |
- ⇒ In 8-bit binary formats,
- | |
|---------------------------------------|
| Valid BCD codes = 100 |
| Invalid BCD codes = $256 - 100 = 156$ |

1.2.2 Excess-3 Code

- It is a 4-bit code.
- It can be derived from BCD code by adding "3" to each coded number.
- It is an "unweighted code".

- It is a "self-complimenting code" i.e. the 1's compliment of an excess-3 number is the excess-3 code for the 9's compliment of corresponding decimal number.
- This code is used in arithmetic circuits because of its property of self complimenting.

Example-1.13 Convert $(48)_{10}$ into Excess-3 code.

Solution:

$$\begin{array}{r} 4 \\ +3 \\ \hline 7 \end{array} \quad \begin{array}{r} 8 \\ +3 \\ \hline 11 \end{array}$$

↓ ↓

0111 1011

$$\therefore (48)_{10} = (01111011)$$

↓
equivalent
4-bitbinary

Example-1.14 Represent the decimal number 6248 in

- BCD code
- Excess-3 code
- 2421 code

Solution:

- BCD code

$$\begin{array}{cccc} 6 & 2 & 4 & 8 \\ 0110 & -0010 & -0100 & -1000 \end{array}$$

- Excess-3 = BCD + 3

$$= 1001 \ 0101 \ 0111 \ 1011$$

- 2421 code

2	4	2	1	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
1	0	1	1	5
1	1	0	0	6
1	1	0	1	7
1	1	1	0	8
1	1	1	1	9

$$6248 = 1100 \ 0010 \ 0100 \ 1110$$

Example-1.15 The state of a 12-bit register is 100010010111. What is its content if it represents?


- Three decimal digits in BCD?
- Three decimal digits in Excess-3 code?

Solution:(i) In BCD \Rightarrow 1000 1001 0111; Decimal digits = 897(ii) In Excess-3 \Rightarrow 1000 1001 0111; Decimal digits = 564
 \downarrow \downarrow \downarrow
 $8-3=5$ $9-3=6$ $7-3=4$ **1.2.3 Gray Code**

- It is a very useful code also called "minimum distance code" in which two succeeding decimal equivalent gray codes differ in only one bit.
- It is also known as "Reflected code".
- It is an unweighted code, meaning that the bit positions in the code groups do not have any specific weight assigned to them.
- This code is not well suited for arithmetic operations but it finds application in input/output devices.
- These are used in instrumentation such as shaft encoders to measure angular displacement or in linear encoders for measurement of linear displacement.

Binary-to-Gray Conversion


- 'MSB' in the gray code is same as corresponding digit in binary number.
- Starting from "Left to Right", add each adjacent pair of binary bits to get next gray code bit. (Discard the carry if generated).

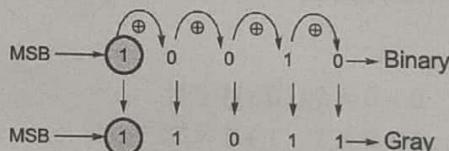Example-1.16 Convert $(10010)_2$ to gray code.**Solution:**

$$\therefore (10010)_2 = (11011)_{\text{Gray}}$$

Gray-to-Binary Conversion

- "MSB" of Binary is same as that of gray code .
- Add each binary bit to the gray code bit of the next adjacent position (discard the carry if generated), to get next bit of the binary number.

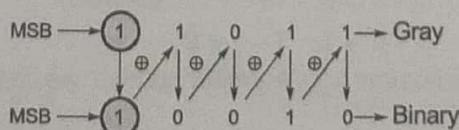Example-1.17 Convert $(11011)_{\text{Gray}}$ to Binary code.**Solution:**

$$\therefore (11011)_{\text{Gray}} = (10010)_2$$

Various Binary Codes

Table-1.2 Various binary codes

Decimal Number	Binary				BCD				Excess-3				Gray			
	B_3	B_2	B_1	B_0	D	C	B	A	E_3	E_2	E_1	E_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0
1	0	0	0	1	0	0	0	1	0	1	0	0	0	0	0	1
2	0	0	1	0	0	0	1	0	0	1	0	1	0	0	0	1
3	0	0	1	1	0	0	1	1	0	1	1	1	0	0	1	0
4	0	1	0	0	0	1	0	0	1	0	0	0	0	0	1	1
5	0	1	0	1	0	1	0	1	1	0	0	1	1	0	1	0
6	0	1	1	0	0	1	1	0	1	0	1	0	0	1	0	0
7	0	1	1	1	0	1	1	1	1	0	1	1	1	1	1	0
8	1	0	0	0	1	0	0	0	1	0	1	1	1	1	0	1
9	1	0	0	1	1	0	0	1	1	1	0	0	1	1	1	1
10	1	0	1	0									1	1	1	0
11	1	0	1	1									1	0	1	0
12	1	1	0	0									1	0	1	1
13	1	1	0	1									1	0	0	1
14	1	1	1	0									1	0	0	0
15	1	1	1	1										1	0	0

1.3 Arithmetic Operations

We are all familiar with the arithmetic operations like addition, subtraction, multiplication and division using decimal numbers. Such operations can also be performed on digital numbers.

1.3.1 Binary Addition

$$0 + 0 = 0; \quad 0 + 1 = 1$$

$$1 + 0 = 1; \quad 1 + 1 = 10$$

For example:

Add the binary numbers 110110 and 101101

$$\begin{array}{r}
 \begin{array}{c} \curvearrowleft \curvearrowright \\ 1 \ 1 \ 0 \ 1 \ 1 \ 0 \end{array} \\
 \Rightarrow \begin{array}{r} + 1 \ 0 \ 1 \ 1 \ 0 \ 1 \\ \hline \end{array}
 \end{array}
 \quad \text{Arrow indicates the carry propagation}$$

① 1 0 0 0 1 1
Carry

1.3.2 Binary Subtraction

$$0 - 0 = 0; \quad 10 - 1 = 1 \text{ (Borrow)}$$

$$1 - 0 = 1; \quad 1 - 1 = 0$$

While subtracting a large number from a smaller number, we can subtract the smaller from the larger and change the sign.

For example:

Subtract two binary numbers 11011 and 10110.

$$\begin{array}{r} 11011 \\ - 10110 \\ \hline 00101 \end{array}$$

Represents borrow

1.3.3 Binary Multiplication

Multiply two binary numbers 1010 and 101

$$\begin{array}{r} 1010 \times 101 \\ 1010 \\ 000 \times \\ 1010 \times \\ \hline 110010 \end{array}$$

Example-1.18 If $(10W1Z)_2 \times (15)_{10} = (Y01011001)_2$ then find the value of W, Y, Z.

Solution:

$$\begin{array}{r} 10W1Z \times 1111 \\ 10W1Z \\ 10W1Z \\ 10W1Z \\ \hline Y01011001 \end{array}$$

$(15)_{10} = (1111)_2$

Also,
 $W=1$

$\therefore W=Y=Z=1$

Example-1.19 $(1111)_2 \times (1111)_2 = ?$

Solution:

$$\begin{array}{r} 1111 \times 1111 \\ 1111 \\ 1111 \times \\ 1111 \times \\ 1111 \times \\ \hline 11100001 \end{array}$$

1.3.4 Octal Addition

$$0 + 0 = 0$$

$$0 + 2 = 2$$

$$1 + 6 = 7$$

$$1 + 7 = 0 \text{ with carry } 1$$

Whenever the generated number is greater than 7 then, after decimal addition it should be converted into octal.

For example:

$$7 + 2 = 9$$

$$\begin{array}{r} 8 \mid 9 \\ \hline 1 \rightarrow 1 = 11 \end{array}$$

$$7 + 17 = 26$$

$$\begin{array}{r} 8 \mid 14 \\ \hline 1 \rightarrow 6 = 16 \end{array}$$

Example - 1.20 Add two octal numbers 567 and 243.

Solution:

$$\Rightarrow \begin{array}{r} 1 \\ 567 \\ + 243 \\ \hline 1032 \end{array} \quad \text{Here,} \quad \begin{array}{r} 7+3=10 \\ 8 \mid 10 \\ \hline 1 \rightarrow 2 \end{array}$$

$$\begin{array}{r} 10+1=11 \\ 8 \mid 11 \\ \hline 1 \rightarrow 3 \end{array}$$

1.3.5 Octal Subtraction

Perform subtraction operation $(723)_8 - (564)_8$

Then,

$$\Rightarrow \begin{array}{r} 723 \\ - 564 \\ \hline 137 \end{array} \quad \begin{array}{l} \text{--- Represents the borrow} \\ \text{---} \end{array}$$

1.3.6 Hexadecimal Addition

$$1+1=2$$

$$1+9=A$$

$$1+15=0 \quad \text{with carry '1'}$$

$$A+A=14$$

$$\begin{array}{r} 16 \mid 20 \\ \hline 1 \rightarrow 4 \end{array}$$

Example - 1.21

Add two Hexadecimal numbers ADD + DAD = ?

Solution:

$$\Rightarrow \begin{array}{r} 1 \\ \text{ADD} \\ + \text{DAD} \\ \hline 188A \end{array}$$

$$\begin{array}{r} 16 \mid 26 \\ \hline 1 \rightarrow A \end{array}$$

$$\begin{array}{r} 16 \mid 24 \\ \hline 1 \rightarrow 8 \end{array}$$

$$\begin{array}{r} 16 \mid 24 \\ \hline 1 \rightarrow 8 \end{array}$$

1.3.7 Hexadecimal Subtraction

Perform subtraction operation $(974B)_{16} - (587C)_{16}$

$$\Rightarrow \begin{array}{r} 974B \\ - 587C \\ \hline 3ECF \end{array} \quad \begin{array}{l} \text{--- Represents borrow} \\ \text{---} \end{array}$$

1.3.8 BCD Addition

- Addition is the most important operation because subtraction, multiplication, and division can all be done by a series of additions or two's-compliment additions.
- The procedure for BCD addition is as follows:
 - (i) Add the BCD numbers as similar to adding two binary numbers.

- (ii) If the sum is 9(1001) or less, it is a valid BCD answer; leave it as it is.
- (iii) If the sum is greater than 9 or if there is a carry-out of the MSB, it is an invalid BCD number.
- (iv) If it is invalid, add 6 (0110) to the result to make it valid. Any carry-out of the MSB is added to the next-most-significant BCD digit.
- (v) Repeat steps 1 to 4 for each group of BCD bits.

Example - 1.22 Convert the decimal number $(76)_{10}$ and $(94)_{10}$ in BCD and add them. Convert the result back to decimal to check the answer.

Solution:

$$\begin{array}{r} 76 = 0111 \quad 0110 \\ + 94 = 1001 \quad 0100 \\ \hline 10000 \quad 1010 \end{array}$$

From the rule we add (0110)

$$\begin{array}{r} 10000 \quad 1010 \\ + 0110 \quad 0110 \\ \hline 10110 \quad 0000 \end{array}$$

In BCD $\Rightarrow (170)_{10}$

Also, we have,

$$\begin{array}{r} (76)_{10} \\ +(94)_{10} \\ \hline (170)_{10} \end{array}$$

1.4 Signed Number Representation

So far, we have considered only positive numbers but the representation of negative number is also equally important. There are basically two ways of representing signed number as

- Sign magnitude representation.
- r's compliment representation.

1.4.1 Sign Magnitude Representation

- In sign magnitude form, the most significant bit (MSB) is used to represent sign (0 for positive and 1 for negative number) and the remaining bits are used to represent the magnitude of the number. For example, a 4-bit binary number 0011 represents a positive number (3) and 1011 represents a negative number (-3).
- In general maximum positive number that can be represented using sign magnitude form is $(2^{n-1}-1)$ and the maximum negative number that can be represented is $-(2^{n-1}-1)$; where n is the number of bits.

1.4.2 r's Compliment Representation

In r's compliment representation 'r' represents the radix. It can be divided as

- $(r-1)$'s compliment.
- r's compliment.

Depending upon the radix or base of different number systems the compliment representations are

- Binary number system:
 - 1's complement
 - 2's complement
 - 9's complement
 - 10's complement
- Decimal number system:

- Octal number system:
 - 7's complement
 - 8's complement
- Hexadecimal number system:
 - F's complement
 - 16's complement
- To determine the $(r - 1)$'s compliment subtract the given number from the maximum possible number in the given base (i.e. $(2^n - 1)$) number in binary.
for example, for 4 bit maximum possible number = $2^4 - 1 = (15)_{10} = (1111)_2$

Example-1.23 Determine 9's compliment of a decimal number 2689?**Solution:**

For a decimal number maximum possible number of 4 digit is 9999

$$\therefore \text{9's compliment of 2689 is } \begin{array}{r} 9999 \\ - 2689 \\ \hline 7310 \end{array}$$

Example-1.24 Determine 7's compliment of octal number 5674?**Solution:**

⇒ For an octal number, maximum possible number, maximum possible number of 4 digit is 7777.

$$\therefore \text{7's compliment of 5674 is } \begin{array}{r} 7777 \\ - 5674 \\ \hline 2103 \end{array}$$

Example-1.25 Determine F's compliment of HEX = 2689.**Solution:**

$$\text{FFFF} - 2689 = D976$$

NOTE: To determine the r 's compliment, first write $(r - 1)$'s compliment of given number then add 1 in the least significant position.

Example-1.26 Determine 8's compliment of an octal number 2670?**Solution:**

$$\begin{array}{r} 7777 \\ - 2670 \\ \hline 5107 \end{array}$$

7's complement $\Rightarrow 5107$

Now,

$$8\text{'s compliment} = 7\text{'s compliment} + 1$$

$$= 5107 + 1 = 5108 \text{ octal} = 5108 \quad \begin{matrix} \uparrow \\ \text{Octal} \end{matrix} = 5110$$

Example-1.27Given that $(EOB)_H - (ABF)_H = Y$. The radix 8's compliment of Y is

- (a) 844
(c) 6264

- (b) 1514
(d) 6263

Solution: (c)

$$\begin{aligned}
 (EOB)_H - (ABF)_H &= (34C)_H \\
 (34C)_H &= (001101001100)_2 = (1514)_8 \\
 7\text{'s compliment} &= (6263)_8 \\
 8\text{'s compliment} &= (6263)_8 + 1 = (6264)_8
 \end{aligned}$$

One's Compliment Representation

- In a binary number if we replace each 0 by 1 and each 1 by 0, the obtained binary number is called one's compliment of the given binary number.
- For example, while $(0111)_2$ represents $(+7)_{10}$ and $(1000)_2$ represents $(-7)_{10}$. Here, the MSB denotes the sign of the number (0 for positive and 1 for negative number is obtained by taking one's compliment of that number).
- Thus, the maximum positive and negative number that can be represented using one's compliment are $(2^{n-1} - 1)$ and $-(2^{n-1} - 1)$ respectively.

Example-1.28 The one's compliment representation of a binary number 101101 is**Solution:****Method 1:**

One's compliment can be obtained by subtracting the given number with 111111

$$\begin{array}{r}
 111111 \\
 \underline{-} 101101 \\
 \hline
 010010
 \end{array}
 \Rightarrow \text{One's complement}$$

Method 2:

One's compliment of the given number can be obtained by replacing each 0 with 1 and each 1 with 0.

$$\therefore 101101 \rightarrow 010010$$

Two's Compliment Representation

- By adding a '1' to the one's compliment representation of a binary number we can get the 2's compliment of that number.
- For n -bit number, the maximum positive number that can be represented is $(2^{n-1} - 1)$ and the maximum negative number that can be represented is $-(2^{n-1})$.

Example-1.29 The two's compliment of binary number 10110.11 is**Solution:**

One's compliment of the given binary number can be obtained by replacing its 0 by 1 and 1 by 0.

$$\therefore 10110.11 \rightarrow 01001.00$$

Two's compliment can be obtained by adding 1 at the LSB of one's complimented representation of the given number.

$$01001.00 + 1 = 01001.01$$

Remember

Special case of 2's compliment representation: Whenever a signed number has a 1 in the sign bit and all 0's for the magnitude bits, the decimal equivalent is -2^n , where n is the number of bits in the magnitude. For example

$$(1000)_2 = -8 \text{ and } (10000)_2 = -16$$

Characteristics of 2's compliment representation:

- There is only one way to represent a zero.
- The 2's compliment of 0 is 0.
- In 2's compliment representation, to extend the number of bits copy MSB bit only.

For example

$$-7 \rightarrow 1001$$

$$-7 \rightarrow 111001$$

$$-7 \rightarrow 1111001$$

- The 2's compliment representation of a 2's complimented binary number is equal to the binary number itself.

For example

Binary number of 7 = 0111.

Two's compliment of 7 is 1001

Two's compliment of 1001 is 0110

$$\begin{array}{r} 0110 \\ + 1 \\ \hline 0111 \end{array} \Rightarrow 7$$

- A negative number may be converted into a positive number by finding its two's compliment.

Signed Binary Numbers

Table-1.3

Decimal	Binary	Sign Magnitude Form	1's compliment form	2's compliment form
+7	0111	0111	0111	0111
+6	0110	0110	0110	0110
+5	0101	0101	0101	0101
+4	0100	0100	0100	0100
+3	0011	0011	0011	0011
+2	0010	0010	0010	0010
+1	0001	0001	0001	0001
+0	0000	0000	0000	0000
-0	-	1000	1111	-
-1	-	1001	1110	1111
-2	-	1010	1101	1110
-3	-	1011	1100	1101
-4	-	1100	1011	1100
-5	-	1101	1010	1011
-6	-	1110	1001	1010
-7	-	1111	1000	1001
-8	-	-	-	1000

- Most of the digital systems perform subtraction by using 2's compliment method or by using 1's compliment method. The advantage of performing subtraction by using compliment method is reduction in hardware i.e. instead of using separate digital circuits for addition and subtraction, only adding circuit is needed.
- To perform subtraction using 2's (or 1's) compliment method, represent both the subtrahend and the minuend by the same number of bits.
- Take the 2's (1's) compliment of the subtrahend including the sign bit. Keep the minuend in its original form, and add the 2's (or 1's) compliment of the subtrahend to it.

- In 2's compliment subtraction if carry is generated ignore it. If the MSB of the sum is '0' the result is in its true binary form, however if the MSB is '1' (whether there is a carry or not), the result is negative and the magnitude is in 2's compliment form.

Example - 1.30

Subtract 17 from 46 using 8-bit 2's compliment method.

Solution:

⇒ Binary form of 17 → 00010001

2's compliment of 17 → 11101111

Binary form of 46 → 00101110

$$\begin{array}{r}
 +46 \\
 -17 \\
 \hline
 29
 \end{array} \Rightarrow \begin{array}{r}
 00101110 \\
 +11101111 \\
 \hline
 \textcircled{1} 00011101
 \end{array}$$

↑
Carry
(ignore it)

Here, MSB is '0' so, the result is positive and in its normal binary form. Therefore, the result is 00011101 = 29.

Example - 1.31

Subtract decimal number 22 from 17 using 8 bit 2's compliment method.

Solution:

Binary form of 22 → 00010110

2's compliment of 22 → 11101010

Binary form of 17 → 00010001

$$\begin{array}{r}
 17 \\
 -22 \\
 \hline
 -5
 \end{array} \Rightarrow \begin{array}{r}
 00010001 \\
 +11101010 \\
 \hline
 11111011
 \end{array}$$

In the above addition, there is no carry. The MSB of the result is '1' hence, it is a negative number and the magnitude is in 2's compliment form.

∴ 2's compliment (11111011) = 00000101 = (5)₁₀

Therefore the answer is -5 in decimal representation.

- In 1's compliment subtraction, if carry is present, bring the carry around and add it to the LSB. This is called "add end around carry". If the MSB of the result is '0' is in its binary form. However, if the MSB of the result is '1', the result is negative and magnitude in 1's compliment form. To get the magnitude in binary take its 1's compliment.

Example - 1.32

Subtract 25 from 14 using 8-bit 1's compliment method.

Solution:

(i)

$$(25)_{10} \rightarrow (00011001)_2$$

$$(14)_{10} \rightarrow (00001110)_2$$

$$\text{1's compliment of } (14)_{10} \rightarrow (11110001)_2$$

$$\begin{array}{r}
 25 \\
 -14 \\
 \hline
 11
 \end{array} \Rightarrow \begin{array}{r}
 00011001 \\
 +11110001 \\
 \hline
 \textcircled{1}00001010
 \end{array}
 \begin{array}{l}
 \text{Carry} \\
 \downarrow \\
 +1
 \end{array}
 \begin{array}{r}
 00001011
 \end{array}$$

Since MSB is '0' means, the result is positive and is in pure binary form. Therefore, the result is $(00001011)_2 = (+11)_{10}$

(ii) 1's compliment of $(25)_{10} \rightarrow 11100110$

$$\begin{array}{r}
 -25 \\
 14 \\
 \hline
 -11
 \end{array} \Rightarrow \begin{array}{r}
 11100110 \\
 +00001110 \\
 \hline
 11110100
 \end{array}$$

There is no carry. The MSB is a '1' so, the result is negative and the magnitude is in 1's compliment form. Therefore the result is

1's compliment of $(11110100) = 00001011 = -11$


Example-1.33 A system has following negative numbers stored in 2's form as shown. The wrongly stored number is

- | | |
|-------------------------|-------------------------|
| (a) -32 as 11100000 | (b) -37 as 11011011 |
| (c) -48 as 11101000 | (d) -89 as 10100111 |


Solution: (c)

$$\begin{aligned}
 48_{10} &= (00110000)_2 \\
 -48_{10} &= 2\text{'s compliment of } 00110000 \\
 &= 11001111 + 1 = 11010000
 \end{aligned}$$

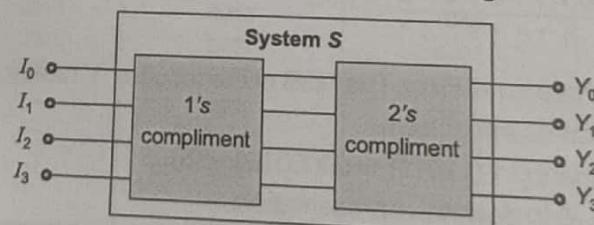Example-1.34 Consider a System S as shown in the figure below:



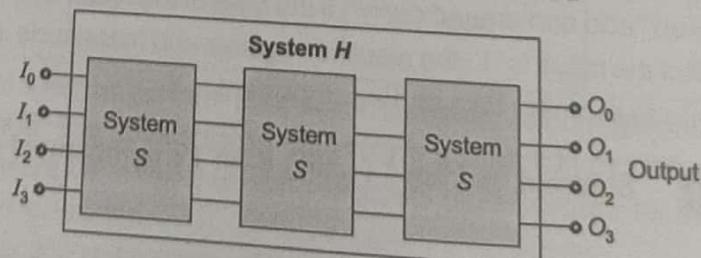System S performs 1's compliment of the input and then 2's compliment to produce output. A new System H is designed in which 3 S Systems are cascaded



- the applied input $(I_3 I_2 I_1 I_0)$ is 1010, then the output $(O_3 O_2 O_1 O_0)$ is
- | | |
|----------|----------|
| (a) 1010 | (b) 0101 |
| (c) 1101 | (d) 1100 |

Solution : (c)

Let a number N is given to the system

$$\text{output after 1's compliment} = 15 - N$$

$$\text{output after 2's compliment} = 16 - 15 + N = N + 1$$

3 such systems are connected in cascade.

So,

$$\text{Final output} = \text{Input} + (3)_{10} = 1010 + 0011 = 1101$$

1.5 Over Flow Concept

- If we add two same signed numbers and in the result if sign bit is opposite then it indicates "OVERFLOW".
- When "OVERFLOW" occurs, then number of bits being increased by "1-bit in MSB".

1.5.1 Overflow Condition

- If X and Y are the MSB's of two number and Z is the resultant MSB after adding two numbers then overflow condition is, $\bar{X}\bar{Y}Z + XY\bar{Z}$
- In 2's compliment arithmetic operation, if carry in and carry out from MSB bit position are different then it indicates overflow. $C_{in} \oplus C_{out}$

1.5.2 EX-OR Logic Diagram for overflow

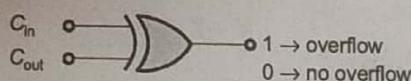


Figure-1.1

[Since, $A \oplus A = 0$ and $A \oplus \bar{A} = 1$]

Example-1.35

How many bits are 1 in the binary representation of $3 \times 512 + 7 \times 64 + 5 \times 8 + 3$

- | | |
|--------|--------|
| (a) 8 | (b) 9 |
| (c) 10 | (d) 12 |

Solution : (b)

Given, $3 \times 512 + 7 \times 64 + 5 \times 8 + 3 = (3753)_8 \rightarrow (011111101011)_2$

Number of 1's are $2 + 3 + 2 + 2 = 9$.

Example-1.36 Which one of the following is the correct sequence of the numbers represented in the series $(2)_3, (10)_4, (11)_5, (14)_6, (22)_7, \dots$?

- | | |
|--------------------------|--------------------------|
| (a) 2, 3, 4, 5, 6, ... | (b) 2, 4, 6, 8, 10, ... |
| (c) 2, 4, 6, 10, 12, ... | (d) 2, 4, 6, 10, 16, ... |

Solution : (d)

Converting into decimal,

$$(2)_3 = 2 \times 3^0 = 2$$

$$(10)_4 = 1 \times 4^1 + 0 \times 4^0 = 4$$

$$(11)_5 = 1 \times 5^1 + 1 \times 5^0 = 6$$

$$(14)_6 = 1 \times 6^1 + 4 \times 6^0 = 10$$

$$(22)_7 = 2 \times 7^1 + 2 \times 7^0 = 16$$

Example - 1.37 The base of the number system for the addition operation $24 + 14 = 41$ to be true is

- (a) 8
(c) 6

- (b) 7
(d) 5

Solution : (b)

Let the base is x , then

$$\begin{aligned} (24)_x + (14)_x &= (41)_x \\ (2x^2 + 4x) + (x^2 + 4x) &= 4x^2 + x \\ 3x^2 + 8x &= 4x^2 + x \\ x^2 = 7x &\Rightarrow x = 7 \end{aligned}$$

Example - 1.38 $X = 01110$ and $Y = 11001$ are two 5-bit binary numbers represented in two's compliment format. The sum of X and Y represented in two's compliment format using 6 bits is

- (a) 100111
(c) 000111

- (b) 001000
(d) 101001

Solution : (c)

$$\begin{array}{r} X = 01110 \\ Y = 11001 \\ \hline X + Y = \underline{\quad 0\ 0\ 1\ 1\ 1} \end{array}$$

Carry is discarded in the addition of numbers represented in 2's compliment form. $X + Y$ in 6 bits is 000111.

Remember



- BCD code is used in calculators, counters, digital voltmeters, digital clocks etc.
- BCD code has the advantage that it can be easily converted to and from the decimal code.
- Gray code is also known as "minimum distance code".
- A group of bits is called "word".
- "CHUNKING" is replacing a longer string by a shorter one.
- The largest number that can be represented by using N -bits is $(2^N - 1)_{10}$.
- In self complimented weighted code, the sum of each weightage is equal to 9.
- The weighted codes 2421, 3321, 4311 and 5211 are also self complimented code.
- Excess-3 code is unweighted self complimentary code.
- Integer part will increase whenever there is conversion from higher base to lower base and vice-versa.
- Fraction part will decrease whenever there is a conversion from higher base to the lower base and vice-versa.

Student's
Assignments

1

Q.1 List out the rules for the BCD (Binary Coded Decimal) addition with corresponding examples?

Q.2 For two binary numbers $X = 1010100$ and $Y = 1000011$. Perform the subtraction.

(i) $X - Y$

(ii) $Y - X$ by using 2's compliment method.**Answer: (Conventional)**

2. (i) (0010001) (ii) -(0010001)

Student's
Assignments

2

Q.1 If we convert a binary sequence, $(1100101 \cdot 1011)_2$ into its octal equivalent as (X)s, the value of 'X' will be

- (a) (145.13) (b) (145.54)
 (c) (624.54) (d) (624.13)

Q.2 A binary $(11011)_2$ may be represented by following ways:

1. $(33)_8$ 2. $(27)_{10}$
 3. $(10110)_{GRAY}$ 4. $(1B)_H$

Which of these above is/are correct representation?

- (a) 1, 2 and 3 (b) 2 and 4
 (c) 1, 2, 3 and 4 (d) only 2

Q.3 Consider $X = (54)_b$, where 'b' is the base of the number system. If $\sqrt{X} = 7$ then base 'b' will be

- (a) 7 (b) 8
 (c) 9 (d) 10

Q.4 Addition of all gray code to convert decimal (0–9) into gray code is

- (a) 129 (b) 108
 (c) 69 (d) 53

Q.5 The decimal equivalent of hexadecimal number of '2A0F' is

- (a) 17670 (b) 17607
 (c) 17067 (d) 10767

Q.6 A new Binary Coded Pentary (BCP) number system is proposed in which every digit of a base-5 number is represented by its corresponding 3-bit binary code. For example, the base-5 number 24 will be represented by its BCP code 010100. In this numbering system, the BCP code 100010011001 corresponds to the following number in base-5 system

- (a) 423 (b) 1324
 (c) 2201 (d) 4231

Q.7 The sign-magnitude form and 2's complement form of a signed binary number $(10111)_2$ are:

- (a) -23 and -25 (b) -23 and -9
 (c) -7 and -23 (d) -7 and -9

Q.8 The number of digit '1' present in the binary representation of the number $(1199)_{12}$ is

- (a) 7 (b) 8
 (c) 10 (d) 12

Q.9 When signed numbers are used in binary arithmetic, then which one of the following notations would have unique representation for zero?

- (a) Sign magnitude (b) 1'S complement
 (c) 2'S complement (d) 9'S complement

Q.10 A signed integer has been stored in a byte using 2's complement format. We wish to store the same integer in 16-bit word. We should copy the original byte to the less significant byte of the word and fill the more significant byte with

- (a) 0 (b) 1
 (c) equal to the MSB of the original byte
 (d) complement of the MSB of the original byte.

Q.11 The result of $(54)_{10} - (54)_{16}$, expressed in 6-bit 2's complement representation is given by

- (a) 111110 (b) 101110
 (c) 100010 (d) 100011

Answer Key :

1. (b) 2. (c) 3. (c) 4. (d) 5. (d)
 6. (d) 7. (d) 8. (a) 9. (c) 10. (c)
 11. (c)



Boolean Algebra & Minimization Techniques

Introduction

- The binary operations performed by any digital circuit with the set of elements 0 and 1, are called logical operation or logic function. The algebra used to symbolically represent the logic function is called Boolean algebra. It is a two state algebra invented by George Boole in 1854.
- Thus, a Boolean algebra is a system of mathematic logic for the analysis and designing of digital systems.
- A variable or function of variables in Boolean algebra can assume only two values, either a '0' or a '1'. Hence, (unlike another algebra) there are no fractions, no negative numbers, no square roots, no cube roots, no logarithms etc.

2.1 Logic Operations

In Boolean algebra, all the algebraic functions performed is logical. These actually represent logical operations. The AND, OR and NOT are the basic operations in Boolean algebra. In addition to these operations, there are some derived operation such as NAND, NOR, EX-OR, EX-NOR in Boolean algebra.

2.1.1 AND Operation

The AND operation in Boolean algebra is similar to the multiplication in ordinary algebra. It is a logical operation performed by AND gate.

AND operation:

$$\begin{array}{l} A \cdot A = A \\ A \cdot 0 = 0 \quad \rightarrow \text{Null law} \\ A \cdot 1 = A \quad \rightarrow \text{Identity law} \\ A \cdot \bar{A} = 0 \end{array}$$

2.1.2 OR Operation

The OR operation in Boolean algebra is performed by OR-gate.
OR operation:



Theory with Solved Examples

MADE EASY

Publications

www.madeeasypublications.org

$A + A = A$	
$A + 0 = A$	Null law
$A + 1 = 1$	Identity law
$A + \bar{A} = 1$	

2.1.3 NOT Operation

The NOT operation in Boolean algebra is similar to the complementation or inversion in ordinary algebra. The NOT operation is indicated by a bar ($\bar{}$) or (' \prime ') over the variable.

Example: $A \xrightarrow{\text{NOT}} \bar{A}$ or A' (complementation law)

and

$\bar{\bar{A}} = A \Rightarrow$ double complementation law.

NOT operation is performed by NOT gate.

2.1.4 NAND Operation

The NAND operation is AND operation followed by NOT operation i.e. the negation of AND gate operation is performed by the NAND gate.

2.1.5 NOR Operation

The NOR operation is OR operation followed by NOT operation. i.e. the negation of OR gate operation is performed by the NOR gate.

2.2 Laws of Boolean Algebra

The Boolean algebra is governed by certain well defined rules and laws.

2.2.1 Commutative Laws

- The commutative law allows change in position of AND or OR variables.
 - $A + B = B + A$
Thus, the order in which the variables are ORed is immaterial.
 - $A \cdot B = B \cdot A$
Thus, the order in which the variables are ANDed is immaterial.
- This law can be extended to any number of variables.

2.2.2 Associative Laws

- The associative law allows grouping of variables.
 - $(A + B) + C = A + (B + C)$
Thus, the way the variables are grouped and ORed is immaterial.
 - $(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Thus, the way the variables are grouped and ANDed is immaterial.
- This law can be extended to any number of variables.

2.2.3 Distributive Laws

- The distributive law allows factoring or multiplying out of expressions.
 - $A(B + C) = AB + AC$
 - $A + BC = (A + B)(A + C)$
- This law is applicable for single variable as well as a combination of variables.

2.2.4 Idempotence Laws

Idempotence means the same value.

$$(i) A \cdot A = A$$

i.e. ANDing of a variable with itself is equal to that variable only.

$$(ii) A + A = A$$

i.e. ORing of a variable with itself is equal to that variable only.

2.2.5 Absorption Laws

$$(i) A + AB = A(1 + B) = A$$

$$(ii) A(A + B) = A$$

2.2.6 Involutionary Law

This law states that, for any variable 'A'

$$\bar{\bar{A}} = (A')' = A$$

2.3 Boolean Algebraic Theorems

2.3.1 De Morgan's Theorem

- De Morgan's theorem represents two of the most important rules of Boolean algebra.

$$(i) \overline{A \cdot B} = \bar{A} + \bar{B}$$

Thus, the complement of the product of variables is equal to the sum of their individual complements.

$$(ii) \overline{A+B} = \bar{A} \cdot \bar{B}$$

Thus, the complement of a sum of variables is equal to the product of their individual complements.

- The above two laws can be extend for 'n' variables as

$$\overline{A_1 \cdot A_2 \cdot A_3 \cdots A_n} = \bar{A}_1 + \bar{A}_2 + \cdots + \bar{A}_n$$

$$\text{and } \overline{A_1 + A_2 + \cdots + A_n} = \bar{A}_1 \cdot \bar{A}_2 \cdot \bar{A}_3 \cdot \bar{A}_4 \cdots \bar{A}_n$$

2.3.2 Transposition Theorem

Theorem:

$$(AB + \bar{A}C) = (A + C)(\bar{A} + B)$$

Proof:

$$\text{RHS} = (A + C)(\bar{A} + B)$$

$$= A\bar{A} + \bar{A}C + AB + CB$$

$$= 0 + \bar{A}C + AB + BC$$

$$= \bar{A}C + AB + BC(A + \bar{A})$$

$$= AB + ABC + \bar{A}C + \bar{A}BC$$

$$= AB + \bar{A}C = \text{LHS}$$

2.3.3 Consensus Theorem/Redundancy Theorem

- This theorem is used to eliminate redundant term.
- A variable is associated with some variable and its compliment is associated with some other variable and the next term is formed by the left over variables, then the term becomes redundant.
 - (i) Contains 3-variables.
 - (ii) Each variable present in two terms.
 - (iii) Only one variable is in complemented or uncomplemented form.

Then, the related terms to that complemented and uncomplemented variable is the answer.

- Consensus theorem can be extended to any number of variables.

e.g. $AB + \bar{A}C + BC = AB + \bar{A}C$

Example - 2.1

$$AB + B\bar{C} + AC = AC + B\bar{C}$$

Solution:

Proof:

$$\begin{aligned} \text{LHS} &= AB + B\bar{C} + AC \\ &= AB(C + \bar{C})B\bar{C}(A + \bar{A}) + A(B + \bar{B}) \\ &= ABC + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}C \\ &= ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C \\ &= AC(B + \bar{B}) + B\bar{C}(A + \bar{A}) = AC + B\bar{C} = \text{RHS} \end{aligned}$$

Example - 2.2

$$(A + B)(\bar{B} + C)(C + A) = (A + B)(\bar{B} + C)$$

Solution:

Proof:

$$\begin{aligned} \text{LHS} &= (A + B)(\bar{B} + C)(C + A) \\ &= (A\bar{B} + AC + BC)(C + A) \\ &= A\bar{B}C + AC + BC + A\bar{B} + AC + ABC = AC + BC + A\bar{B} \\ \text{RHS} &= (A + B)(\bar{B} + C) = A\bar{B} + AC + BC = \text{LHS} \end{aligned}$$

2.3.4 Duality Theorem

- "Dual expression" is equivalent to write a negative logic of the given boolean relation. For this we,
 - (i) Change each OR sign by an AND sign and vice-versa.
 - (ii) Complement any '0' or '1' appearing in expression.
 - (iii) Keep literals as it is.

2.3.5 Complementary Theorem

- For obtaining complement expression we
 - (i) Change each OR sign by AND sign and vice-versa.
 - (ii) Complement any '0' or '1' appearing in expression.
 - (iii) Complement the individual literals.

2.3.6 Summary Table

Table-2.1

Theorem No.	Theorem
1	$A + 0 = A$
2	$A \cdot 1 = A$
3	$A + 1 = 1$
4	$A \cdot 0 = 0$
5	$A + A = A$
6	$A \cdot A = A$
7	$A + \bar{A} = 1$
8	$A \cdot \bar{A} = 0$
9	$A \cdot (B + C) = AB + AC$
10	$A + BC = (A + B)(A + C)$
11	$A + AB = A$
12	$A(A + B) = A$
13	$A + \bar{A}B = (A + B)$
14	$A(\bar{A} + B) = AB$
15	$AB + A\bar{B} = A$
16	$(A + B) \cdot (A + \bar{B}) = A$
17	$AB + \bar{A}C = (A + C)(\bar{A} + B)$
18	$(A + B)(\bar{A} + C) = AC + \bar{A}B$
19	$AB + \bar{A}C + BC = AB + \bar{A}C$
20	$(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$
21	$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$
22	$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \dots$

Example - 2.3Write complement function of, $f = A\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$ **Solution:**

$$\bar{f} = \text{Compliment of } f$$

$$\bar{f} = (\bar{A} + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + C)$$

NOTE

- For any logical expression, if we take two times Dual, we get same given expression as previous.
- For 1-time Dual, if we get same function or expression it is called "Self Dual Expression".
- With N -variables, maximum possible Self-Dual Function = $(2)^{2^n-1} = 2^{(2^n)/2}$.
- Remember that with N -variables, maximum possible distinct logic functions = 2^{2^n} .

2.4 Minimization of Boolean Functions

Every Boolean function must be reduced to as simple form as possible before realization, because every logic operation in the expression represents a corresponding element of hardware. Realization of a digital circuit with minimal expression has several advantages as:

- The number of logic gates will reduce.
- Power dissipation will decrease.
- The complexity of the circuit reduces
- The speed of operation will increase.
- The fan in may reduce.

The simple method of minimization of Boolean functions using certain algebraic rules which results in the reduction of number of terms and/or number of logical operations. The various theorems and rules that are already discussed are very useful for the simplification of Boolean expressions/functions.

Example-2.4

Simplify the Boolean function

$$F = (A + \overline{B}\overline{C})(A\overline{B} + ABC).$$

Solution:

$$\begin{aligned} \text{Using De' Morgan's theorem } (\overline{A + \overline{B}\overline{C}}) &= (\overline{A} \cdot \overline{\overline{B}\overline{C}})(A\overline{B} + ABC) = (\overline{ABC})(A\overline{B} + ABC) \\ &= \overline{ABC}A\overline{B} + \overline{ABC}BC = 0 \end{aligned}$$

Example-2.5

Let $F(A, B) = \overline{A} + B$, then the value of $f(f(x + y, y), z) = ?$

Solution:

⇒ Let

$$A = x + y, B = y$$

∴

$$f(x + y \cdot y) = (x + y)' + y = \overline{x}\overline{y} + y = \overline{x} + y$$

$$f((\overline{x} + y), z) = (\overline{x} + y)' + z = \overline{\overline{x}}\overline{y} + z = x\overline{y} + z$$

2.5 Representation of Boolean Functions

- A function of ' n ' Boolean variables denoted by $f(A_1, A_2, \dots, A_n)$ is another variable of algebra and takes one of the two possible values either 0 or 1. The various ways of representing a given function are discussed below:

Boolean Function Representation

Canonical form

All the terms contain all the variables either in complementary or in uncomplementary form.

Minimal form

Each term with minimum numbers of literal and expression with minimum number of terms.

Example:

$$F(A, B, C) = \overline{ABC} + ABC + \overline{A}\overline{B}\overline{C}$$

Example:

$$F(A, B, C) = A + ABC + \overline{A}\overline{B}C = A$$

- The term 'literal' means a binary variable either in complementary or in uncomplementary form.

2.5.1 Minterms and Maxterms

- n -binary variables have 2^n possible combinations.
- Minterm is a product term, it contains all the variables either complementary or uncomplementary form for that combination the function output must be '1'.
- Maxterm is a sum term, it contains all the variables either complementary or uncomplementary form for that combination the function output must be '0'.

For 3-Variable**Table-2.2**

A	B	C	Minterm	Maxterm
0	0	0	$m_0 = \bar{A}\bar{B}\bar{C}$	$M_0 = A+B+C$
0	0	1	$m_1 = \bar{A}\bar{B}C$	$M_1 = A+B+\bar{C}$
0	1	0	$m_2 = \bar{A}BC$	$M_2 = A+\bar{B}+C$
0	1	1	$m_3 = ABC$	$M_3 = A+\bar{B}+\bar{C}$
1	0	0	$m_4 = A\bar{B}\bar{C}$	$M_4 = \bar{A}+B+C$
1	0	1	$m_5 = A\bar{B}C$	$M_5 = \bar{A}+B+\bar{C}$
1	1	0	$m_6 = AB\bar{C}$	$M_6 = \bar{A}+\bar{B}+C$
1	1	1	$m_7 = ABC$	$M_7 = \bar{A}+\bar{B}+\bar{C}$

From the above table we conclude that:

- In "Minterms" we assign '1' to each uncomplemented variable and '0' to each complemented variable.
- In "Maxterms" we assign '0' to each uncomplemented variable and '1' to each complemented variable.

2.5.2 Sum of Product (SOP) Form

- The SOP expression contains OR operation among product terms. Each product term may be minterm or implicant.

$$Y = \bar{A}BC + A\bar{B} + AC$$

$$Y = A\bar{B} + B\bar{C}$$

- This form is also called the "disjunctive normal form".
- SOP expressions are realized using 2 level AND-OR circuit.
- SOP expression output is logic 1.

Example:

Table-2.3

Input (3-Variables)			Output (Y)
A	B	C	
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 \therefore Notation of SOP expression is,

$$f(A, B, C) = \Sigma m(3, 5, 6, 7)$$

$$\therefore Y = m_3 + m_5 + m_6 + m_7$$

also,

$$Y = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

2.5.3 Product of Sum (POS) Form

- The POS expression contains AND operation among sum terms.

Example: $Y = (A + \bar{B} + C) \cdot (\bar{B}\bar{C} + D)$

- This form is also called the "Conjunctive normal form".
- Each individual term in standard POS form is called *Maxterm*.
- POS expression output is Logic '0'.

Same as Table (2.3), we get

$$f(A, B, C) = \prod M(0, 1, 2, 4)$$

$$\therefore Y = M_0 \times M_1 \times M_2 \times M_4$$

also,

$$Y = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + C)$$

- We also conclude that from Table (2.3), and from above equations if,

$$Y = \Sigma m(3, 5, 6, 7)$$

then,

$$Y = \prod M(0, 1, 2, 4)$$

2.5.4 Standard Sum of Product Form

- In this form the function is the sum of product terms. Each product term contains all the variables of the function, either in complemented or uncomplemented form.
- It is also called canonical SOP form or expanded SOP form.

Example: Function $[Y = A + B\bar{C}]$ can be represented in canonical form as:

$$Y = A + B\bar{C} = A(B + \bar{B})(C + \bar{C}) + B\bar{C}(A + \bar{A})$$

$$= ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + \bar{A}B\bar{C}$$

$$Y = ABC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + \bar{A}B\bar{C}$$

2.5.5 Standard Product of Sum Form

- In this form the function is the product of sum terms. Each sum term contains all the variables of the function, either in complemented or uncomplemented form.
- This form is also called canonical POS form or expanded POS form.

Example: $Y = (B + \bar{C}) \cdot (A + \bar{B})$

Then, the canonical form of the given function

$$\begin{aligned} Y &= (B + C + A\bar{A})(A + \bar{B} + C\bar{C}) \\ &= (B + \bar{C} + A)(B + \bar{C} + \bar{A})(A + \bar{B} + C)(A + \bar{B} + \bar{C}) \end{aligned}$$

2.5.6 Truth Table Form

A truth table is a tabular form representation of all possible combinations of given function.

Example: $Y = \bar{A}B + \bar{B}C$

Then,

	A	B	C	Y
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

Example - 2.6

Simplify the function Y , which is given in the truth table.

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

Solution:

\Rightarrow

$$Y = \bar{A}\bar{B} + A\bar{B} \Rightarrow Y = \bar{B}$$

Example - 2.7

Simplify the expression $Y(A, B) = \text{IIM}(1, 3)$.

Solution:

$$(1)_{10} = (01)_2 = \bar{A}B \text{ (SOP)} = A + \bar{B} \text{ (POS)}$$

$$(3)_{10} = (11)_2 = AB \cdot (\text{SOP}) = \bar{A} + \bar{B} \text{ (POS)}$$

\therefore

$$Y(A, B) = (A + \bar{B})(\bar{A} + \bar{B}) = \bar{A}\bar{B} + A\bar{B} = \bar{B}$$

2.5.7 Dual Form

- Dual form is used to convert positive logic to the negative logic and vice-versa.
- In positive logic system, higher voltage is taken as logic '1' and in negative logic system, higher voltage is taken as logic '0'.

For example:

For (positive) logic


$$\text{Logic '1'} = 0 \text{ V}, \quad \text{Logic '0'} = -5 \text{ V}$$

For (negative) logic

$$\text{Logic '1'} = -0.8 \text{ V}, \quad \text{Logic '0'} = -1.7 \text{ V}$$

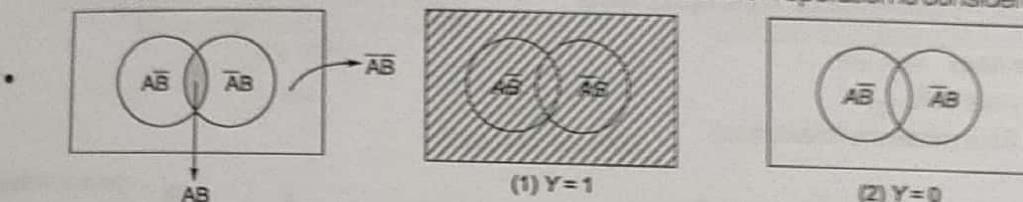
2.5.8 Venn Diagram Form

- A Boolean algebra can be represented by a Venn diagram in which each variable is considered as a set.
- The AND operation is considered as an intersection and the OR operation is considered as a union.



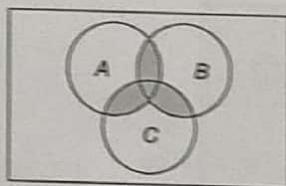Example-2.8

For the given Venn diagram minimize the expression for the shade area.



Solution:

The shaded area includes

$ABC, A\bar{B}\bar{C}, \bar{A}BC, A\bar{B}C$

∴

$$\begin{aligned} Y &= ABC + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} \\ &= AB + AC(B + \bar{B}) + BC(A + \bar{A}) = AB + BC + AC \end{aligned}$$

2.5.9 Statement Form

Example-2.9

A logic circuit have three inputs A, B and C and output Y, Y is '1' for the following combinations

- B and C are true (1)
- A and C are false (0)
- A, B and C are true (1)
- A, B and C are false (0)

Then the minimized expression for Y is

Solution:

Truth Table:

From the truth table, we get

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC$$

$$Y = \bar{A}\bar{C}(\bar{B} + B) + BC(A + \bar{A})$$

$$Y = BC + \bar{A}\bar{C}$$


	A	B	C	Y
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

2.5.10 Karnaugh Map

- The "Karnaugh map" is a graphical method which provides a systematic method for simplifying and manipulating the Boolean functions.
- In this technique, the information contained in a truth table or available in SOP or POS form is represented in the K-map.
- Although this technique may be used for any number of variables, it is generally used up to 6-variables beyond which it becomes very cumbersome.
- In n -variable K-map there are 2^n cells.


Two-variable K-Map

- Four cells
- Four minterms (maxterms)

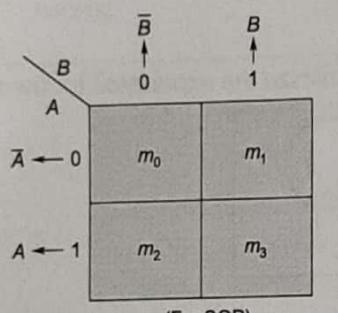

(For SOP)

(a)

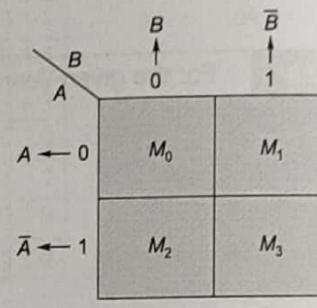


(For POS)

(b)

Figure-2.1: (a) and (b)


Three-variable K-map

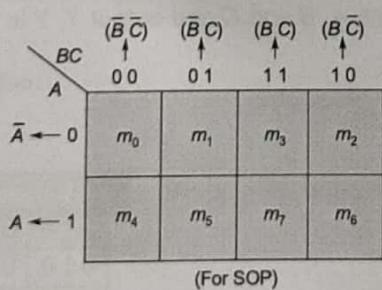- Eight cells
- Eight minterms (maxterms)



(For SOP)

(a)

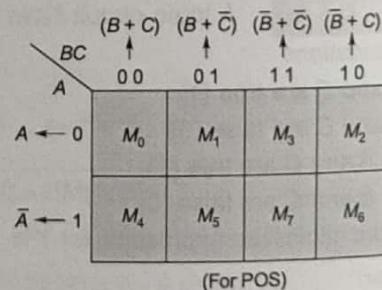

(For POS)

(b)

Figure-2.2: (a) and (b)

Four-variable K-map

- Sixteen cells
- Sixteen minterms (maxterms)

	$\overline{AB} \leftarrow 00$	$\overline{AB} \leftarrow 01$	$AB \leftarrow 11$	$A\bar{B} \leftarrow 10$
CD	$(\overline{C}\overline{D})$ 00	$(\overline{C}D)$ 01	(CD) 11	$(C\overline{D})$ 10
\overline{AB}	m_0	m_1	m_3	m_2
$\overline{A}\overline{B}$	m_4	m_5	m_7	m_6
AB	m_{12}	m_{13}	m_{15}	m_{14}
$A\bar{B}$	m_8	m_9	m_{11}	m_{10}

(For SOP)

(a)

	$\overline{AB} \leftarrow 00$	$(A+B) \leftarrow 00$	$(A+\overline{B}) \leftarrow 01$	$(\overline{A}+\overline{B}) \leftarrow 11$	$(\overline{A}+B) \leftarrow 10$
CD	$(C+D)$ 00	$(C+\overline{D})$ 01	$(\overline{C}+\overline{D})$ 11	$(\overline{C}+D)$ 10	
\overline{AB}	M_0	M_1	M_3	M_2	
$\overline{A}\overline{B}$	M_4	M_5	M_7	M_6	
AB	M_{12}	M_{13}	M_{15}	M_{14}	
$A\bar{B}$	M_8	M_9	M_{11}	M_{10}	

(For POS)

(b)

Table-2.3: (a) and (b)

Five-variable K-map

- 32-cells
- 32-minterms (maxterms)
- Here, we have $f(A, B, C, D, E)$

For $A = 0$				
DE	$\overline{D}\overline{E}$	$\overline{D}E$	DE	$D\overline{E}$
\overline{BC}	m_0	m_1	m_3	m_2
$\overline{B}C$	m_4	m_5	m_7	m_6
$B\overline{C}$	m_{12}	m_{13}	m_{15}	m_{14}
$B\overline{C}$	m_8	m_9	m_{11}	m_{10}

For $A = 1$				
DE	$\overline{D}\overline{E}$	$\overline{D}E$	DE	$D\overline{E}$
\overline{BC}	m_{16}	m_{17}	m_{19}	m_{18}
$\overline{B}C$	m_{20}	m_{21}	m_{23}	m_{22}
$B\overline{C}$	m_{28}	m_{29}	m_{31}	m_{30}
$B\overline{C}$	m_{24}	m_{25}	m_{27}	m_{26}

(From 0 – 15)

(From 16 – 31)

(For SOP)

Figure-2.4

Simplification of Logical Functions Using K-map:

Simplification of logical functions with K-map is based on the principle of combining terms in adjacent cells.

Grouping

- The expression for output 'Y' can be simplified by properly combining those cells in the K-map which contains 1's (for SOP form) or 0's (for POS form). The process for combining these 1's or 0's is called "Grouping".
- Groups are made up of 2, 4, 8, 16 and so on.
- By folding K-map over its edges, the number of 1's or 0's overlapping forms the Group.

Groups of Two (Pairs)

A pair of adjacent 1's in a K-map eliminates the variable that appears in complemented and uncomplemented form.

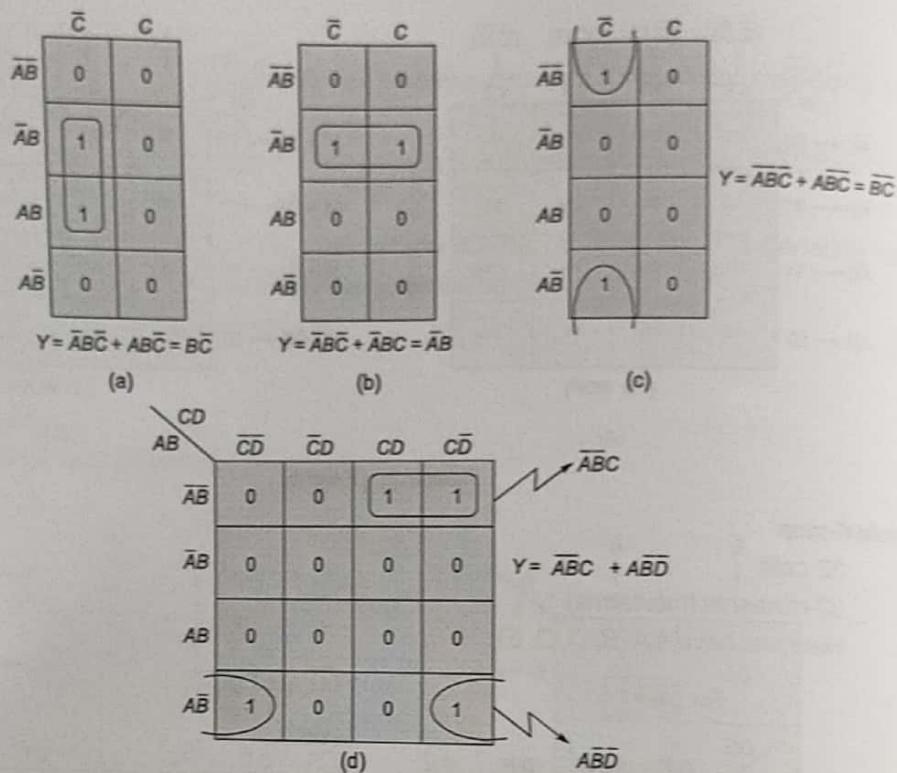


Figure-2.5: (a), (b), (c) and (d)

Groups of Four (Quads)

A quad of 1's eliminates those two variables that appear in both complemented and uncomplemented form.

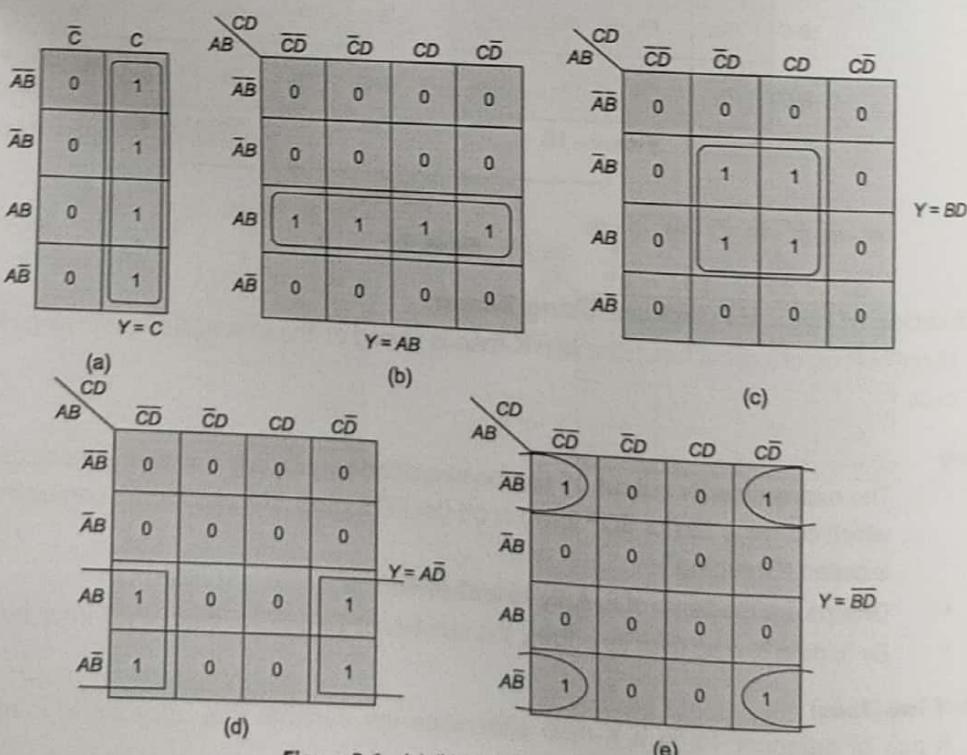


Figure-2.6: (a), (b), (c), (d) and (e)

Groups of Eight (Octets)

An octet of 1's eliminates those three variables that appear in both complemented and uncomplemented form.

CD	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
$\bar{A}B$	0	0	0	0
$\bar{A}\bar{B}$	1	1	1	1
$A\bar{B}$	1	1	1	1
AB	0	0	0	0

$Y = B$

CD	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
$\bar{A}B$	1	1	0	0
$\bar{A}\bar{B}$	1	1	0	0
$A\bar{B}$	1	1	0	0
AB	1	1	0	0

(b)

CD	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
$\bar{A}B$	1	1	1	1
$\bar{A}\bar{B}$	0	0	0	0
$A\bar{B}$	0	0	0	0
AB	1	1	1	1

$Y = \bar{B}$

(c)

CD	$\bar{C}D$	$C\bar{D}$	CD	$C\bar{D}$
$\bar{A}B$	1	0	0	1
$\bar{A}\bar{B}$	1	0	0	1
$A\bar{B}$	1	0	0	1
AB	1	0	0	1

(d)

Figure-2.7: (a), (b), (c) and (d)

NOTE: Those literals which are not same in the maxterm or minterms get eliminated.

Complete Simplification Rules:

- Draw the K-map and place 1's in those cells corresponding to the 1's in the truth table. Place 0's in the other cells.
- Examine the map for adjacent 1's and group those 1's which are not adjacent to any other 1's. These are called isolated 1's.
- Next, look for those 1's which are adjacent to only one other 1. Any pair containing such a 1.
- Any octet even it contains some 1's that have already been grouped.
- Any quad that contains one or more 1's which have not already been grouped.
- Group any pairs necessary to include any 1's that have not yet been grouped making sure to use the minimum number of groups.
- Form the OR sum of all the terms generated by each group.

Example-2.10

Simplify a four-variable logic function using K-map.

$f(A, B, C, D) = \Sigma m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ also implement the simplified expression with AND-OR logic.

Solution:


Given,

$$f(A, B, C, D) = \Sigma m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$


Step-I: Draw a 16-cell map and put 1's in such cell as given in $f(A, B, C, D)$.

Step-II: One group of 8, and two-groups of 4-one's are formed.

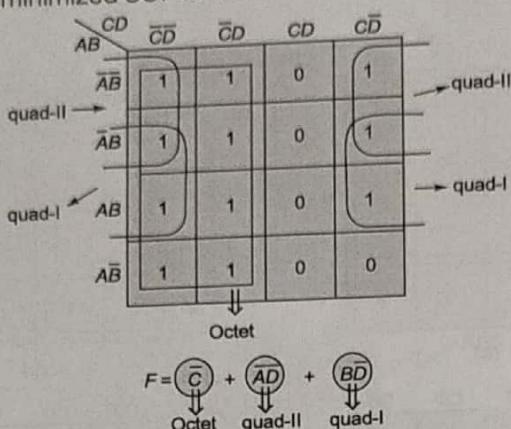Step-III: Finally we write minimized SOP form.



⇒ Gate implementation:

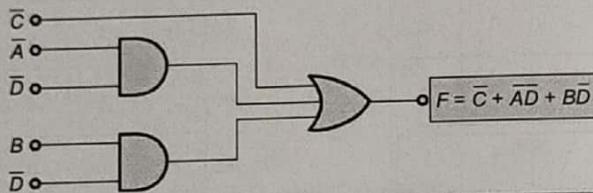

Don't Care Condition

- Some logic circuits can be designed so that there are certain input combinations for which there are no specified output levels, usually because these input combinations will never occur.
- So, a circuit designer is free to make the output for any "don't care" condition either a 0 or 1 in order to produce the simplest output expression.

Example-2.11 Convert the Boolean function from a sum of products form to a simplified product of sums form.

$$F(w, x, y, z) = \Sigma(0, 1, 2, 5, 8, 10, 13)$$

Solution:

Using K-Map for given function, we get

wz	yz	00	01	11	10
00	1	1			1
01		1			
11			1		
10	1				1

$$F = x'z' + xy'z + w'x'y'$$

To convert it in POS form (using 0's), we get

wz	yz	00	01	11	10
00	0			0	
01	0			0	0
11	0			0	0
10	0	0	0	0	0

$$F' = yz + xz' + xy + wx'z$$



or $F = (y' + z')(x' + z)(x' + y')(w' + x + z')$

Example-2.12 Simplify the given Boolean functions.

(i) $f(A, B, C, D) = \Sigma m(1, 3, 7, 11, 15) + d(0, 2, 5)$

(iii) $f(A, B, C, D) = \Pi M(4, 5, 6, 7, 8, 12). d(1, 2, 3, 9, 11, 14)$

Solution:

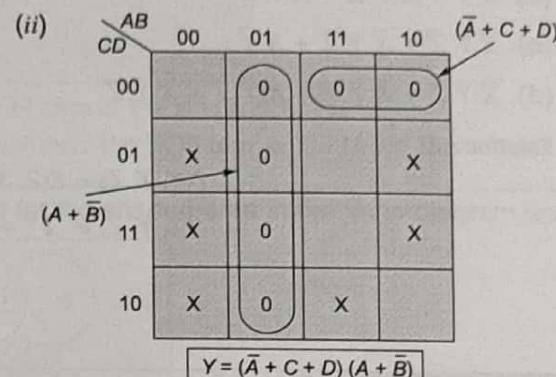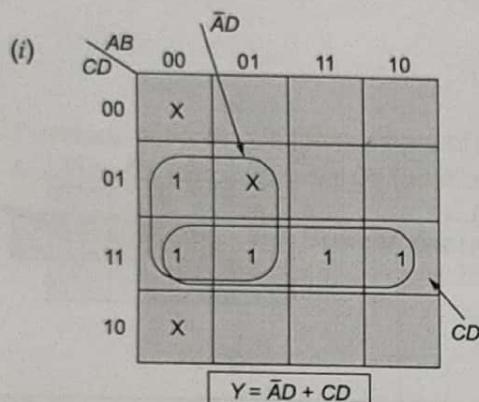

2.6 Implicants, Prime Implicants and Essential Prime Implicants

Implicant

Implicant is a product term on the given function for that combination the function output must be 1.


Prime Implicant

Prime implicant is a smallest possible product term on the given function, removing any one of the literal from which is not possible.


Essential Prime Implicant

Essential prime implicant is a prime implicant it must cover atleast one minterm, which is not covered by any other prime implicant.

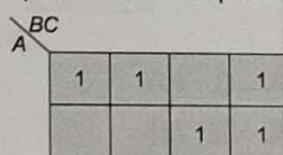Example-2.13 For the given K-map, find Prime Implicants and Essential Prime Implicants.



Solution:

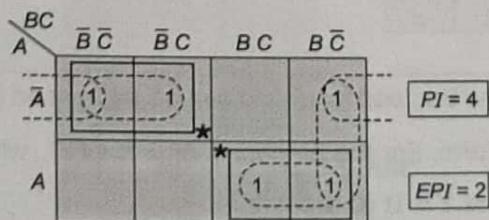

Prime implicant (PI) = $\bar{A}\bar{B}, \bar{A}\bar{C}, AB, B\bar{C}$

and Essential Prime Implicants (EPI) = $\bar{A}\bar{B}, AB$

Example-2.14 For the given Boolean function
 $f(X, Y, Z) = \sum(2, 3, 4, 5)$,

the minimal expression is


- (a) $\bar{X}Y + X\bar{Y}$
- (b) $\bar{X}Y + X\bar{Y}\bar{Z} + X\bar{Y}Z$
- (c) $\bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}$
- (d) $\bar{X}Y\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + X\bar{Y}Z$

Solution: (a)

$$f(X, Y, Z) = \sum(2, 3, 4, 5)$$

$$f(X, Y, Z) = X\bar{Y} + \bar{X}Y$$

∴

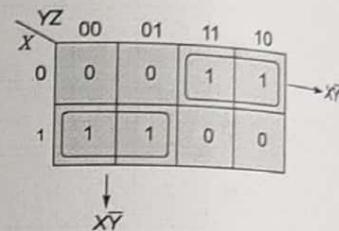

Example-2.15 A logic circuit implements the boolean function $F = \bar{X} \cdot Y + X \cdot \bar{Y} \cdot \bar{Z}$. It is found that the input combination $X = Y = 1$ can never occur. Taking this into account, a simplified expression for F is given by


- | | |
|---------------------------------------|---------------------------|
| (a) $\bar{X} + \bar{Y} \cdot \bar{Z}$ | (b) $X + Z$ |
| (c) $X - Z$ | (d) $Y + X \cdot \bar{Z}$ |

Solution: (d)

Truth table:

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	x
1	1	1	x

K-map:

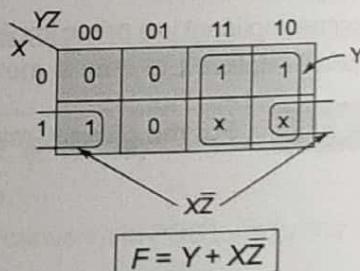

$$F = Y + XZ̄$$

Example-2.16 The Boolean functions can be expressed in canonical SOP (sum of products) and POS (product of sums) form. For the functions, $Y = A + \bar{B}C$, which are such two forms

- (a) $Y = \Sigma(1, 2, 6, 7)$ and $Y = \Pi(0, 2, 4)$
- (b) $Y = \Sigma(1, 4, 5, 6, 7)$ and $Y = \Pi(0, 2, 3)$
- (c) $Y = \Sigma(1, 2, 5, 6, 7)$ and $Y = \Pi(0, 1, 3)$
- (d) $Y = \Sigma(1, 2, 4, 5, 6, 7)$ and $Y = \Pi(0, 2, 3, 4)$



Solution : (b)

Plotting the 1's in Karnaugh map for the function $Y = A + \bar{B}C$ to represent SOP.


	BC	00	01	11	10
A	0		1		
	1	1	1	1	1

Therefore, according to the positions of 1's, SOP form is $Y = \Sigma(1, 4, 5, 6, 7)$.

According to the positions of 0's (positions other than 1's), POS form is $Y = \Pi(0, 2, 3)$.

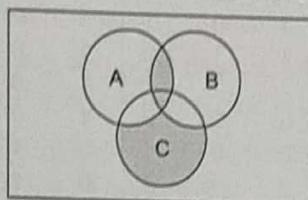Example - 2.17

The Boolean expression for the shaded area in the Venn diagram shown is



- (a) $A + \bar{B} + C$
 (c) $A\bar{B}C + \bar{A}\bar{B}C$

- (b) $AB + \bar{A}BC$
 (d) $AB + \bar{A}\bar{B}C$


Solution : (d)

∴

$$Y = AB\bar{C} + ABC + \bar{A}\bar{B}C = AB + \bar{A}\bar{B}C$$

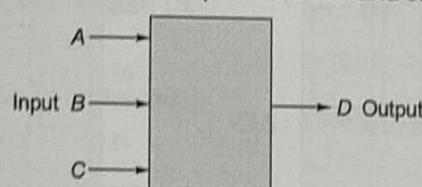Example - 2.18

For the box shown the output D is true if and only if a majority of the inputs are true.



The Boolean function for the output is

- (a) $D = A\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C$
 (b) $D = ABC + \bar{A}BC + A\bar{B}C + AB\bar{C}$
 (c) $D = \bar{A}\bar{B}\bar{C} + AB + AC + BC$
 (d) $D = \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + ABC$

Solution : (b)

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\Rightarrow \bar{A}BC$
 $\Rightarrow A\bar{B}C$
 $\Rightarrow ABC$
 $\Rightarrow ABC$



Example-2.19 Design a 4-bit combinational circuit 2's complimenter (i.e. the output generates 2's compliment of the input binary number). Show that the circuit can be constructed with EX-OR gates.

Solution:

Let the inputs are A, B, C and D and the 2's complimented outputs are W, X, Y and Z respectively.
Therefore the truth table is


Input				Output			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	0	1
1	0	0	0	1	1	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

Using K-map

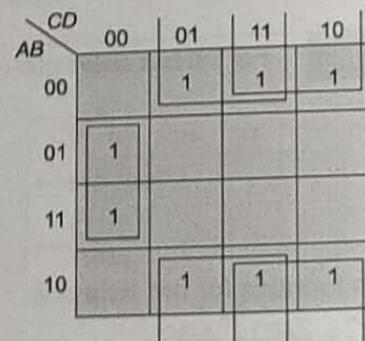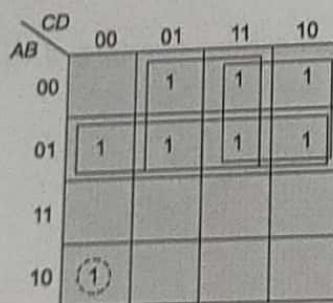

$$W = \bar{A}(B+C+D) + A\bar{B}\bar{C}\bar{D}$$


$$\Rightarrow W = A \oplus (B + C + D)$$

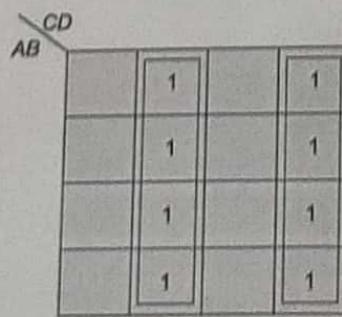

$$Y = \bar{C}\bar{D} + \bar{C}D = C \oplus D$$

$$X = \bar{B}(C+D) + B\bar{C}\bar{D}$$

$$= B \oplus (C + D)$$

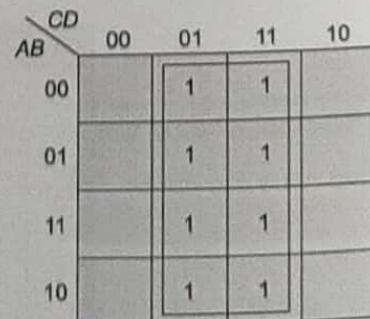

$$Z = D$$



Thus, the circuit can be constructed using Ex-OR gate as

$$\begin{aligned}W &= A \oplus (B + C + D) \\X &= B \oplus (C + D) \\Y &= C \oplus D \\Z &= D\end{aligned}$$

Summary

- With 'n' number of variables the maximum possible minterm or maxterm is equal to 2^n .
- With 'n' number of variables, the maximum possible logical expression is equal to 2^{2^n} , i.e. Boolean expression = 2^{2^n} .
- For 'n' number of variable the maximum possible self dual expression = $2^{2^{n-1}}$.
- K-map will provide minimized expressions but not necessarily unique.
- The two K-maps are said to be equal if '1's are placed in the same position on both the maps. Thus, the logical expression is also same.
- The two K-maps are said to be complemented if one K-map has 1's and another K-map has 0's on the same location.

**Student's Assignments****1**

Q.1 Explain De-Morgan's first theorem using circuits of NOR gate as well as AND gate with inverted inputs. Give the relevant table using NAND gate and OR gate with inverted inputs, explain De-Morgan's second theorem.

Q.2 Identify the number of PI and EPI for the following function as, $f(A, B, C) = \Sigma m(0, 1, 5, 7)$.

Q.3 (i) What are the main advantages of K-map over the algebraic methods in digital simplification circuitry.

(ii) Find the minimize form of the logical expression

$$Z = ABC + ABD + \bar{A}\bar{B}\bar{C} + CD + B\bar{D},$$

by using K-map technique.

Answer : (Conventional)

3. (ii) $B + CD$

- (a) $(16)^8$ (b) $(16)^{16}$
 (c) $(16)^{32}$ (d) $(16)^{64}$


Q.2 For a 3-variable function given that

$$f(A, B, C) = \prod M(0, 1, 2, 3, 4, 5, 6, 7)$$

The minimized Boolean function is

- (a) $A\bar{B}C$ (b) $(A + B + C)$
 (c) 0 (d) 1

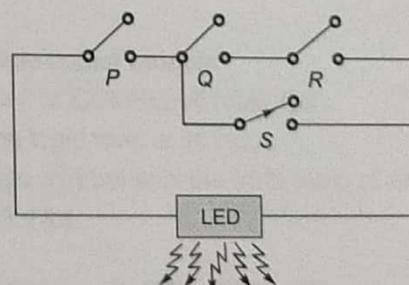Q.3 For the switching circuit shown below, taking open as '0' and closed as '1', the expression for the circuit when LED glows is,



- (a) $P + (Q + R)S$
 (b) $P(QR + S)$
 (c) $P + QR + S$
 (d) LED can not glow

**Student's Assignments****2**


Q.1 For an 8-bit microprocessor, the maximum possible number of self dual-functions equals to

Q.4 A combinational circuit has input A , B , and C and its K-map is as shown in figure. The output of the circuit is given by

		BC	
		00	01
A	00		1
	01	1	

- (a) $(\bar{A}B + A\bar{B})\bar{C}$ (b) $(AB + \bar{A}\bar{B})\bar{C}$
 (c) $\bar{A}\bar{B}\bar{C}$ (d) $A \oplus B \oplus C$

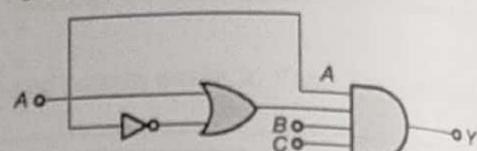Q.5 The Boolean expression for the output in the logic circuit is



- (a) $A\bar{B}C$ (b) ABC
 (c) $\bar{A}BC$ (d) $\bar{A}\bar{B}\bar{C}$

Answer Key:

1. (c) 2. (c) 3. (b) 4. (d) 5. (b)

• • •

Logic Gates and Switching Circuits

Introduction

- Logic gates are the fundamental building blocks of any digital system.
- The name logic gate is derived from the ability of such a device to make decisions, in the sense that, it produces outputs for different combinations of applied inputs.
- The inputs and outputs of logic gates can occur only in two levels as HIGH and LOW, MARK and SPACE, TRUE and FALSE, ON and OFF, or simply 1 and 0.
- The function of each logic gate will be represented by Boolean expression.
- Logic gates are classified as
 - Basic Gates : NOT, AND, OR
 - Universal Gate : NAND, NOR
 - Special purpose Gate : EX-OR, EX-NOR
- A "truth table" is a means for describing how a logic circuit's output depends on the logic levels present at circuit's input.
- The number of combinations are 2^N for " N -variable" truth table.

3.1 Basic Gates

3.1.1 The NOT Gate

- The NOT gate has a single input variable and a single output variable.
- The NOT operation is also referred to as 'INVERSION' or 'COMPLEMENTATION'.
- Thus, its output logic level is always opposite to the logic level of its input.
- Figure 3.1 (a) and (b) respectively shows the logic symbol and the truth table of an inverter. However the waveform sample is shown in Figure 3.1 (c).

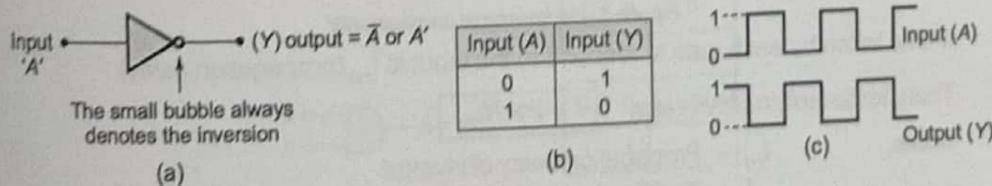


Figure-3.1 The NOT Gate (a) Logical symbol (b) Truth table (c) Sample waveform

- The symbol of NOT operation is represented by ' \neg ' (bar) or ('). Therefore, for input A the output of the NOT gate is $Y = \bar{A} = A'$.
- The switching circuit of a NOT gate is in Figure (3.2), where as the transistor circuit is shown in Figure (3.3).
- \Rightarrow When switch A is open i.e. logic '0' then, the bulb glows (shows logic '1').
- \Rightarrow When switch is closed i.e. logic '1' then, the bulb does not glow (shows logic '0').

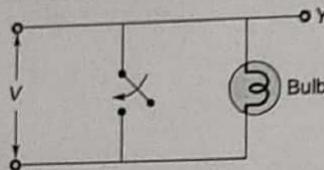


Figure-3.2: Switching circuit of NOT gate

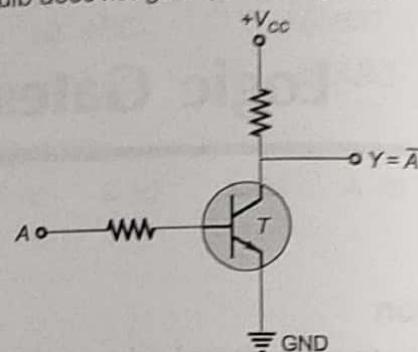


Figure-3.3 Transistor as an inverter

Similarly for transistor circuit

$$\text{when, } \begin{aligned} A = 0 ; T = \text{OFF} &\text{ and } Y = +V_{CC} (1) \\ A = 1 ; T = \text{ON} &\text{ and } Y = \text{GND} (0) \end{aligned}$$

- When even number of NOT gates/inverters are connected in feedback, it acts like a bistable multivibrator (basic memory element) shown in Figure 3.4 (a).

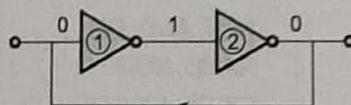


Figure-3.4 (a) Basic memory element

- Even number of NOT gates/inverters without feedback act like a buffer.

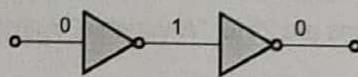


Figure-3.4 (b) Inverter as a buffer

NOTE: Buffers are used to increase the driving capacity of a gate.

- Odd number of NOT gates/inverters connected in feedback act like an astable multivibrator or, a square wave generator, or a clock pulse generator or, a free running oscillator.

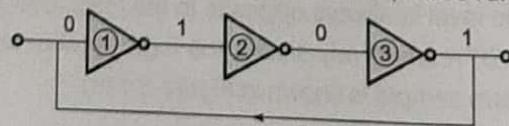


Figure-3.4 (c) Inverter as an astable MV

If time taken by each gate to respond to the input is t_{pd} (propagation delay).

Then, for astable multivibrator, $T = 2 \times N t_{pd}$

where,

t_{pd} = Propagation delay of inverter


T = Time period of a square wave generator

N = Number of inverters

and

$$\text{Frequency of oscillation} = \frac{1}{2Nt_{pd}}$$

Example-3.1 For the given ring oscillator, the propagation delay of each inverter is 100 pico sec. What is the fundamental frequency of the oscillator output?

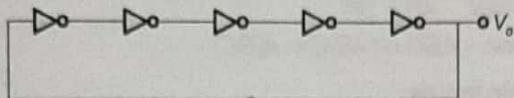**Solution:**

Here,

$$N = 5$$


$$t_{pd} = 100 \times 10^{-12} \text{ sec.}$$

$$\therefore f = \frac{1}{2Nt_{pd}} = \frac{1}{2 \times 5 \times 100 \times 10^{-12}} = 1 \text{ GHz}$$

Example-3.2 In the circuit shown below, the propagation delay of each NOT gate is 2 nsec then, the time period of generated square wave is

- (a) 6 nsec
(c) 12 nsec


- (b) 16 nsec
(d) 10 nsec

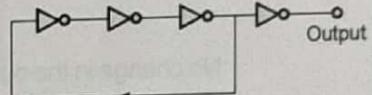**Solution : (c)**

$$N = 3 \text{ and } t_{pd} = 2 \text{ nsec}$$


$$T = 2Nt_{pd} = 2 \times 3 \times 2 \times 10^{-9} = 12 \text{ nsec}$$

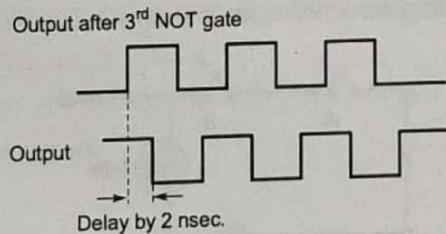* Here, the last inverter is only used to invert and delay the generated square wave by the astable multivibrator.



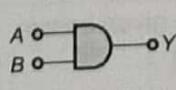3.1.2 The AND Gate

- The AND gate can have two or more inputs but only one output.
- The logic symbol and the truth table of a two input AND gate is shown in Figure 3.5 (a) and (b) respectively.




(a)

Input		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(b)

Figure-3.5 The AND Gate (a) Logic symbol and (b) Truth table

- The logical expression is $Y = AB$
- It is clear from the truth table that, if all the inputs or any of the input is LOW (logic '0') the output is also at logic '0'. However the output is 1 only when all the inputs are 1.
- AND gate follows both commutative and associative law as:
 - (i) Commutative law: $AB = BA$
 - (ii) Associative law: $ABC = (AB)C = A(BC)$
- Enable and disable inputs:
For AND operations

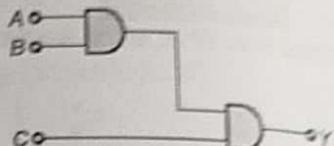

If control = 0;

A	Control	Y
0	0	0
1	0	0

No change in the output, hence logic '0' is considered as **disable** input for AND gate.

If control = 1;

A	Control	Y
0	1	0
1	1	1

Due to change in the input output also changes therefore logic '1' is **enable** input for AND gate.

- The switching circuit diagram of AND gate is shown in *Figure (3.6)*.

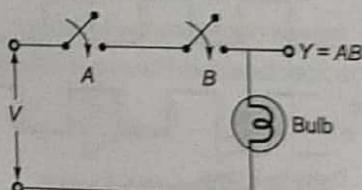


Figure-3.6 Switching circuit

The bulb will glow only when both the switches A and B are closed or at logic '1'.

- The AND operation is performed exactly like ordinary multiplication of 1's and 0's.
- In multi input AND gate, the unused input can be connected to
 - (i) Logic '1' or pull up (enable)
 - (ii) One of the used input
 - (iii) Left open for TTL logic circuit

Out of these three procedure the best way is to connect the logic '1' or pull up.


Example-3.3

Consider the logical functions given below.

$$f_1(A, B, C) = \Sigma(2, 3, 4)$$

$$f_2(A, B, C) = \pi(0, 1, 3, 6, 7)$$

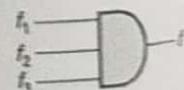If f is logic zero, then maximum number of possible minterms in function f_3 are



Solution:

$$f_1(A, B, C) = \Sigma_m(2, 3, 4)$$

$$f_2(A, B, C) = \Pi_M(0, 1, 3, 6, 7) = \Sigma_m(2, 4, 5)$$

$$f = f_1 \cdot f_2 = \Sigma_m(2, 4)$$


For function f to be zero

$$f_3 = \Pi_M(2, 4) = \Sigma_m(0, 1, 3, 5, 6, 7)$$

Maximum minterms possible are 6.

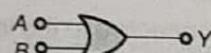3.1.3 The OR Gate

- The OR gate can have two or more inputs but only one output. The logic symbol and the truth table for OR gate is shown in Figure 3.7 (a) and (b) respectively.





(a)

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(b)

Figure-3.7 The OR Gate (a) Logic symbol and (b) Truth table

- Thus, the logical expression is
$$Y = A + B$$
- It is clear from the truth table that, if all the inputs or any of the input is high the output Y is HIGH. Whereas if all the inputs are LOW then the output Y is low.
- OR gate follows both commutative and associative laws as:
 - Commutative law: $A + B = B + A$
 - Associative law: $(A + B + C) = (A + B) + C = A + (B + C)$
- Enable and disable inputs:**
For an OR gate

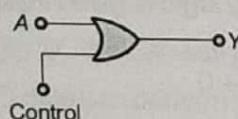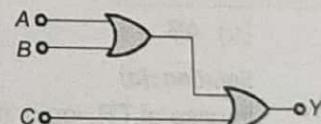

For control = 0;

A	Control	Y
0	0	0
1	0	1

The change in the input causes the change in the output hence, for OR gate logic '0' is an enable input.

For control = 1;

A	Control	Y
0	1	1
1	1	1

Due to change in the input, output remains the same therefore for OR gate logic '1' is a disable input.

- The switching circuit diagram for OR gate is shown in Figure (3.8).

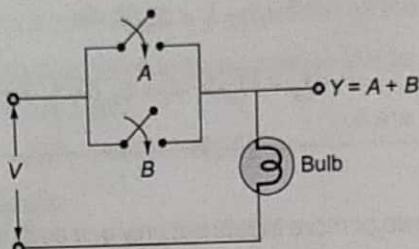



Figure-3.8 Switching circuit

Here, the bulb will glow when any of the switch (either A or B), or both the switches are closed.

- In a multi input OR gate an unused input can be connected to
 - Logic '0' (Enable) or pull-down.
 - Any of the used input.
 - Left open or floating in case of ECL logic.

Out of these procedures, the best way is to connect to the logic '0' or pull down.

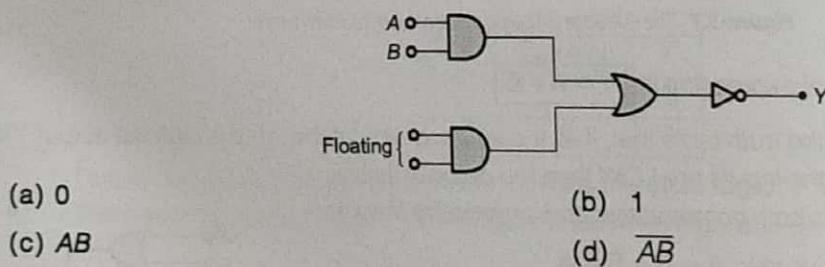Example-3.4 The circuit shown in the below figure is a TTL circuit. The output of the circuit is



(a) 0

(b) 1

(c) AB

(d) \overline{AB}

Solution : (a)

In case of TTL logic, the floating input is accepted by the logic gate as logic '1'.

Therefore, Input to the OR gate = AB and 1 = Input to the NOT gate = 1 and $Y = 0$

Note that in the above question if ECL logic is given instead of TTL logic then the floating inputs are accepted by the logic gate as '0'.

Therefore, input to the OR gate = $AB + 0$

Output of the OR gate = AB

Hence, output of the inverter $Y = \overline{AB}$.

Example-3.5 A car alarm system is to be designed considering 4 inputs, door closed (D), key in (K), seat pressure (S) and seat belt closed (B).

The alarm (A) should sound if

1. The key is in and door is not closed or
2. The door is closed, the key is in, driver in the seat and seat belt is not closed.

The system is to be designed with 2 input basic gates and NOT gates. The number of gates required are

(a) 6


(b) 7

(c) 8

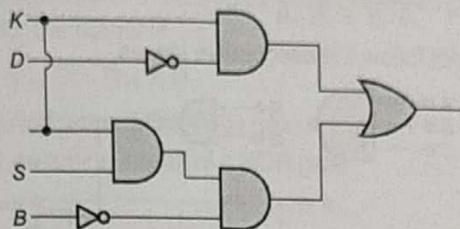(d) 9

Solution: (a)

$$A = K\bar{D} + KDS\bar{B} = K\bar{D} + KS\bar{B}$$



3.2 Universal Gates

The NAND gate and NOR gate are called Universal gates because they can perform all the three basic functions of AND, OR and NOT gates.

3.2.1 The NAND Gate

- The NAND gate is a AND gate followed by NOT gate. Thus, we can say, it is a AND-NOT operation. It may have two or more inputs but only one output. The logical symbols of a NAND gate are shown in Figure 3.9 (a), (b) and (c) and the truth table is shown in Figure 3.9 (d).

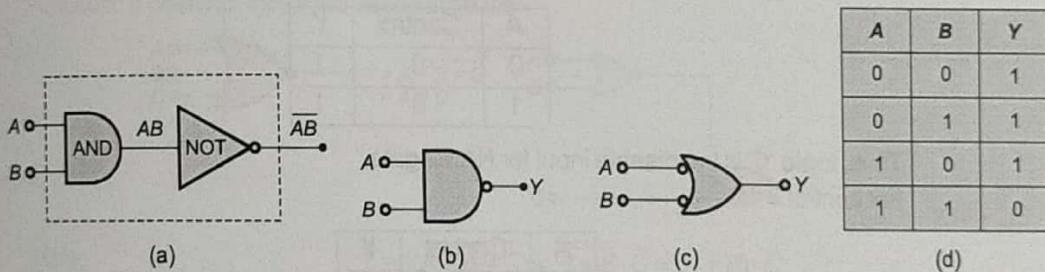


Figure-3.9 The NAND Gate (a), (b), (c) and (d)

- Thus, the logical expression for the output is $Y = \overline{A \cdot B} = \bar{A} + \bar{B}$. It is clear from the truth table of two input NAND gate, that the output is 1 when either A or B or when both the inputs are at logic '0'. We can say that, if $\bar{A} = 1 = \bar{B}$ are both \bar{A} and \bar{B} are '1', the output is 1. Therefore, the NAND gate can perform the OR function by inverting the inputs and then ORing it (Figure 3.9 (c)).
- In NAND gate output is exact inverse of the AND gate for all possible input combinations.
- The OR gate with inverted inputs is called bubbled OR gate or negative OR gate. The NAND gate is also called active low OR gate.
- The switching circuit diagram for a NAND gate is shown in Figure (3.10).

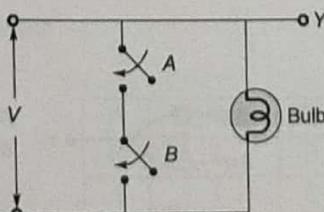



Figure-3.10 Switching Circuit

The bulb will glow when any of the switches A or B will open (logic 0).

- NAND gate follows the commutative law as

$$\overline{A \cdot B} = \overline{B \cdot A}$$

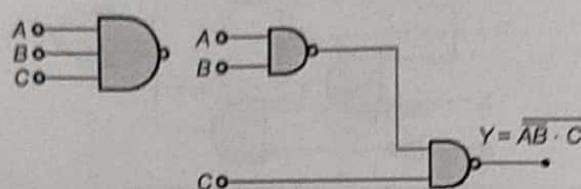
- NAND gate will not follow the associative law as



$$Y = \overline{\overline{AB} \cdot C} = \overline{AB} + \overline{C} = A + B + \overline{C}$$

- Enable and disable inputs:

For a NAND Gate

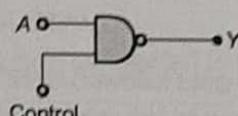

For control = 0;

A	Control	Y
0	0	1
1	0	1

Thus, logic '0' is the **disable** input for NAND gate

For control = 1;




A	Control	Y
0	1	1
1	1	0

Thus, logic '1' is the **enable** input for NAND gate.

NOTE: Unused input in any multi input NAND gate is always connected to the enable logic or Pull-up.

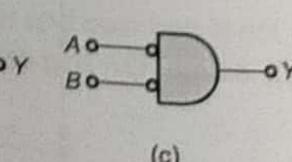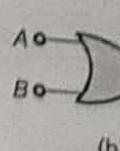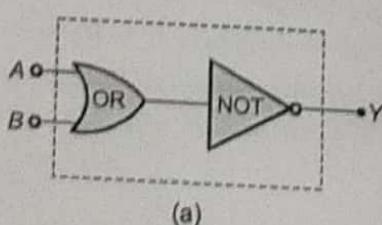3.2.2 The NOR Gate

- A NOR gate is a combination of OR gate and NOT gate. So we can say it is a OR-NOT operation. It may have two or more input and an output. The logical symbols of NOR gate is shown in Figure 3.11 (a), (b) and (c), whereas, the truth table is listed in Figure 3.11 (d).



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Figure 3.11 The NOR Gate (a), (b), (c) and (d)

- It is clear from the truth table that the output is '1' only if all the inputs are at logic '0'. It can also say that if the inputs $\bar{A} = \bar{B} = 1$, then the output Y is 1. Thus, the NOR gate is equivalent to the AND gate with inverted inputs and it can be realized by a bubbled AND gate as shown in Figure 3.11 (c). The logical expression for the output is

$$Y = \overline{A+B} = \bar{A}\bar{B}$$

- The NOR gate is also called active LOW AND gate.
- Figure (3.12) shows the switching circuit of a NOR gate.


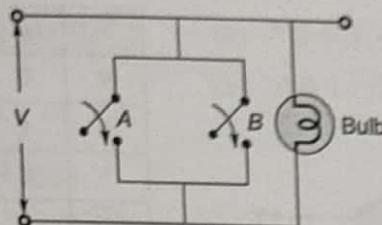


Figure-3.12 Switching circuit

- When any of the switches either A or B is closed, the bulb will not glow.
- NOR gate follows the commutative law as

$$\overline{A+B} = \overline{B+A}$$

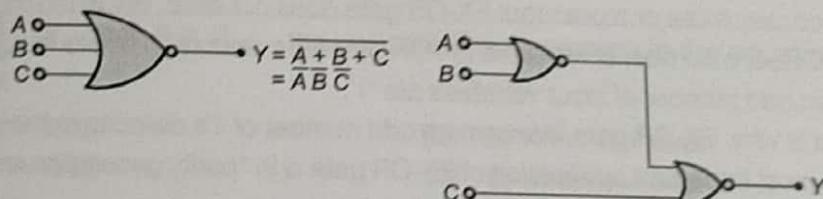
However, it does not follow the associative law.



Here,

$$Y = \overline{(\overline{A+B} + C)} = \overline{\overline{A+B}} \cdot \overline{C} = (A+B) \cdot \overline{C}$$

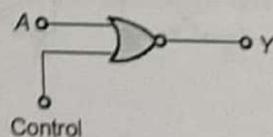- Enable and disable inputs:
For a NOR Gate



If control = 0;

A	Control	Y
0	0	1
1	0	0

Thus, logic '0' is enable input.
If control = 1;

A	Control	Y
0	1	0
1	1	0

Thus, logic '1' is disable input.

NOTE: Unused input in any multi input NOR gate is always connected to the enable logic or Pull-Down.

3.3 Special Purpose Gate

3.3.1 The Exclusive-OR Gate (EX-OR)

- A EX-OR gate is a two input single output logic gate, whose output is assumed to be HIGH only when one and only one of its inputs is HIGH. The logic symbol and the truth table for a two input EX-OR gate is shown in Figure 3.13 (a) and (b) respectively.

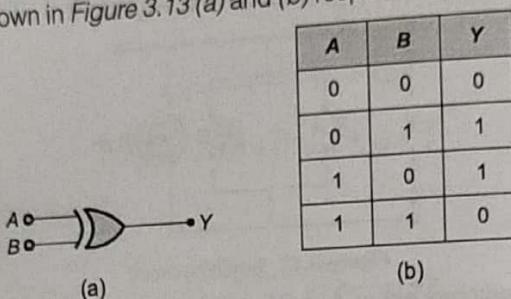


Figure-3.13: The EX-OR Gate (a) Logic symbol and (b) Truth table

- If input variables are represented by A and B then the logical expression for output is

$$Y = A\bar{B} + \bar{A}B = A \oplus B$$

- Practically three or more input EX-OR gate does not exist. But when more than two variables are EX-ORed, a number of two input EX-OR gates are cascaded where the output is assumed to be '1' when odd number of input variables are '1'. That is why, EX-OR gate is known as odd number of 1's detector in the input.
- The most important application of EX-OR gate is in "parity generation and detection".
- It is also known as "stair case switch".
- The switching circuit of EX-OR gate is shown in Figure (3.14).

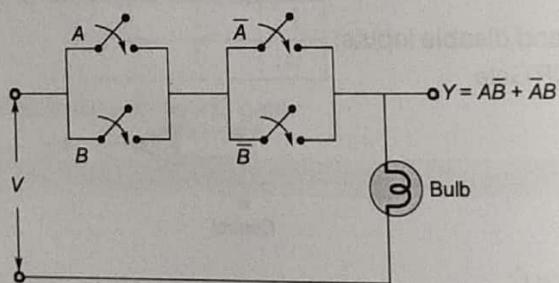



Figure-3.14 Switching circuit

$$Y = (A+B)(\bar{A}+\bar{B}) = A\bar{B} + \bar{A}B \text{ or } A \oplus B$$

- The EX-OR gate follows both commutative and associative law.
- Enable and disable inputs:

For an EX-OR Gate

For control = 0;

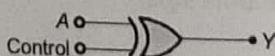

A	Control	Y
0	0	0
1	0	1

Thus, the EX-OR gate acts as a buffer for controlled input of logic '0'.
For control = 1;

A	Control	Y
0	1	1
1	1	0

Thus, the EX-OR gate acts as an inverter for control input of logic '1'.

Properties of EX-OR gate:

- (i) $A \oplus A = 0$
- (ii) $A \oplus 0 = A$
- (iii) $A \oplus \bar{A} = 1$
- (iv) $A \oplus 1 = \bar{A}$
- (v) $A \oplus A \oplus A = A$

Internal diagram of EX-OR gate.

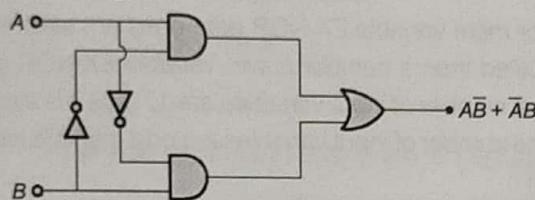


Figure-3.15

Example-3.6 $Y = B \oplus B \oplus B \dots$ the variable B is appearing in the equation n times, then the value of Y is

- (a) Zero when n = even
- (b) B, when n = even
- (c) Zero when n = odd
- (d) B, when n = odd

Solution: (a) & (d)

For even number $Y = 0$ as $B \oplus B = 0$

For odd number $Y = B$ as $B \oplus B \oplus B = B$

Example-3.7 Show that the dual of the exclusive OR is equal to its complement.

Solution:

Let A and B are the two inputs

Then,

$$A \oplus B = A\bar{B} + \bar{A}B$$

$$\text{Dual of } (A \oplus B) = (A + \bar{B}) \cdot (\bar{A} + B) = AB + \bar{A}\bar{B}$$

$$\begin{aligned} \text{Complement of } (A \oplus B) &= (A\bar{B} + \bar{A}B)' = (\bar{A} + B)(A + \bar{B}) \\ &= AB + \bar{A}\bar{B} = \text{Dual of } (A \oplus B) \end{aligned}$$

3.3.2 The Exclusive NOR (EX-NOR) Gate

- An EX-NOR gate is an EX-OR gate followed by NOT gate. The EX-NOR gate is a two input and one output logic circuit in which the output is '1' only when both the inputs are same. Thus, it is also called "gate of equivalence" or "coincidence logic".
- The logic symbol and the truth table of a two input EX-NOR gate are shown in Figure 3.16 (a) and (b) respectively.

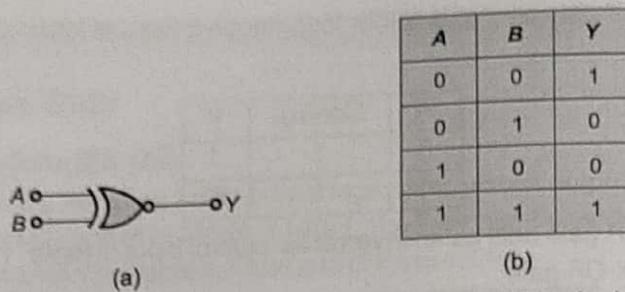


Figure-3.16 The EX-NOR Gate (a) Logical symbol and (b) Truth table

Thus, for input variables A and B the logical expression for the output of an EX-NOR gate is given by

$$Y = AB + \bar{A}\bar{B} = A \odot B$$

- Practically, three or more variable EX-NOR gate does not exist. However if number of variables have to be EX-NORED then a number of two variable EX-NOR gates will be used in which the output is '1' for even number of input variables are 1. Thus it is also known as "even number of 1's detector". When the number of input variables are odd then it is also known as "odd number of 1's detector".
- Switching circuit for EX-NOR gate is shown in Figure (3.17).


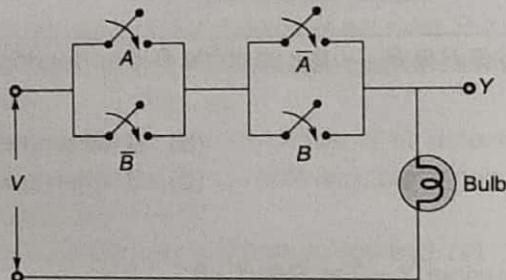


Figure-3.17 Switching circuit

- EX-NOR gate follows both commutative and associative law.
- Enable and disable inputs:**

For an EX-NOR Gate

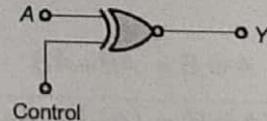

For control = 0;

A	Control	Y
0	0	1
1	0	0

Thus, it acts as an inverter for logic '0'.

For control = 1;

A	Control	Y
0	1	0
1	1	1

Thus, it acts like a buffer for logic '1'.

Properties of EX-NOR gate:

$$(i) A \odot A = 1$$

$$(ii) A \odot 1 = A$$

$$(iii) A \odot 0 = \bar{A}$$

$$(iv) A \odot \bar{A} = 0$$

$$(vi) A \odot A \odot A \odot A = 1$$

Thus for odd number of same input the output is same as input and for the even number of same input the output is equals to logic '1'.

Note: $(A \oplus B) \odot C = A \odot (B \odot C)$

Example-3.8

Find (i) $\bar{A} \oplus B = ?$ (ii) $A \oplus B \oplus AB = ?$

Solution:

(i)

$$\bar{A} \oplus B = \bar{A}\bar{B} + \bar{A}B$$

$$\bar{A}\bar{B} + AB = A \odot B$$

(ii)

$$\begin{aligned} A \oplus B \oplus AB &= (\bar{A}\bar{B} + \bar{A}B) \oplus AB = (\bar{A}\bar{B} + \bar{A}B)'AB + (\bar{A}\bar{B} + \bar{A}B)\bar{A}\bar{B} \\ &= (A + \bar{B})(\bar{A} + B)AB + (\bar{A}\bar{B} + \bar{A}B)(\bar{A} + \bar{B}) \\ &= AB + \bar{A}B + \bar{B}A = A + B \end{aligned}$$

Example-3.9

7EH and 5FH are EX-ORed. The output is multiplied by 10H. The result is

(a) 0210 H

(b) 7E5F H

(c) 5F7E H

(d) 2100 H


Solution: (a)

$$\begin{array}{rcl} 7EH \rightarrow 0111 \ 1110 & & 21H \\ 5FH \rightarrow 0101 \ 1111 & & \\ \text{Ex-ORed} \quad \underline{\underline{0010 \ 0001}} & = 21H & \times 10H \\ & & \text{Result} \rightarrow \underline{\underline{0210H}} \end{array}$$

NOTE: For two inputs EX-OR gate if one of the input is in complemented form, then it gives EX-NORed output and vice-versa.

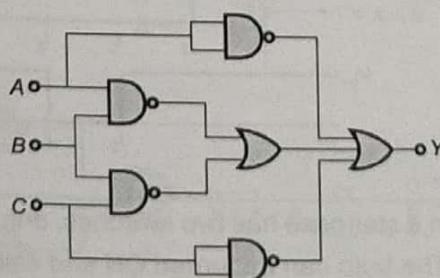Example-3.10

For the logic circuit shown in Figure, the output is equal to




(a) \overline{ABC}

(b) $\bar{A} + \bar{B} + \bar{C}$



(c) $\overline{AB} + \overline{BC} + \overline{A} + \overline{C}$

(d) $\overline{AB} + \overline{BC}$

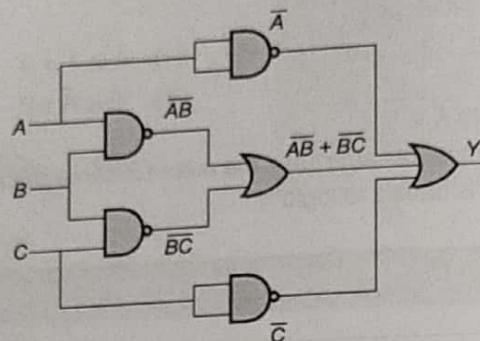Solution:(b)

$$Y = \bar{A} + \bar{AB} + \bar{BC} + \bar{C} = \bar{A} + (\bar{A} + \bar{B}) + (\bar{B} + \bar{C}) + \bar{C} = \bar{A} + \bar{B} + \bar{C}$$

Example-3.11 The gates G_1 and G_2 in the figure have propagation delays of 10 nsec and 20 nsec respectively. If the input V_i makes an abrupt change from logic 0 to 1 at time $t = t_0$, then the output waveform V_o is

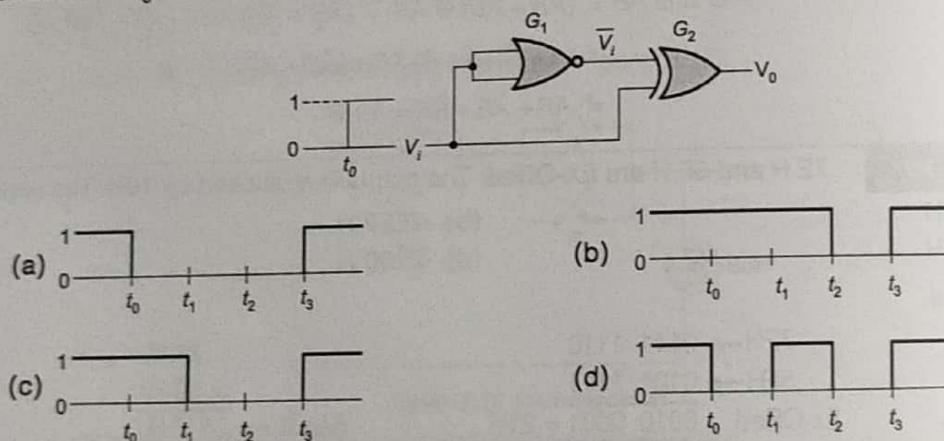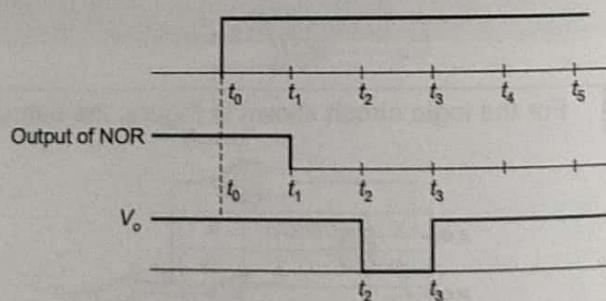**Solution:(b)**

Example-3.12 A bulb in a staircase has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and also can be turned OFF by any one of the switches irrespective of the state of the other switch. The logic of switching of the bulb resembles

- (a) an AND gate
- (b) an OR gate
- (c) an XOR gate
- (d) a NAND gate

Solution: (c)

Truth table of XOR gate


So, from the XOR gate truth table it is clear that the bulb can be turned ON and also can be turned OFF by any one of the switches irrespective of the state of the other switch.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


3.4 Realization of Logic Gates Using Universal Gates

3.4.1 Realization of basic gates using NAND and NOR Gate


(i) NOT Gate Realization

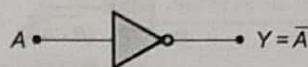


Using NAND gate:

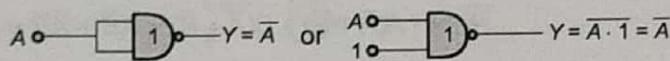


Using NOR gate:

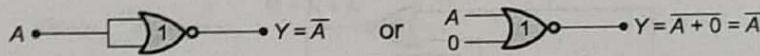


(ii) AND Gate Realization

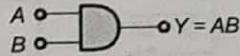


Using NAND Gate:

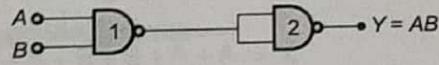


Using NOR Gate:

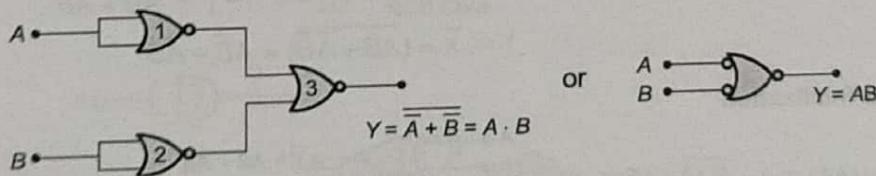


(iii) OR Gate Realization

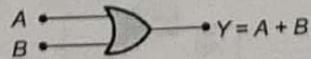

Using NAND Gate:

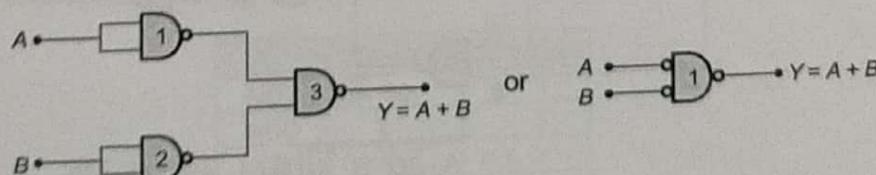

Using NOR gate:

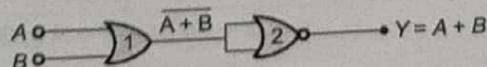


3.4.2 Realization of special purpose gate using NAND and NOR gate

(i) EX-OR Gate Realization




Using NAND Gate:

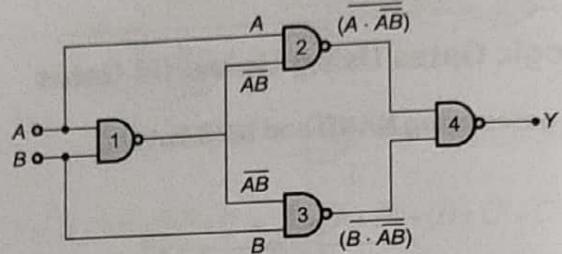

$$\begin{aligned} Y &= \overline{(\overline{A} \cdot \overline{AB})} \cdot (\overline{B} \cdot \overline{AB}) = A \cdot \overline{AB} + B \cdot \overline{AB} \\ &= A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B}) = A\overline{B} + \overline{A}B = A \oplus B \end{aligned}$$

Using NOR Gate:

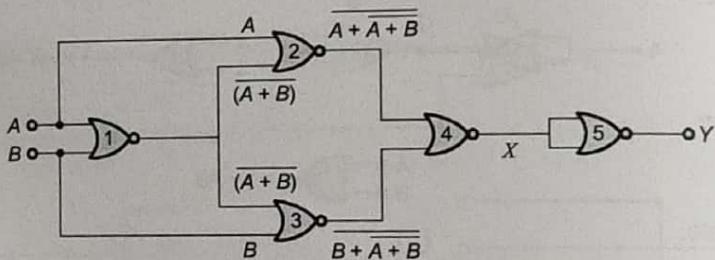


Here,

$$\begin{aligned} X &= \overline{A + A + B + B + A + B} = [A + (\overline{A} + B)] \cdot [B + (\overline{A} + B)] \\ &= [A + (\overline{A}\overline{B})] [B + \overline{A}\overline{B}] = AB + \overline{A}\overline{B} \end{aligned}$$


Now,

$$Y = \overline{X} = \overline{(AB + \overline{A}\overline{B})} = A\overline{B} + \overline{A}B$$

(ii) EX-NOR Gate Realization

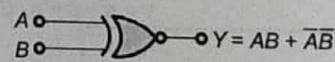

Using NAND Gate:

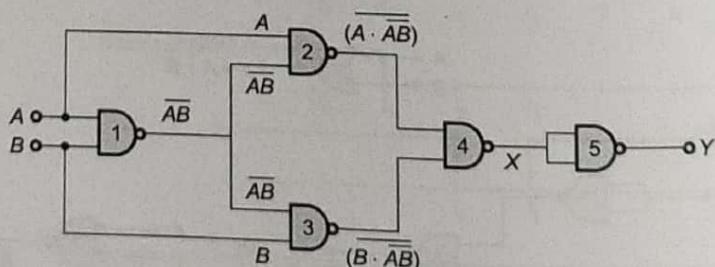


Here,

$$\begin{aligned} X &= \overline{A \cdot \overline{AB} \cdot B \cdot \overline{AB}} = (A \cdot \overline{AB} + B \cdot \overline{AB}) \\ &= A \cdot (\overline{A} + \overline{B}) + B(\overline{A} + \overline{B}) = A\overline{B} + \overline{A}B \end{aligned}$$


Now,

$$Y = \overline{X} = \overline{A\overline{B} + \overline{A}B} = A \odot B$$


Using NOR Gate:

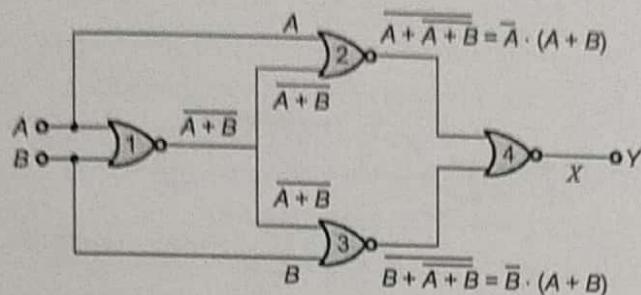

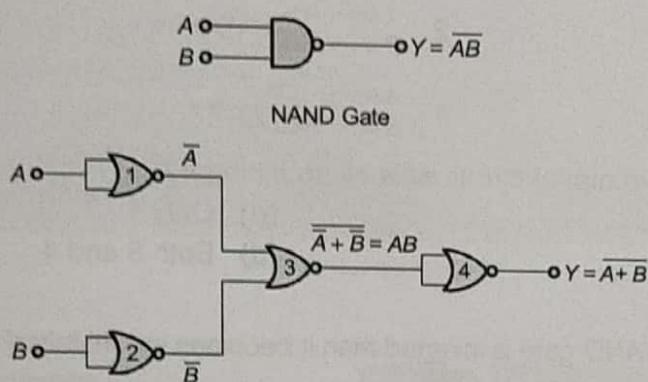3.4.3 Realization of NAND gate using NOR gate



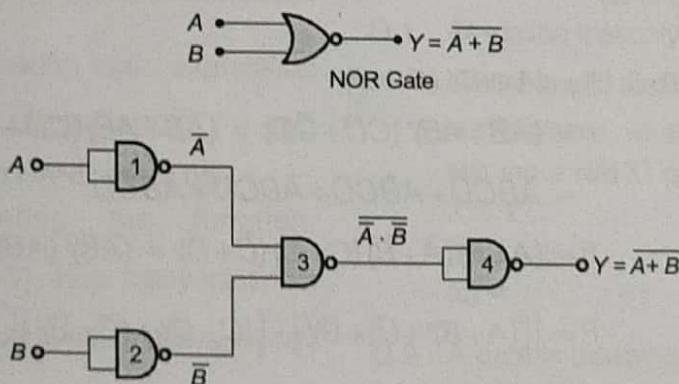3.4.4 Realization of NOR Gate using NAND Gate




3.4.5 Shortcut for Realization of Logic Gates using NAND and NOR

	NAND	$\xrightarrow{4}$	NOR
NOT	1		1
AND	2		3
OR	3		2
EX-OR	4		5
EX-NOR	5		4





Example-3.13 How many NOR gates are required to implement the Boolean function $(A + B) \cdot (C + D)$?

Solution: (3)

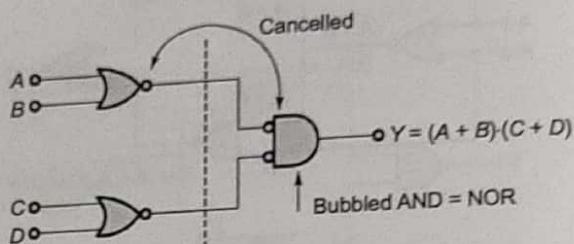

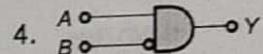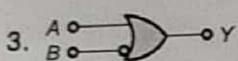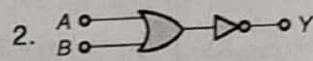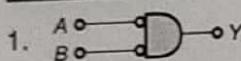Example-3.14

Consider the following digital logic circuits.



Which of these above digital circuit acts as an Inhibitor?

- (a) Only 3
(c) 1 and 4

- (b) Only 4
(d) Both 3 and 4

Solution: (b)

If one of the inputs to AND-gate is inverted then it becomes an "Inhibitor".

Example-3.15 Draw a logic diagram using only two-input NOR gate to implement $F(A, B, C, D) = (A \odot B)' (C \oplus D)$

Solution:

$$F(A, B, C, D) = (A \odot B)' (C \oplus D)$$

$$= (\bar{A}\bar{B} + AB)' (C\bar{D} + \bar{C}D) = (\bar{A}B + A\bar{B})(C\bar{D} + \bar{C}D)$$


$$= \bar{A}BC\bar{D} + A\bar{B}C\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D$$

or,

$$F = (A+B)(\bar{A}+\bar{B})(C+D)(\bar{C}+\bar{D}) = (\bar{A}\bar{B})' (AB)' (\bar{C}\bar{D})' (CD)'$$

or,
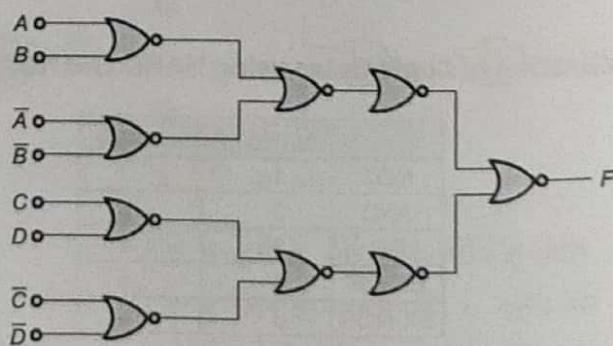
$$F = \left\{ [(A+B)' + (\bar{A}+\bar{B})'] + [(C+D)' + (\bar{C}+\bar{D})'] \right\}'$$



Summary



- Universal gates do not follow associative law.
- EX-OR gate is also called, controlled inverter (control = 0).
- EX-NOR gate is also called, controlled inverter (control = 1).
- For SOP implementation AND-OR logic is used.
- For POS implementation OR-AND logic is used.
- The AND-OR logic is equivalent to NAND-NAND logic.
- The OR-AND logic is equivalent to NOR-NOR logic.
- NAND gate is preferable than NOR gate, because it consumes less power.
- In EX-OR gate if the number of variables are ' n ', then the total number of minterms in Boolean expression is $n^2/2$.
- AND gate is known as detector logic.
- Degenerated form: two level logic circuit is represented by a single gate:
 - (i) AND-AND \rightarrow AND
 - (ii) OR-OR \rightarrow OR
 - (iii) AND-NAND \rightarrow NAND
 - (iv) OR-NOR \rightarrow NOR
 - (v) NOR-NAND \rightarrow OR
 - (vi) NAND-NOR \rightarrow AND



Student's Assignments

1

Q.1 (i) Simplify the following logic expression

$$F = A\bar{B} + A\bar{B}\bar{C} + ABCD + A\bar{B}C\bar{D}$$

and realize it by using NAND gates only.

(ii) For implementing the function,

$$F = (\bar{X} + \bar{Y})(Z + W)$$

How many minimum number of two input NAND gates required?

Q.2 Realise the logical expressions:

(i) $Y = \overline{AB} + A + (\overline{B} + \overline{C})$ using NAND-gates only.

(ii) $Y = (A + C)(A + \bar{D})(A + B + \bar{C})$ using NOR-gates only.

Answer: (Conventional)

1. (i) A (ii) 4



Student's Assignments

2


Q.1 Assuming that only the X and Y logic inputs are available and their complements \bar{X} and \bar{Y} are not available, what is the minimum number of two input NAND gates required to implement $X \oplus Y$?

- (a) 2 (b) 3
(c) 4 (d) 5

Q.2 A gate is disabled when its disable input is at logic 0. The gate is

- (a) OR (b) AND
(c) NOR (d) EX-OR

Q.3 The circuit shown in the figure is

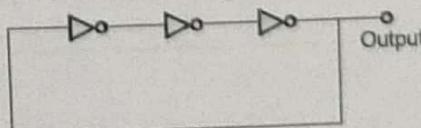

- (a) an oscillating circuit and its output is a square wave

- (b) one whose output remains stable in '1' state
 (c) one whose output remains stable in '0' state
 (d) having a single pulse of 3 times of propagation delay

Q.4 For the figure shown below, the input is considered as signed number. The decimal equivalent of output is

$$\text{Input } \begin{matrix} X_1 = 10101010 \\ X_2 = 11111111 \end{matrix} \rightarrow \text{EX-OR} \rightarrow \text{Gray Code} \xrightarrow{\text{Output decimal}}$$

- (a) +255 (b) +127
 (c) +143 (d) +31

Q.5 Consider a 4-input NAND gate, how many number of input conditions are possible, that will produce output "HIGH".


- (a) 0 (b) 1
 (c) 2 (d) 15

Q.6 If $A \neq B$, then the value of Boolean expression,

$$\overline{(A+B)} + \overline{(A+B)} + \overline{(AB)} \overline{(AB)}$$

- (a) 0 (b) 1
 (c) $A + B$ (d) AB

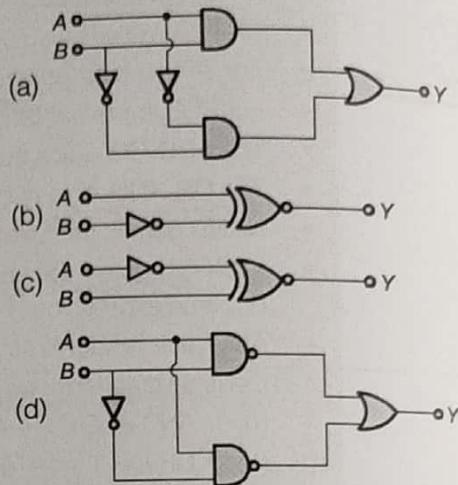Q.7 Which one of the following digital circuits does not represent the 'Stair-case switch'?



Q.8 After the simplification of a 3-variable Boolean function,

$$f(A, B, C) = (A \oplus B \oplus AB) (A \oplus C \oplus AC)$$

we require,

- (a) 1-AND and 1-OR gate
 (b) 1-AND and 2-OR gate
 (c) 2-AND and 1-OR gate
 (d) Only 1-AND gate

Answer Key:

1. (c) 2. (b) 3. (a) 4. (b) 5. (d)
 6. (a) 7. (d) 8. (a)



Combinational Logic Circuits

Introduction

A combinational circuit consists of an interconnection of logic gates, whose outputs at any instant of time are determined from present combination of inputs only. A block diagram of a combinational circuit is shown in Figure 4.1. The ' n ' input binary variables come from external sources; the ' m ' output variables are produced by the internal combinational logic circuit and go to an external destination. Each input and output variables exist physically as an analog signal whose values are interpreted to be a binary signal that represents logic '1' and logic '0'.

For ' n ' input variables, there are 2^n possible combinations of binary inputs. For each possible input combination, there is only one possible output combination. Therefore, a combinational circuit can be described by ' m ' boolean functions. One for each output variable. Each output function is expressed in terms of n input variables. A combinational circuit can also be specified by a truth table that lists the output for each combination of input variables.

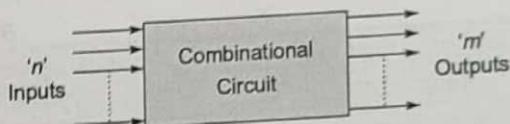


Figure-4.1 Basic diagram of combinational circuit

4.1 Design Procedure for Combinational Circuit

The design of combinational circuits starts from the specification of design objective and ends in a set of Boolean functions from which a logic circuit diagram can be easily obtained. The procedure involves the following steps:

- (i) From the specification of given circuit; determine the number of input and output variables.
- (ii) Assign symbols to each variable.
- (iii) Derive the truth table which defines the required relationship between input and output variables.
- (iv) Obtain the simplified Boolean function for each output in Sum of Product (SOP) or Product of Sum (POS).
- (v) Implement the logic circuit.

Example-4.1 Consider the following:

Any combinational circuit can be built using

1. NAND gates
3. Ex-OR gates
2. NOR gates
4. Multiplexers

Which of these are correct?

- (a) 1, 2 and 3
- (b) 1, 3 and 4
- (c) 2, 3 and 4
- (d) 1, 2 and 4

Solution: (d)

NAND & NOR are universal gates, so along with multiplexers they can be used to implement any combinational circuit.

4.2 Arithmetic Circuits

4.2.1 Adders

The Half-Adder

- The half adder is an arithmetic circuit used to perform the addition of two single bits.
- The two input variables to the half adder designate the augend and addend bits and the output variables produce the sum and carry. The block diagram of a half adder is shown in Figure 4.2. The truth table for half adder is listed in Table 4.1.

Let A and B are the two input variables and sum (S) and carry (C) are the two output variables then,

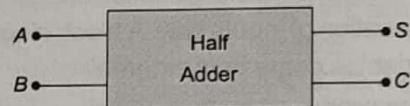


Figure-4.2 Block diagram of Half-adder

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

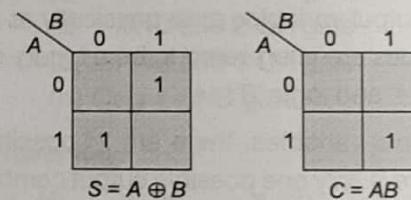


Table-4.1 Truth table of a Half-adder

The simplified Boolean functions for the two outputs can be obtained directly from the truth table. The logical expressions for sum and CARRY are:

$$S = \bar{A}\bar{B} + A\bar{B} = A \oplus B \quad \text{and} \quad C = AB$$

- **Implementation of half adder circuit:** From the given expression, a half adder can be realized by using one Ex-OR gate and an AND gate as shown in Figure 4.3 (a).

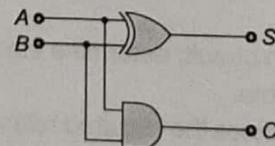


Figure-4.3 (a) Logic diagram of half-adder

- A half-adder can also be realized in universal logic by using either only NAND gates or only NOR gates as shown in Figure 4.3 (b) and (c) respectively.
NAND logic:

$$\begin{aligned} S &= \bar{A}\bar{B} + A\bar{B} = \bar{A}B + A\bar{B} + A\bar{B} + B\bar{B} \\ &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) = (A + B) + B \cdot \bar{A}B = \overline{A \cdot \overline{AB} \cdot B \cdot \overline{AB}} \\ C &= AB = \overline{\overline{AB}} \end{aligned}$$

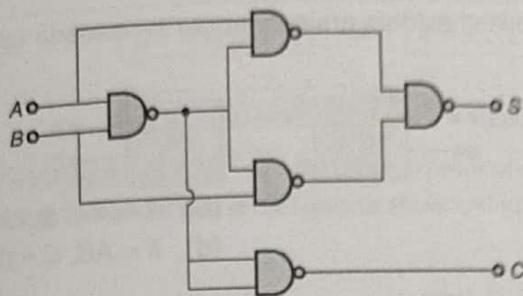


Figure 4.3 (b) NAND realization of a half-adder

NOR logic:

$$\begin{aligned}
 S &= \bar{A}\bar{B} + A\bar{B} = A\bar{B} + A\bar{A} + \bar{A}\bar{B} + B\bar{B} \\
 &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) \\
 &= (A + B)(\bar{A} + \bar{B}) \\
 &= \overline{A + B + \bar{A} + \bar{B}} \\
 C &= AB = \overline{\bar{A} + \bar{B}}
 \end{aligned}$$


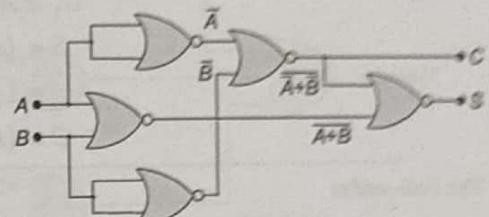


Figure 4.3 (c) NOR realization of a half-adder

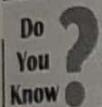

The Half-adder can also be realized using universal logic, i.e., either only NAND gates or only NOR gates. The total number of NAND/NOR gates required to implement a half-adder is equals to "5".

- Implementation of half-adder circuit by minimum number of logic gates, if we have all gates except EX-OR and EX-NOR is "3".

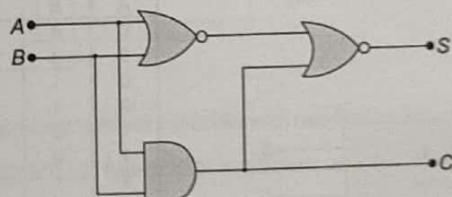


Figure 4.3 (d)

Example-4.2 The half-adder circuit in the given Figure has inputs $AB = 11$

The logic level of P and Q outputs will be


- $P = 0$ and $Q = 0$
- $P = 0$ and $Q = 1$
- $P = 1$ and $Q = 0$
- $P = 1$ and $Q = 1$

Solution: (b)


$$A = 1, B = 1$$

$$P = A \oplus B = A\bar{B} + \bar{A}B = 0$$

$$Q = AB = 1$$

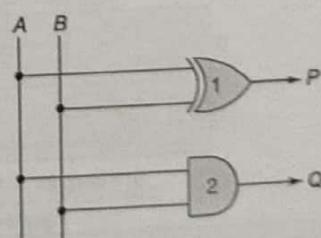

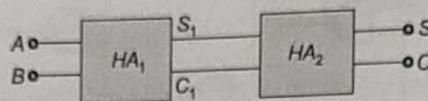Example-4.3 Two Half Adders are connected in cascade as shown in figure below. The output "S" and "C" are



- (a) $S = A \oplus B, C = AB$
(c) $S = A + B, C = 0$

- (b) $S = A \odot B, C = 0$
(d) $S = AB, C = 0$

Solution: (c)

$$S_1 = A \oplus B$$

$$C_1 = AB$$

$$\begin{aligned} S &= (A \oplus B) \oplus AB = (A \oplus B) \cdot \overline{AB} + (\overline{A} \oplus B) \cdot AB \\ &= (A\bar{B} + \bar{A}\bar{B})(\bar{A} + \bar{B}) + (AB + \bar{A}\bar{B})(AB) = A\bar{B} + \bar{A}\bar{B} + AB = A + B \\ C &= (A \oplus B) \cdot AB = (A\bar{B} + \bar{A}\bar{B}) \cdot AB = 0 \end{aligned}$$

The Full-adder

- A full-adder is a combinational circuit that performs the arithmetic sum of three input bits. It consists of three input variables designated by augend, addend and the carry bit. The two output variables produce the SUM and CARRY.
- The block diagram of a full adder is shown in Figure 4.4 and the truth Table for full-adder is listed in Table 4.2.

Let the two input variables are denoted by A and B , represent the two significant bits to be added. The third input C represents the carry from the previous lower significant position. The two outputs are sum (S) and CARRY (C_{out}).

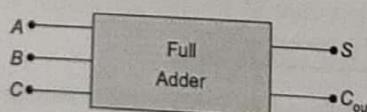


Figure-4.4 Block diagram of a full-adder

INPUT			OUTPUT	
A	B	C	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Table-4.2 Truth Table for full-adder

BC	00	01	11	10
A	0	1		1
0	1		1	
1		1		

(i) K-map for SUM

BC	00	01	11	10
A	0		1	
0		1		1
1		1	1	1

(ii) K-map for CARRY

Figure-4.5 K-maps for full-adder

- From the truth Table and the maps for the outputs of the full-adder as shown in Table 4.2 and Figure 4.5 respectively, the logical expressions for sum and CARRY are:

$$\begin{aligned} S &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC \\ C_{out} &= AB + BC + CA \end{aligned}$$

Therefore,

$$S = A \oplus B \oplus C \quad \text{or} \quad S = \Sigma_m(1, 2, 4, 7)$$

and

$$C_{out} = AB + C(A \oplus B) \quad \text{or} \quad C_{out} = \Sigma_m(3, 5, 6, 7)$$

- Implementation of full-adder circuit: From the given expression a full adder circuit can be realized in SOP form or with two half adder and an OR gate as shown in Figure 4.6 (a) and 4.6 (b) respectively.

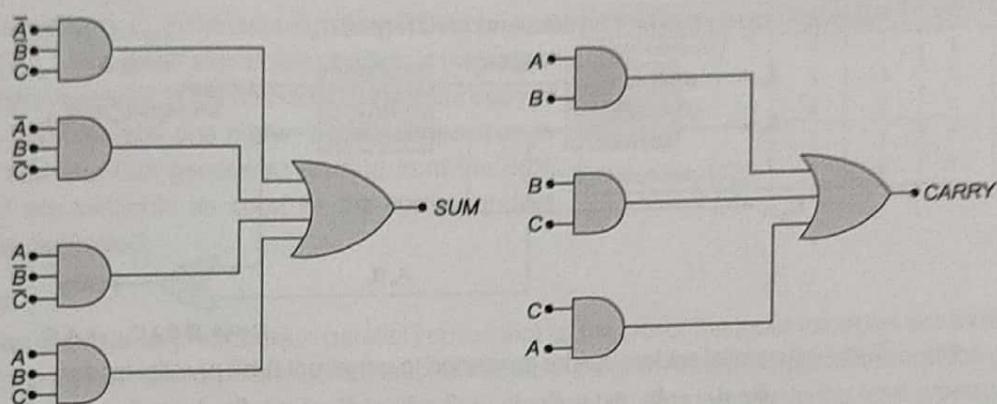


Figure-4.6 (a) Logic diagram of full-adder in SOP form

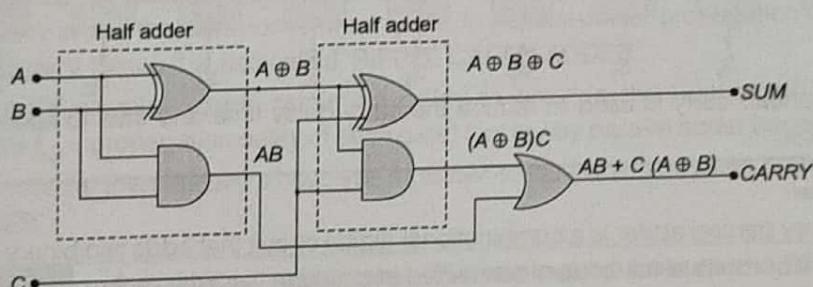


Figure-4.6 (b) Implementation of full-adder with two half adders and OR gate

- The ANSI/IEEE logic diagram for full-adder is shown as.


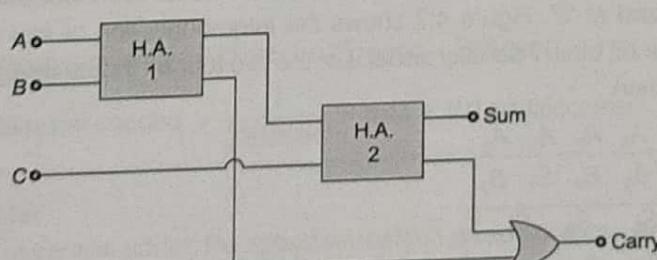


Figure-4.6 (c) IEEE/ANSI logic diagram for full-adder

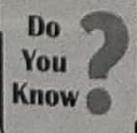


The full-adder can also be realized using universal logic, i.e., either only NAND gates or only NOR gates. The total number of NAND/NOR gates required to implement a full-adder is equals to "9".

Example 4.4 Which one of the following statements is not correct?


- (a) A full adder can be constructed using two half-adders and an OR gate.
- (b) Two four bit parallel adders can be cascaded to construct 8-bit parallel adder.
- (c) Ripple carry adder has addition time independent of the number of bits.
- (d) Carry look ahead is used to speed up the parallel addition.

Solution: (c)

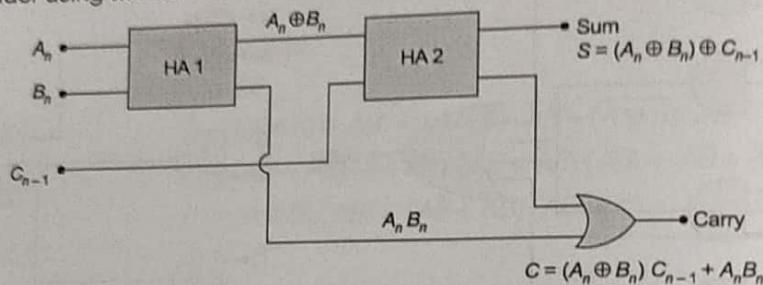- (i) Full adder using two half adders and an OR gate:



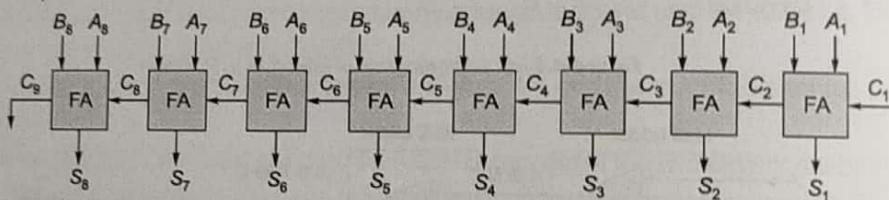- (ii) Two 4-bit parallel adders can be cascaded to construct 8-bit parallel adder.



- (iii) Look-ahead carry is used to reduce the carry delay time and thus to speed up the parallel addition.

Binary Parallel Adder

- A binary parallel adder is a combinational digital circuit that adds two binary numbers in parallel form. It consists of full-adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder.
- For addition of n -bit numbers a chain of n full adders is required or a chain of one half adder and $(n - 1)$ full adders is required. However in former case, the input carry to the least significant position is fixed at '0'. Figure 4.7 shows the interconnection of four full-adder (FA) circuits to provide a four bit binary parallel adder. Let the two four bit inputs designated as A (Augend) and B (Addend) then,

$$\begin{array}{r}
 A_3 \ A_2 \ A_1 \ A_0 \\
 + B_3 \ B_2 \ B_1 \ B_0 \\
 \hline
 \text{carry} \leftarrow C_4 \quad S_3 \quad S_2 \quad S_1 \quad S_0
 \end{array}$$

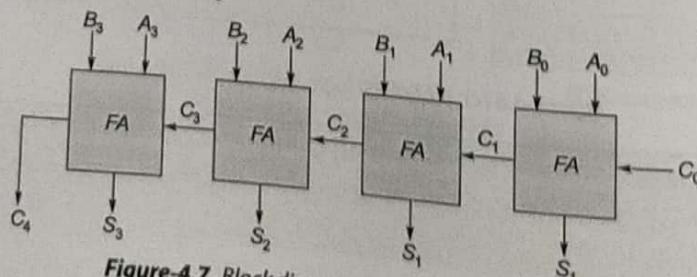


Figure-4.7 Block diagram of four bit parallel adder

Hence, 'n' binary parallel adder requires-

- 'n' full adder.
- or $(n-1)$ full adder and a half adder
- or $(n-1) [2 \text{ half adder} + 1 \text{ OR gate}]$ and a half adder
- or $(2n-1)$ half adder and $(n-1)$ OR gate.

To demonstrate with a specific example, consider the two binary numbers

$$A = 1011 \text{ and } B = 0011$$

Here, the input carry C_0 in the least significant position must be 0. The value of C_{i+1} in a given significant position is the output carry of the full adder. This value is transferred into the input carry of the full adder that adds the bits one higher significant position to the left. The sum bits are thus generated starting from the right most position and are available as soon as the corresponding previous carry bit is generated.

Subscript (i)	3	2	1	0
Input carry (C_i)	0	1	1	0
Augend (A_i)	1	0	1	1
Addend (B_i)	0	0	1	1
Sum (S_i)	1	1	1	0
Output carry (C_{out})	0	0	1	1

Carry Propagation

The addition of two binary numbers in parallel implies that all the bits of the input variables are available for computation at the same time. As, in any combinational circuit, the signal must propagate through the gates before the output is available in the output terminals. The total propagation time is equal to the total propagation delay of typical gates in the circuit. The longest propagation delay time in an adder is the time it takes the carry to propagate through the full adder. Thus, carry propagation delay for each full adder is the time between the application of the carry in and the occurrence of carry out. In parallel adder, propagation delay is present from input carry to output carry, hence it is also called 'RIPPLE CARRY ADDER'.

- In 'n' bit parallel adder, minimum delay to provide the final result is equal to $2nt_{pd}$ (where t_{pd} = propagation delay of each gate) that is why parallel adder becomes very slow.
- To overcome this difficulty a new type of adder is used which is called "LOOK AHEAD CARRY ADDER".

Example - 4.5 A one bit full adder takes 75 nsec to produce sum and 50 nsec to produce carry. A 4 bit parallel adder is designed using this type of full adder. The maximum rate of additions per second can be provided by 4 bit parallel adder is $A \times 10^6$ additions/sec. The value of A is

Solution:

$$\text{Minimum propagation delay} = (3 \times 50 + 75) \text{ nsec} = 225 \text{ nsec}$$

$$\text{Maximum additions per second} = \frac{1}{225 \text{ nsec}} = 4.44 \times 10^6 \text{ additions/sec} \Rightarrow A = 4.44$$

The Look-ahead Carry Adder

- In the case of parallel adder, the speed with which an addition can be performed is governed by the time required for the carries to propagate or ripple through all of the stages of the adder. The look-ahead-carry adder speeds up the process by eliminating this ripple carry delay.
- It examines all the input bits simultaneously and also generates the carry-in bits for all the stages simultaneously.
- Consider the full adder circuit shown in Figure 4.8.

$$\text{We have, } P_i = A_i \oplus B_i \Rightarrow \text{Carry propagates}$$

$$G_i = A_i B_i \Rightarrow \text{Carry generates}$$

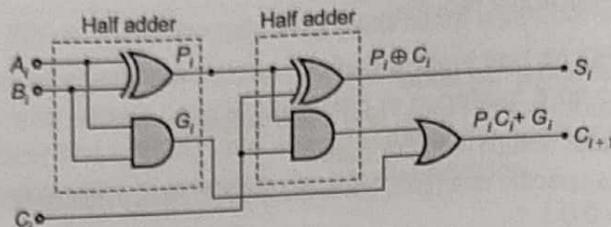


Figure 4.8 Lookahead carry adder

Thus, the output sum and carry can respectively be expressed as

$$S_i = P_i \oplus C_i \quad \text{and} \quad C_{i+1} = G_i + P_i C_i$$

Based on these, the expressions for sum and carry for four bit addition are:

$$C_0 = \text{input carry}; \quad C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 \quad \text{or} \quad C_2 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + G_0 P_1 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 \cdot [P_1 P_0 C_0 + P_1 G_0] + G_1$$

$$\text{or} \quad C_3 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

Since, the boolean function for each output carry can be expressed in sum-of-product form, thus each function can be implemented with one level of AND gates followed by an OR gate.

- The construction of a four bit adder with a lookahead carry scheme is shown in Figure 4.9. It is clear that C_3 does not have to wait for C_2 and C_1 to propagate; in fact C_3 is propagated at the same time as C_2 and C_1 . So that delay for output carry must be reduced and the increase in the speed of operation is achieved at the expense of additional hardware complexity.

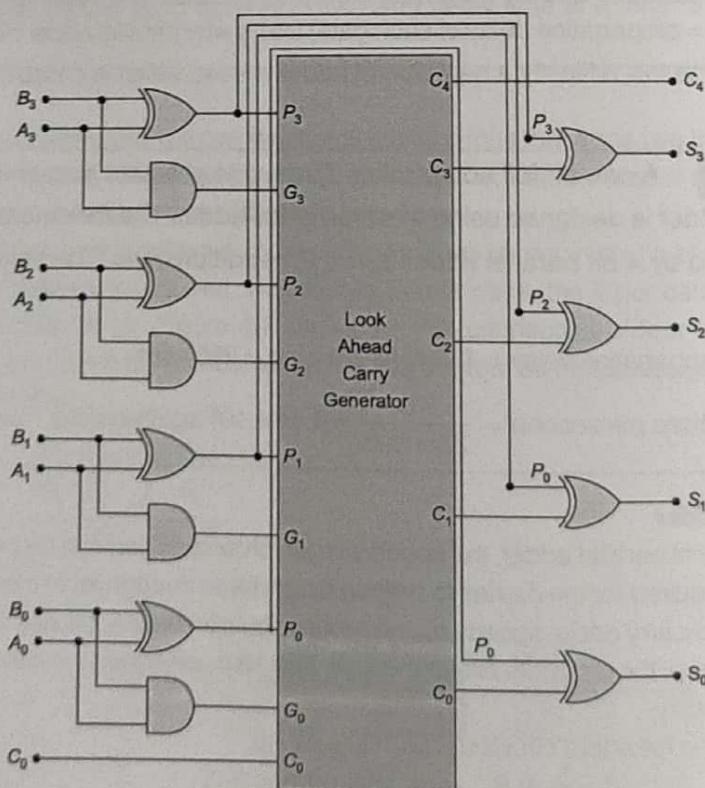


Figure 4.9 A four bit adder with lookahead carry scheme

Remember

- A Look-ahead-carry scheme for 'n' bit addition requires n OR gates and $\frac{n(n+1)}{2}$ AND gates.
- To generate the carry output, the carry circuit requires 3 logic gate delay and for sum output it requires 4 logic gate delay.

The Serial Adder

- A serial adder is used to add two binary numbers in serial form.
- The two binary numbers to be added serially are stored in two shift registers designated as A and B. The circuit adds one pair at a time with the help of one full adder circuit as shown in Figure 4.10. The carry output from the full adder is applied to a D flip-flop, the output of which is then used as a carry input for the next pair of significant bits. However the sum bit S from the output of the full adder can be transferred into a third shift register.

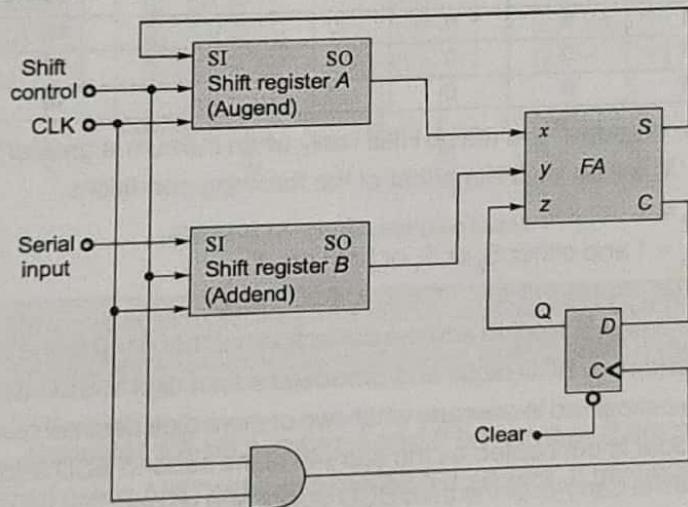


Figure-4.10 Block diagram of serial adder

Difference between Serial adder and Parallel adder

Table-4.3 Difference between serial and parallel adder

Serial Adder	Parallel Adder
<ol style="list-style-type: none"> 1. A serial adder uses shift registers 2. A serial adder requires only one full adder and a carry flip flop. 3. Serial adder is a sequential circuit. 	<ol style="list-style-type: none"> 1. A parallel adder uses registers with parallel loads. 2. The numbers of full adder circuits in the parallel adder is equal to the number of bits in the binary number. 3. Parallel adder, excluding registers, is a combinational circuit

The BCD Adder

- The BCD addition can be performed in accordance with the following steps:
1. Add two 4-bit BCD code groups for each decimal digit position using straight binary addition.
 2. For those positions where the sum is 9 (1001) is less, the SUM is in proper form and no correction is required.

3. When the sum of two digits is greater than 1001 (decimal 9), 0110 must be added to this sum and the generated carry must be added to the next decimal position.

Therefore unlike the binary parallel adder the circuitry for a BCD addition must include the logic needed to detect whenever the sum is greater than 1001 (decimal 9), so that the correction can be added in. Those cases where the sum is greater than 1001 are listed in Table 4.4.

For example, if the two BCD code groups $A_3 A_2 A_1 A_0$ and $B_3 B_2 B_1 B_0$ are applied to a 4 bit adder, the adder will output $S_4 S_3 S_2 S_1 S_0$ where S_4 is actually C_4 , the carry out of the MSB bits.

Table-4.4

S_4	S_3	S_2	S_1	S_0	Decimal Number
0	1	0	1	0	10
0	1	0	1	1	11
0	1	1	0	0	12
0	1	1	0	1	13
0	1	1	1	0	14
0	1	1	1	1	15
1	0	0	0	0	16
1	0	0	0	1	17
1	0	0	1	0	18

Let us define a logic output 'X' that will go HIGH only when the sum is greater than 01001. Thus from the above table, it is clear that 'X' will be HIGH for either of the following conditions.

- Whenever $S_4 = 1$
- Whenever $S_3 = 1$ and either S_2 or S_1 or both are 1.

This condition can be expressed as: $X = S_4 + S_3(S_2 + S_1)$

Whenever 'X' = 1, it is compulsory to add the correction number 0110 to the sum bit to generate a carry.

A BCD adder that adds two BCD digits and produces a sum digit in BCD as shown in Figure 4.11. Two or more BCD adders can be connected in cascade when two or more digit decimal numbers are to be added. The carry out of the first BCD adder is connected as the carry-in of the second BCD adder, the carry of the second BCD adder is connected as the carry-in of the third BCD adder and so on.

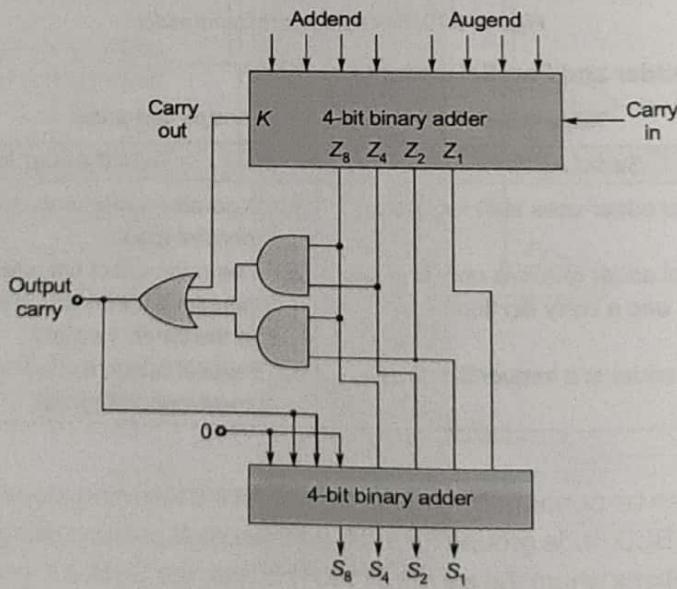


Figure-4.11 Block diagram of a BCD adder



2's Complemented Adder

If we perform $(A - B)$ operation, then we take it as $A + (-B)$ i.e. A (as it is) + (2's complement of B) For this purpose we use a control circuit by using Ex-OR gate. Consider a 4-bit 2's complement parallel adder as shown in Figure 4.12 below:

Let, $A = A_3 \ A_2 \ A_1 \ A_0$
 $B = B_3 \ B_2 \ B_1 \ B_0$

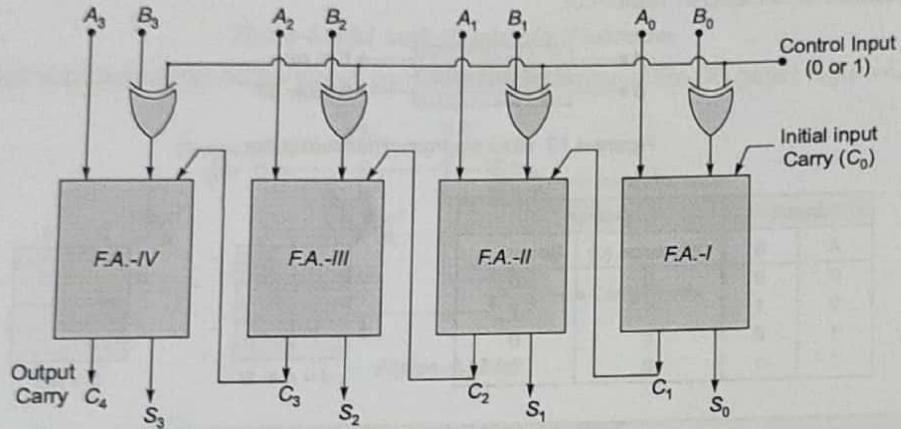
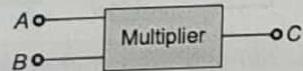


Figure-4.12 2's Complemented Adder

NOTE

- When control input = "0" \Rightarrow circuit acts as an "ADDER".
- When control input = "1" \Rightarrow circuit acts as a "SUBTRACTOR".

Example-4.6 Consider a 3-bit number A and 2 bit number B are given to a multiplier. The output of multiplier is realized using AND gate and one bit full adders. If minimum number of AND gates required are X and one bit full adders required are Y , then $X + Y = \underline{\hspace{2cm}}$.

**Solution:**

Let,

$$\begin{array}{r}
 A = \quad a_2 \quad a_1 \quad a_0 \\
 B = \quad \quad \quad b_1 \quad b_0 \\
 \hline
 A \times B = \quad a_2 b_0 \quad a_1 b_0 \quad a_0 b_0 \\
 \quad b_1 a_2 \quad b_1 a_1 \quad b_1 a_0 \\
 \hline
 \quad b_1 a_2 \quad (a_2 b_0 + a_1 b_1) \quad (a_1 b_0 + b_1 a_0) \quad a_0 b_0 \\
 \hline
 C_3 \quad C_2 \quad C_1 \quad C_0
 \end{array}$$

Number of AND gates required $X = 6$

Number of one bit full adders required $Y = 3$

$$X + Y = 6 + 3 = 9$$

4.2.2 Subtractors

The Half Subtractor

- A half subtractor is a combinational circuit that subtracts one bit from the other and produces the difference.
- A half subtractor circuit with two input variables designated as A (minuend) and B (subtrahend), and output variables as Difference ' d ' and Borrow ' b ' is shown in Figure 4.13. The truth Table of half subtractor is listed in Table 4.5.

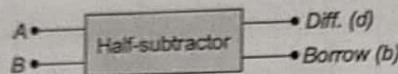


Figure-4.13 Block diagram of half-subtractor

Input		Output	
A	B	Difference (d)	Borrow (b)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

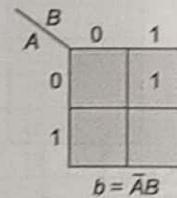
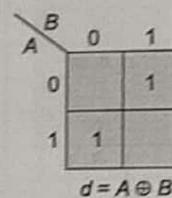


Table-4.5 Truth Table of half-subtractor

- The simplified Boolean expression for the two output can be obtained directly from the truth Table. The logical expressions for difference (d) and Borrow (b) are:

$$d = \bar{A}\bar{B} + A\bar{B} = A \oplus B \quad \text{and} \quad b = \bar{A}B$$

- Implementation of half subtractor circuit:

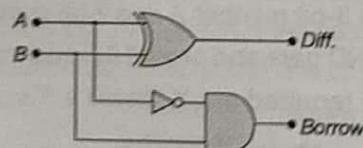


Figure-4.13(a) Logic diagram of half Subtractor

- A half subtractor can also be realized using either only NAND gates or only NOR gates as shown in Figure 4.13 (b) and (c) respectively.

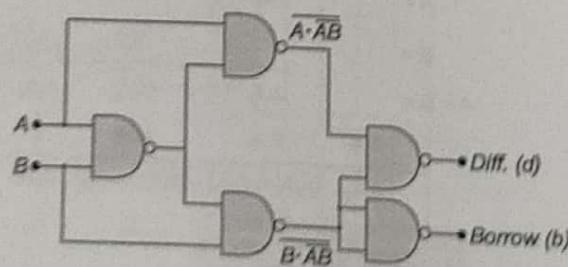


Figure-4.13 (b) Logic diagram of half Subtractor



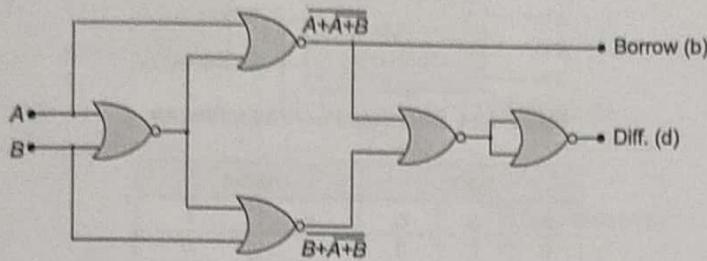


Figure-4.13 (c) Logic diagram of half Subtractor

- Half subtractor/Half adder circuit by using control action of Ex-OR gate (Figure 4.13 (d)):

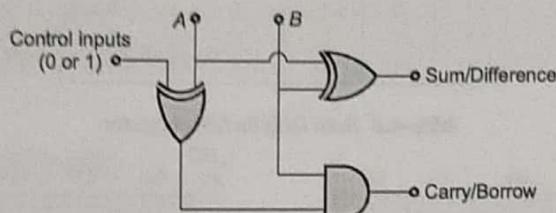


Figure-4.13 (d)

Remember

- When Control input = 0 \Rightarrow Half adder operation
- When Control input = 1 \Rightarrow Half subtractor operation.

Example-4.7 For a binary subtractor having two inputs A and B, the correct set of logical expressions for the output D (= A minus B) and X (= Borrow) are:

- | | |
|------------------------------------------------------|------------------------------------------------------|
| (a) $D = AB + \bar{A}\bar{B}$, $X = \bar{A}B$ | (b) $D = \bar{A}\bar{B} + A\bar{B}$, $X = A\bar{B}$ |
| (c) $D = \bar{A}\bar{B} + A\bar{B}$, $X = \bar{A}B$ | (d) $D = AB + A\bar{B}$, $X = A\bar{B}$ |

Solution: (c)

Truth Table for half subtractor

A	B	D (Difference)	X (Borrow)
0	0	0	0
0	0	0	0
1	1	1	1
1	1	1	1

$$\therefore D = \bar{A}\bar{B} + A\bar{B} = A \oplus B$$

$$X = \bar{A}B$$

The Full Subtractor

- A full subtractor is an arithmetic circuit which performs a subtraction between two bits taking into account that a '1' may have been borrowed by a lower significant stage. Thus a full subtractor has three inputs and two outputs.
- The block diagram of a full subtractor is shown in Figure 4.14. Table 4.6 represents the truth table for full subtractor.


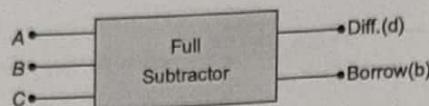


Figure-4.14 Block diagram of a full subtractor

Input			Output	
A	B	C	d	b
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Table-4.6 Truth Table for full subtractor

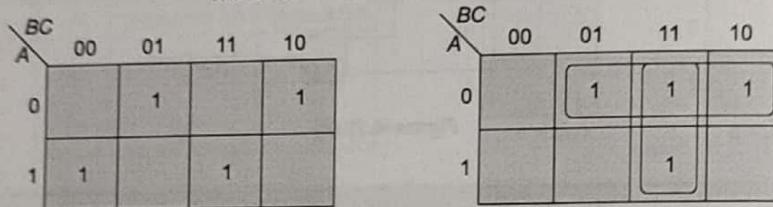

(i) K-map for Difference

(ii) K-map for Borrow

Figure-4.15 K-maps for full subtractor

- From the truth Table and the maps for the outputs of the full adder as shown in Table 4.6 and Figure 4.15 respectively, the logical expressions for Difference and Borrow are:

$$d = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$b = \bar{A}C + \bar{A}B + BC$$

Also,

$$d = A \oplus B \oplus C \quad \text{or} \quad d = \Sigma_m (1, 2, 3, 7)$$

$$\begin{aligned} b &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= C(A \oplus B) + \bar{A}B \end{aligned}$$

- Implementation of full subtractor circuit: From the above expression a full subtractor circuit can be realized in SOP form or with two half subtractor and an OR gate as shown in Figure 4.16 (a).

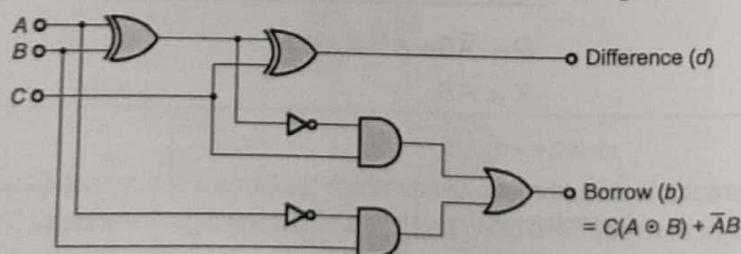


Figure-4.16 (a) Logic diagram of full subtractor in SOP form

- The ANSI/IEEE standard logic diagram of full subtractor is shown as


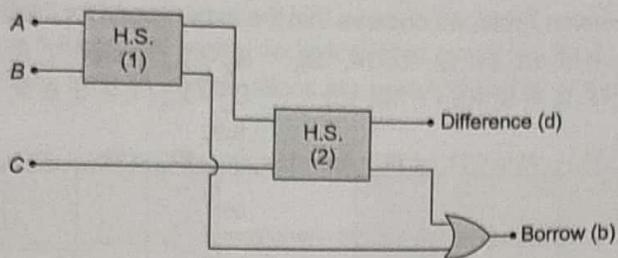


Figure-4.16 (b) ANSI/IEEE standard diagram for full subtractor

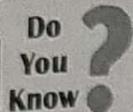

The full subtractor can also be realized using universal logic i.e., either only NAND gates or only NOR gates. The total number of NAND gates/NOR gates required to implement a full subtractor is equal to "9".

4.3 Non-arithmetic Circuit

4.3.1 Code Converters

- The availability of a large variety of codes for the same discrete elements of information results in the use of different codes by different systems. Therefore a conversion circuit is inserted between the two system if each uses different codes for the same information. Hence a "code converter" is a logic circuit which changes data presented in one type of binary code to another type of binary code. It makes two systems compatible even though each uses a different binary code.
- Code converters are usually multiple output circuits.

Binary to Gray Code Converter

- The input to the 4-bit binary-to-gray code converter circuit is a 4-bit binary and the output is a 4-bit gray code. There are 16 possible combinations of 4-bit binary input and all of them are valid. Hence no don't care.
- The 4-bit binary and the corresponding gray code are shown in the conversion Table 4.7.

Table-4.7 Conversion of 4-bit binary to gray code

Binary code				Gray Code			
B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	1
1	0	0	1	1	1	1	1
1	0	1	0	1	1	1	0
1	0	1	1	1	0	1	0
1	1	0	0	1	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	1	0	0	0
1	1	1	1	0	0	0	0

- From the conversion Table, we observe that the expressions for the outputs are:

$$\begin{aligned} G_3 &= \Sigma_m (8, 9, 10, 11, 12, 13, 14, 15); & G_2 &= \Sigma_m (4, 5, 6, 7, 8, 9, 10, 11) \\ G_1 &= \Sigma_m (2, 3, 4, 5, 10, 11, 12, 13); & G_0 &= \Sigma_m (1, 2, 5, 6, 9, 10, 13, 14) \end{aligned}$$

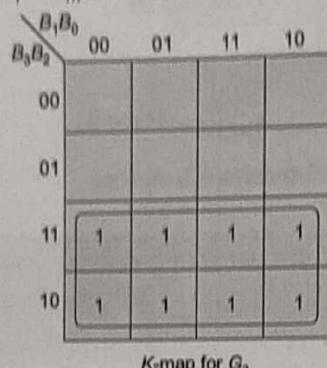
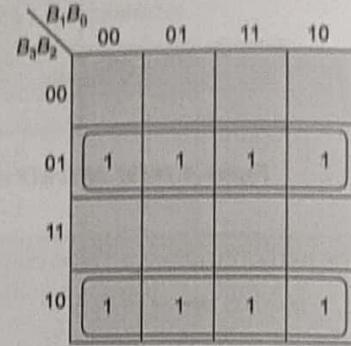
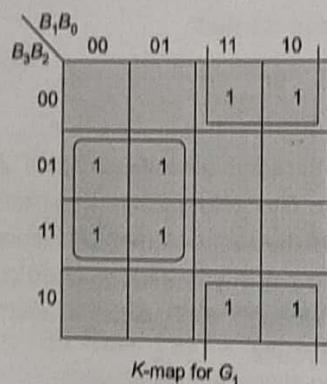
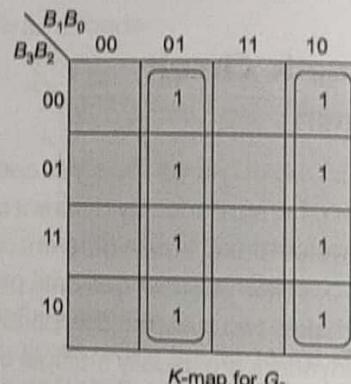
K-map for G_3 K-map for G_2 K-map for G_1 K-map for G_0

Figure-4.17(a) K-map for Binary-to-Gray code converter

- We have, the minimal expressions for the output obtained from the K-map as:

$$G_3 = B_3; \quad G_2 = B_3 \oplus B_2$$

$$G_1 = B_2 \oplus B_1; \quad G_0 = B_1 \oplus B_0$$

- Based on the above expressions, a circuit can be drawn as shown in Figure 4.17(b)

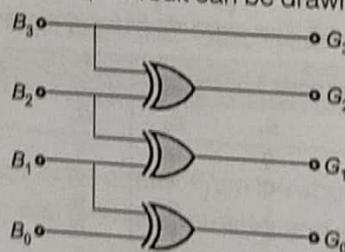


Figure-4.17(b) Logic Diagram of Binary-to-Gray Code Converter

- Thus, the basic conversion concept is,

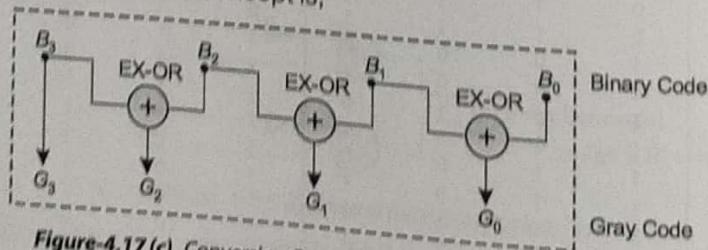


Figure-4.17(c) Conversion Concept for Binary-to-Gray Code converter

Gray-to-Binary code Converter

- The input to the 4-bit gray to binary code converter circuit is a 4-bit gray code and the output is a 4-bit binary. Thus, total 16 combinations are possible and all of them are valid. Hence no don't care.
- The 4-bit input gray code and the corresponding output binary numbers are shown in the conversion Table 4.8.





Table-4.8 Conversion of 4-bit Gray-to-Binary code

Gray Code				Binary Code			
G_3	G_2	G_1	G_0	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

- From the conversion Table, we observe that the expression for the outputs are:

$$B_3 = \Sigma_m(8, 9, 10, 11, 12, 13, 14, 15); \quad B_2 = \Sigma_m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$B_1 = \Sigma_m(2, 3, 4, 5, 8, 9, 14, 15); \quad B_0 = \Sigma_m(1, 2, 4, 7, 8, 11, 13, 14)$$

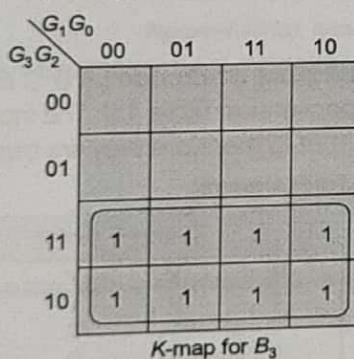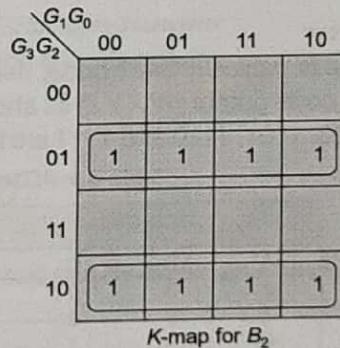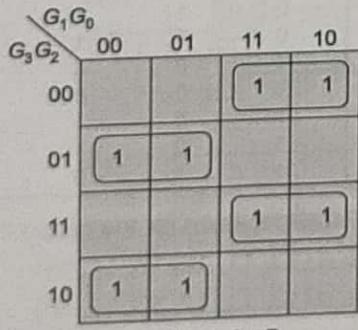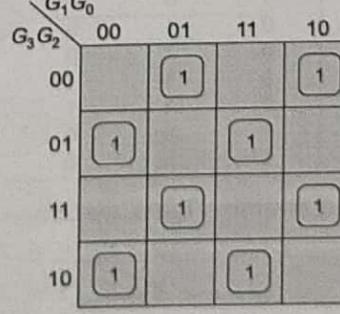K-map for B_3 K-map for B_2 K-map for B_1 K-map for B_0 **Figure-4.18(a)** K-map for Gray-to-Binary code conversion

- We have, the minimal expressions for the outputs obtained from the K-map as

$$\begin{aligned}B_3 &= G_3; & B_2 &= B_3 \oplus G_2 \\B_1 &= B_2 \oplus G_1; & B_0 &= B_1 \oplus G_0\end{aligned}$$

- Based on the above expressions, a logic circuit can be drawn as shown in Figure 4.18(b).

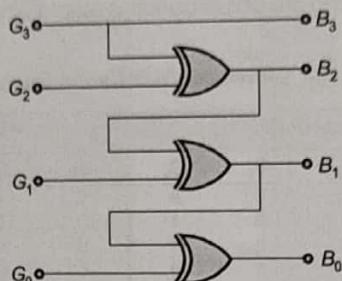


Figure-4.18 (b) Logic Diagram of Gray-to-Binary Code Converter

- Thus, the basic conversion concept is

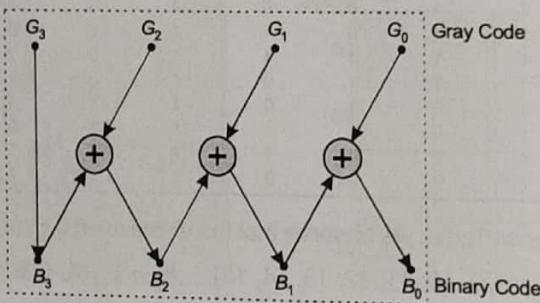


Figure-4.18 (c) Conversion concept for Gray-to-Binary code conversion

BCD to Excess-3 Converter

- BCD code is basically 8421 code, hence 4-bit input BCD code ($A B C D$) is converted into the excess-3 code output ($W X Y Z$) as shown in conversion Table 4.9. The input combinations 1010, 1100, 1101, 1110 and 1111 are invalid in BCD therefore they are treated as don't cares.

Table-4.9 BCD to Excess-3 code converter

BCD Code				Excess-3 Code			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	1
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	1	0
1	0	0	1	1	1	0	0

- From the conversion Table, we observe that the expression for the outputs are:

$$W = \Sigma_m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$X = \Sigma_m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$Y = \Sigma_m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$Z = \Sigma_m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

Drawing the K-map for the above expressions

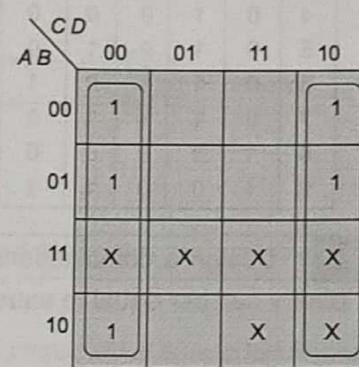
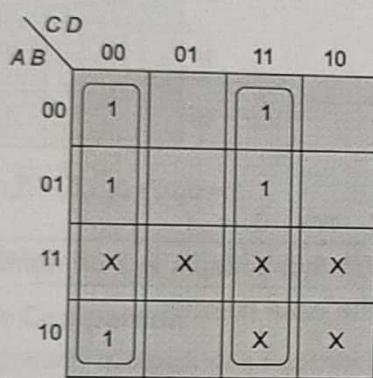
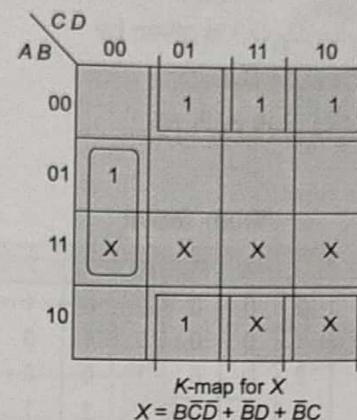
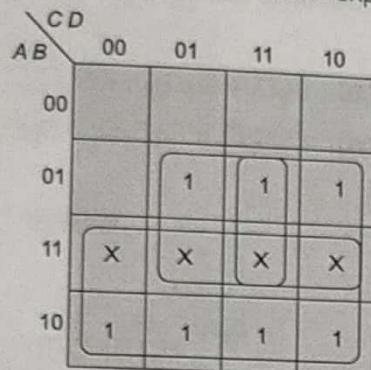


Figure-4.19 (a) K-map for BCD to Excess-3 converter

- Thus, we have the minimal expressions for the outputs obtained from K-map as

$$Z = \bar{D}$$

$$Y = \bar{C}\bar{D} + CD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$W = A + BC + BD$$

- Based on the above expressions, a logic circuit can be drawn as shown in Figure 4.19 (b).

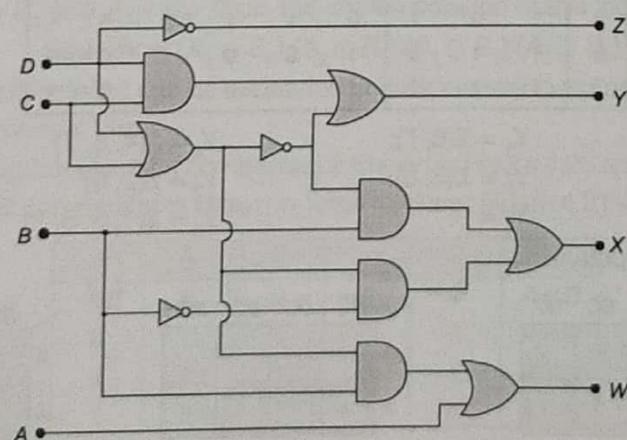


Figure-4.19 (b) Logic Diagram of BCD to Excess-3 Converter

Example - 4.8 The minimal function that can detect a "divisible by 3" 8421 BCD code digit (representation is $D_8 D_4 D_2 D_1$) is given by

- (a) $D_8 D_1 + D_4 D_2 + \bar{D}_8 D_2 D_1$
 (c) $D_8 D_1 + D_4 D_2 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$


- (b) $D_8 D_1 + D_4 D_2 \bar{D}_1 + \bar{D}_4 D_2 D_1 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$
 (d) $D_4 D_2 \bar{D}_1 + D_4 D_2 D_1 + D_8 \bar{D}_4 D_2 D_1$

Solution: (b)

Truth Table:

	D_8	D_4	D_2	D_1	Y
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1

K-Map:

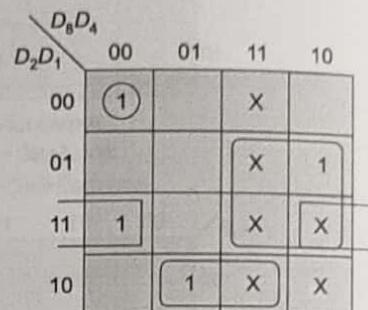

$$Y = D_8 D_1 + D_4 D_2 \bar{D}_1 + \bar{D}_4 D_2 D_1 + \bar{D}_8 \bar{D}_4 \bar{D}_2 \bar{D}_1$$

Example - 4.9 Design a combinational circuit that accepts a 3-bit number as input and generates an output binary number equal to square of the input number.

Solution:

Largest 3 bit number is $= (111)_2 = (7)_{10}$

So square of $(7)^2 = (49)_{10} = (110001)_2$, that is, it requires 6 bits to represent output.




Let these outputs are: $Y_5, Y_4, Y_3, Y_2, Y_1, Y_0$

	Input			Output					
	A	B	C	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	1
2	0	1	0	0	0	0	1	0	0
3	0	1	1	0	0	1	0	0	1
4	1	0	0	0	1	0	0	0	0
5	1	0	1	0	1	1	0	0	1
6	1	1	0	1	0	0	1	0	0
7	1	1	1	1	1	0	0	0	1

Therefore,

$$\begin{aligned} Y_5 &= \Sigma(6, 7); & Y_4 &= \Sigma(4, 5, 7) \\ Y_3 &= \Sigma(3, 5); & Y_2 &= \Sigma(2, 6) \\ Y_1 &= 0; & Y_0 &= \Sigma(1, 3, 5, 7) \end{aligned}$$

Solving for above outputs

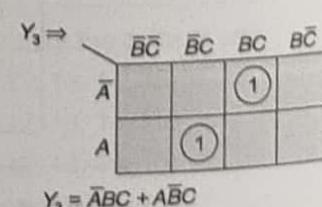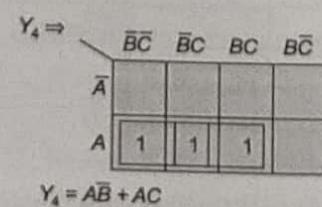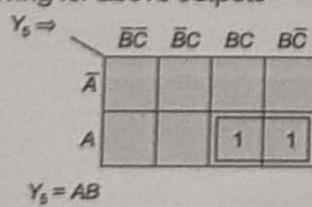

$Y_2 \Rightarrow$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}				1
A				1


$Y_2 = \bar{B}\bar{C}$

 $Y_1 = 0$

$Y_0 \Rightarrow$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}		1	1	
A	1	1		

$Y_0 = C$

Now the circuit will be

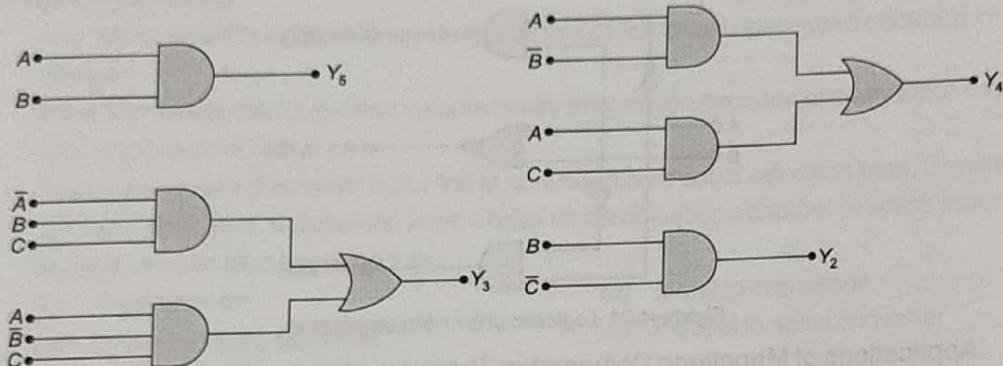

$$Y_1 = 0 \text{ and } Y_0 = C$$

Assuming inverted inputs are available, also 3-input AND gates are available.

4.3.2 Magnitude Comparator

- A magnitude comparator is a combinational circuit which is used to compare two numbers A and B and determines their relative magnitudes.
- Let A and B are the two inputs for which the output of the comparator is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$.

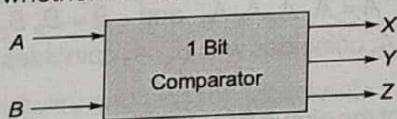


Figure-4.20 Block diagram of 1-bit comparator

- The EX-NOR gate is a basic comparator, because its output is a 1 only if its input bits coincide. For example, two 4-bit binary numbers, $A_3 A_2 A_1 A_0$ and $B_3 B_2 B_1 B_0$ are equal if and only if, $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = B_0$. Thus, the implementation of this logic:

$$\text{Equality} = (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$
It is clear that this circuit can be expanded or compressed to accommodate binary numbers with any other number of bits.
- The block diagram of a 1-bit comparator is shown in Figure 4.20 and the truth table and the logic circuit for 1-bit comparator is shown in Table 4.10 and Figure 4.21 respectively.

A	B	X	Y	Z	Output
0	0	0	1	0	$A = B$
0	1	1	0	0	$A < B$
1	0	0	0	1	$A > B$
1	1	0	1	0	$A = B$

Table-4.10 Truth table for 1-bit comparator

from the truth table it is clear that

if $A = 1$ and $B = 0$, then $A > B$

then, $A > B$; $X = A\bar{B}$

if $A = 0$ and $B = 1$, then $A < B$

then, $A < B$; $X = \bar{A}B$

if A and B coincide, i.e., $A = B = 0$ or if $A = B = 1$, then $A = B$

then, $A = B$; $Y = A \odot B$

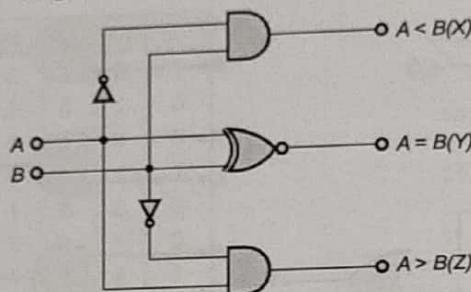


Figure-4.21 Logic circuit for 1-bit comparator

- Applications of Magnitude Comparator:** These are often used as part of the address decoding circuitry used in a computer to select a specific "input-output device" or area of memory for the storage or retrieval of data. It is also useful in control applications where a binary number representing the physical variable being controlled (e.g. position, speed) is compared with a reference value.

Example-4.10 Implement a circuit which gives 4-bit equality condition.

Solution:


Let, the two inputs as

$$A = A_3 A_2 A_1 A_0 \text{ and } B = B_3 B_2 B_1 B_0$$

Equality condition holds when A_3 coincides with B_3 , A_2 coincides with B_2 , A_1 coincides with B_1 and A_0 coincides with B_0 .

Therefore the implementation of the circuit involves.
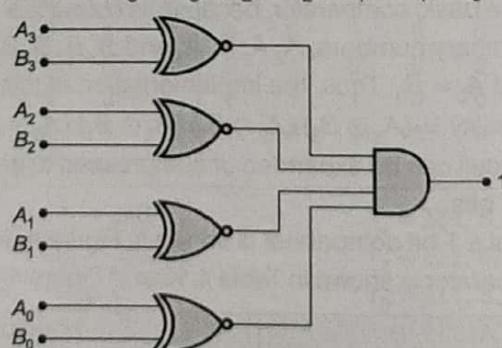
$$\text{Equality} = (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$



Example-4.11 The output Y of a 2-bit comparator is logic 1 whenever the 2-bit input A is greater than the 2-bit input B . The number of combination for which the output is logic 1, is

- (a) 4
(c) 8

- (b) 6
(d) 10



Solution : (b)Output will be 1 if $A > B$.If $B = 00$ then there will be three combinations for which output will be 1 i.e. when $A = 01, 10$ or 11 .If $B = 01$ there will be two conditions i.e. $A = 10$ and 11 .If $B = 10$ there will be one condition i.e. $A = 11$.

So, total 6 combinations are there for which output will be 1.

4.3.3 Multiplexers (MUX)

- The 'Multiplexer' is a special, versatile and one of the most widely used standard circuit in digital design.
- It is a combinational circuit that selects binary information from one of many input lines and directs it to single output line.
- The selection of a particular input line is controlled by a set of selection lines. Generally, there are ' 2^m ' input lines and ' n ' selection lines whose bit combinations determine which input is selected.
- Multiplexer can also be named as
 - (i) Data selector
 - (ii) Many to one circuit
 - (iii) Universal logic converter
 - (iv) Parallel to serial converter
 - (v) Waveform generator
- If ' m ' be the total number of data input and ' n ' be the number of selection lines, then

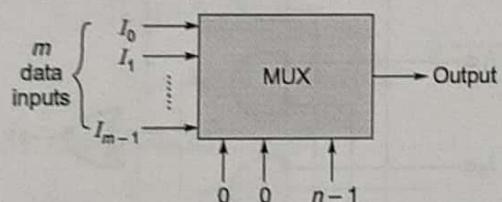


Figure-4.22 Functional diagram of a digital multiplexer

The Basic 2-line to 1-line MUX

Figure 4.23 shows the logic circuitry and function table for 2 : 1 MUX. It has two input lines as I_0 and I_1 , and one data select line S . The output line is designated as Y .

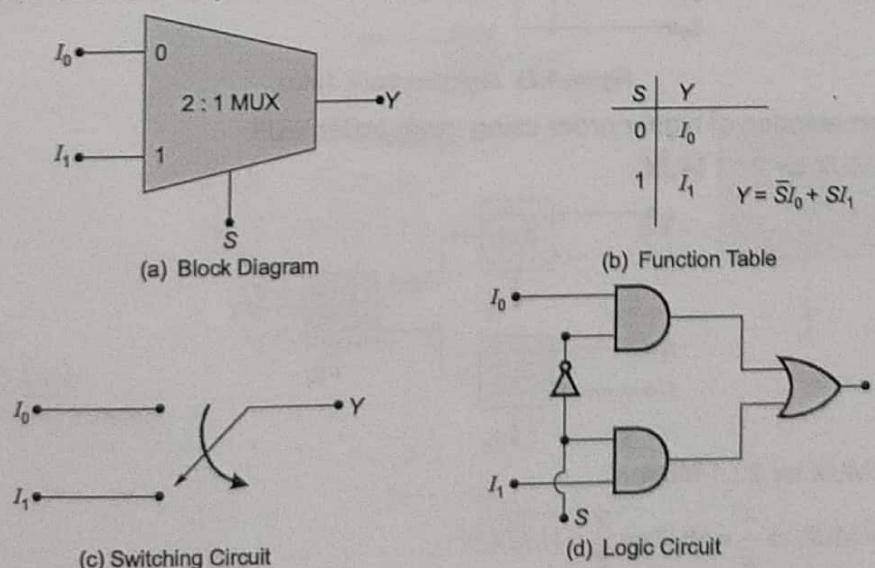
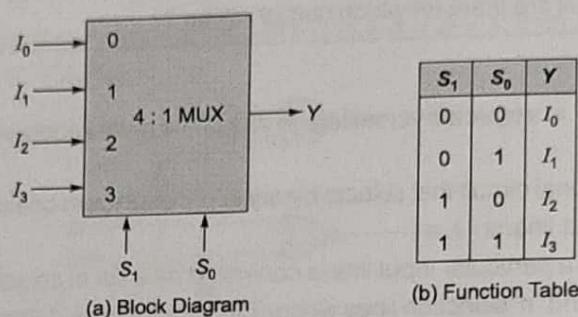


Figure-4.23 2:1 Multiplexer

The 4-line to 1-line MUX


A 4 : 1 line multiplexer is shown in Figure 4.24. Each of the four inputs, I_0, I_1, I_2 and I_3 are applied to the input of MUX and logic levels applied to the selection lines S_0 and S_1 .

The logic circuitry based on the function table is shown in Figure 4.25.

**Figure-4.24** 4:1 Multiplexer


from the function table, we have

$$Y = \overline{S_1} \overline{S_0} I_0 + \overline{S_1} S_0 I_1 + S_1 \overline{S_0} I_2 + S_1 S_0 I_3$$

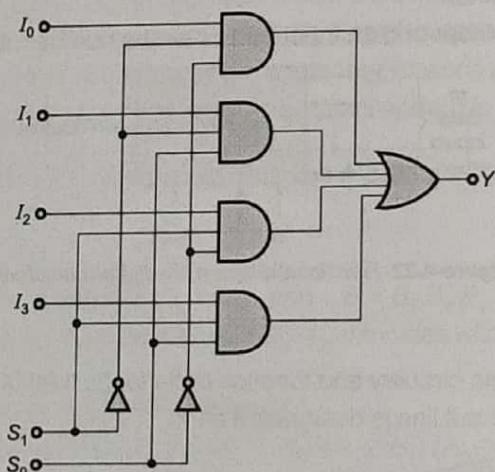**Figure-4.25** Logic circuit of 4:1 MUX

- Implementation of higher order using lower order MUX:

4 : 1 MUX by 2 : 1 MUX

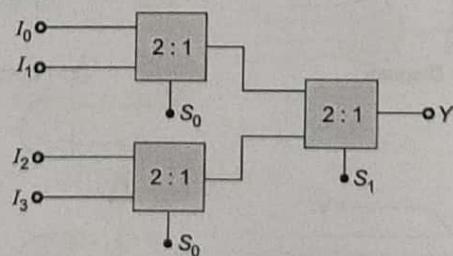

8 : 1 MUX by 2 : 1 MUX

$$\frac{8}{2} = 4 \text{ MUX} \Rightarrow \frac{4}{2} = \text{MUX} \Rightarrow \frac{2}{2} = 1 \text{ MUX}$$


\therefore Total number of 2 : 1 MUX required = $4 + 2 + 1 = 7$

Given MUX	To be Implemented	Required
2:1	16:1	$8 + 4 + 2 + 1 = 15$
4:1	16:1	$4 + 1 = 5$
4:1	64:1	$16 + 4 + 1 = 21$
8:1	64:1	$8 + 1 = 9$
8:1	256:1	$32 + 4 + 1 = 37$

NOTE: To implement $2^n:1$ MUX by using 2:1 MUX, the total number of 2:1 MUX required is $(2^n - 1)$

MUX as an Universal Logic Gate

- Buffer:

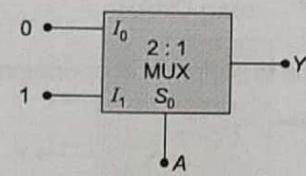

$$Y = \text{Output} = A$$

- NOT gate/Invertor:

As we know,

$$Y = \overline{S_0}I_0 + S_0I_1$$

$$Y = \overline{A}I_0 + AI_1$$

∴

$$Y = \overline{A} \text{ For NOT gate}$$

∴

$$I_0 = 1 \text{ and } I_1 = 0$$


- AND gate:

For AND operation

$$Y = AB$$

$$Y = \overline{S_0}I_0 + S_0I_1$$

Logic

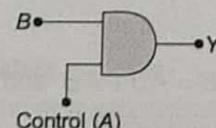

$$A = 0 : Y = 0 = I_0$$

$$A = 1 : Y = 0 = I_1$$

$$Y = \overline{A} \cdot 0 + AB$$




So,

$$I_0 = 0 \text{ and } I_1 = B$$

- OR gate:

For OR operation

$$Y = A + B$$

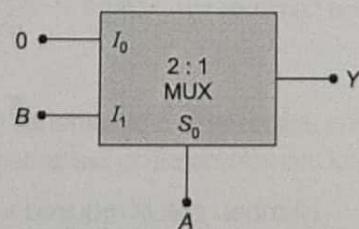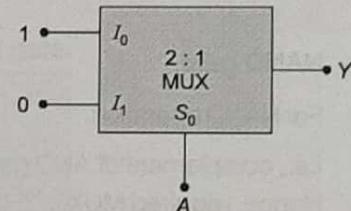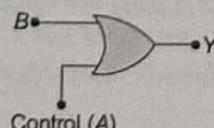


for, $A = 0 : Y = B = I_0$
 for, $A = 1 : Y = 1 = I_1$
 Therefore,

So, $I_0 = B$ and $I_1 = 1$

$$Y = \overline{S_0} I_0 + S_0 I_1$$

$$Y = \overline{A} I_0 + A I_1$$

$$Y = \overline{A} \cdot B + A \cdot 1$$

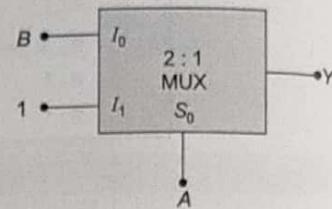


- NOR gate:

$$\text{For NOR operation } Y = \overline{A+B}$$

i.e., complement of OR gate.

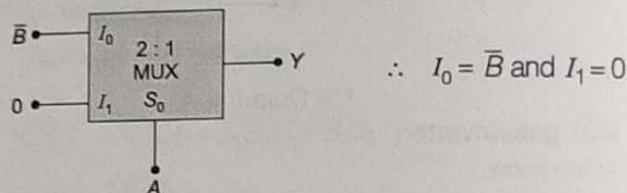Hence, required MUX is 2, one to perform OR operation and other one to perform complement.




- NAND gate:

$$\text{For NAND operation, } Y = \overline{AB}$$

i.e., complement of AND gate.

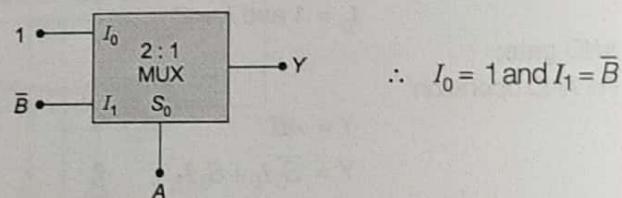
Hence, required MUX is 2, one to perform AND operation and other one to perform complement.



- EX-OR gate:

For Ex-OR operation
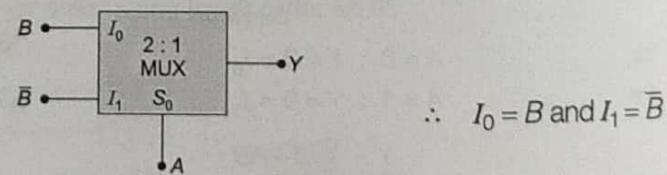
$$Y = A \oplus B = \overline{AB} + A\bar{B} \text{ and } Y = \overline{S_0} I_0 + S_0 I_1 = \overline{A} I_0 + A I_1$$



Number of MUX required = 2


- EX-NOR gate:

For Ex-NOR operation

$$Y = A \odot B = \overline{A}\bar{B} + A\bar{B}$$

$$\therefore Y = \overline{A} I_0 + A I_0$$

Number of required MUX = 2.

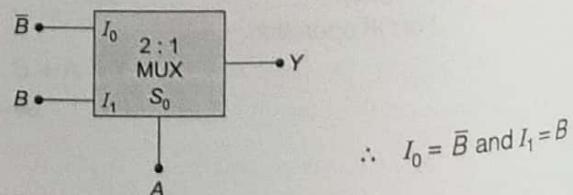


- In order to implement logic gates with 4 : 1 MUX, truth table is required.

For example,

AND gate


Truth table:

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

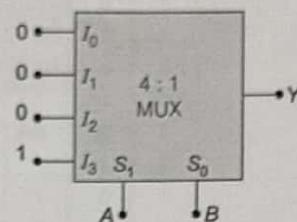


Similarly,


OR gate:

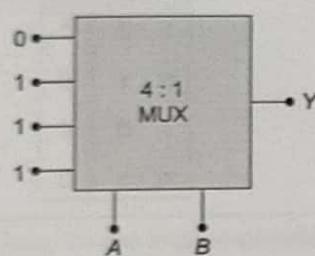


NAND gate:

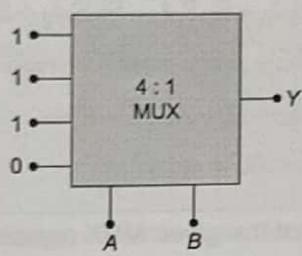


NOR gate:

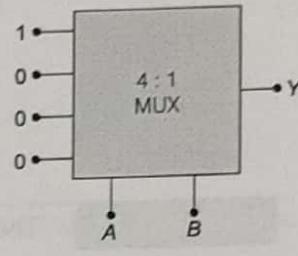

EX-OR gate:

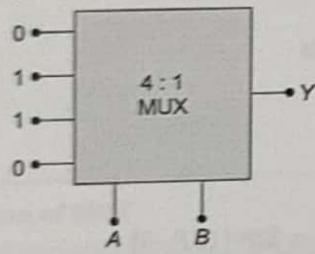

EX-NOR gate:

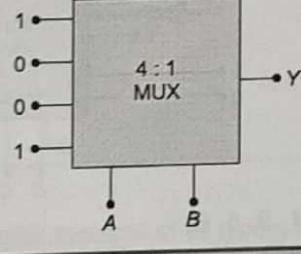

NOTE




- For implementation of basic gates, the required number of 2 : 1 MUX is 1
- For implementation of universal and special purpose gates the required number of 2 : 1 MUX is 2.

Boolean Function Implementation by using MUX

For implementing any boolean function of n -variables with a $2^{n-1} : 1$ MUX, we required some general procedure.

- Express the function in its sum of product (SOP) form.
- In the ordered sequence of n -variables, connect $(n - 1)$ variables to the select line and the single highest order position variable to the input line with complemented or uncomplemented form including 0 and 1.
- List the inputs of MUX (all the minterms) in two rows. The 1st row lists all those minterms where single variable is complemented and in 2nd row with uncomplemented form.
- Circle all the minterms of the function and inspect each column separately.
- If two minterms in a column are not circled, apply '0' to the corresponding MUX input.
- If two minterms are circled, apply '1' to the corresponding MUX input.
- If one minterm is circled (either upper row or lower row), then its front value is the corresponding MUX input.

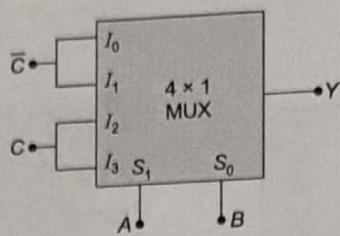Example - 4.12 For given 4 : 1 MUX, the minimize expression is



- (a) $Y = A \oplus C$
(c) $Y = B \odot C$

- (b) $Y = A \odot C$
(d) $Y = B \oplus C$


Solution: (b)

$$\begin{aligned} Y &= \overline{S_0} \overline{S_1} I_0 + S_0 \overline{S_1} I_1 + \overline{S_0} S_1 I_2 + S_0 S_1 I_3 \\ &= \overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} C + A B C \\ &= \overline{A} \overline{C} (\overline{B} + B) + A C (\overline{B} + B) \\ &= \overline{A} \overline{C} + A C = A \odot C \end{aligned}$$

A	B	Y
0	0	\overline{C}
0	1	\overline{C}
1	0	C
1	1	C

Example - 4.13

The output of the given MUX equals to

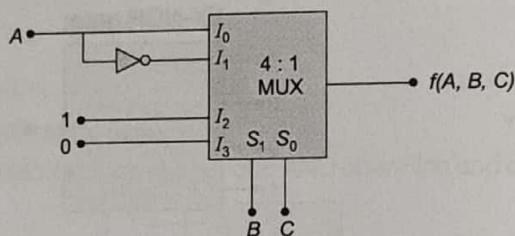

- (a) $f(A, B, C) = \Sigma m(1, 2, 4, 6)$
(c) $f(A, B, C) = \Sigma m(2, 4, 5, 6)$

- (b) $f(A, B, C) = \Sigma m(1, 2, 6)$
(d) $f(A, B, C) = \Sigma m(1, 5, 6)$

Solution: (a)

From the given 4 : 1 MUX we get,


$$\begin{aligned} f(A, B, C) &= A \overline{B} \overline{C} + \overline{A} \overline{B} C + B \overline{C} \cdot 1 \\ &= A \overline{B} \overline{C} + \overline{A} \overline{B} C + B \overline{C} (A + \overline{A}) \\ &= A \overline{B} \overline{C} + \overline{A} \overline{B} C + A B \overline{C} + \overline{A} B \overline{C} \\ &\approx 100, \quad 001, \quad 110, \quad 010 \end{aligned}$$

$$f(A, B, C) \approx \Sigma m(1, 2, 4, 6)$$

B	C	f
0	0	A
0	1	\overline{A}
1	0	1
1	1	0

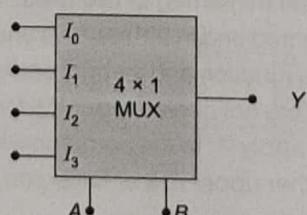Example - 4.14

Implement $f(A, B, C) = \Sigma m(0, 1, 4, 6, 7)$ by using the MUX given below



Solution:


For 3 variable function, the truth table is

	A	B	C	Y
0	0	0	0	1
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Let 'A' and 'B' are the select lines and 'C' be the input

	I_0	I_1	I_2	I_3
\bar{C}	0	2	4	6
C	1	3	5	7
	1	0	\bar{C}	1

Thus, for the implementation of given logical function, required is one 4×1 MUX and an Inverter.

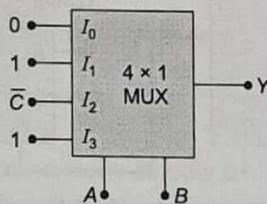**Application of MUX**

Multiplexer finds numerous applications in digital systems of all types. These applications include:

- | | |
|----------------------------|------------------------------------|
| (i) Data selection | (ii) Data routing |
| (iii) Operation sequencing | (iv) Parallel-to-serial conversion |
| (v) Waveform generation | (vi) Logic function generation |

NOTE

- By using $4 : 1$ MUX any two variable function and some of three variable functions can be implemented. However using $4 : 1$ MUX and a NOT gate all two variables as well as all three variable functions can be implemented.
- By using $8 : 1$ MUX any three variable function and some of four variable functions can be implement. However using $8 : 1$ MUX with a NOT gate all three variables as well as four variable functions can be implemented.

Example - 4.15

Consider a multiplexer with X and Y as data inputs and Z as control input.

$Z = 0$ selects input X and $Z = 1$ selects input Y. What are the connections required to realize the 2-variable Boolean function $f = T + R$, without using any additional hardware?

- | | |
|----------------------------|----------------------------|
| (a) R to X, 1 to Y, T to Z | (b) T to X, R to Y, T to Z |
| (c) T to X, R to Y, 0 to Z | (d) R to X, 0 to Y, T to Z |

Solution: (a)

Multiplexer function,


$$f = f = X\bar{Z} + YZ$$

Given Boolean function,
Let

$$\begin{aligned} f &= T + R \\ X = R, Y = 1 \text{ and } Z = T \\ f &= R\bar{T} + 1 \cdot T = R\bar{T} + T = R\bar{T} + T(1+R) = R\bar{T} + TR + T \\ &= R(\bar{T} + T) + T = R + T \end{aligned}$$

Example-4.16

In the below circuit, X is given by

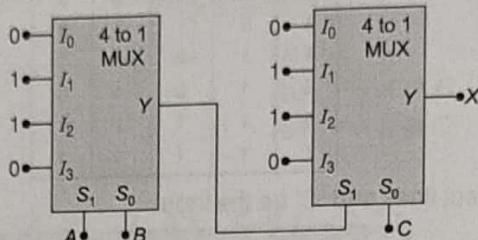

- (a) $X = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$
 (b) $X = \bar{A}\bar{B}C + A\bar{B}C + AB\bar{C} + \bar{A}\bar{B}\bar{C}$
 (c) $X = AB + BC + AC$
 (d) $X = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$

Solution: (a)

A B Y	Y C X
0 0 0	0 0 0
0 1 1	0 1 1
1 0 1	1 0 1
1 1 0	1 1 0

$\Rightarrow Y = \bar{A}B + A\bar{B} = A \oplus B$ and $\Rightarrow X = \bar{Y}C + Y\bar{C} = Y \oplus C$


$$\begin{aligned} X &= \bar{A} \oplus \bar{B}C + (A \oplus B)\bar{C} & \Rightarrow X = (\bar{A}\bar{B} + AB)C + (\bar{A}B + A\bar{B})\bar{C} \\ \Rightarrow X &= \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C} + A\bar{B}\bar{C} & \Rightarrow X = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC \end{aligned}$$

Example-4.17 A 2-to-1 digital multiplexer having a switching delay of 1 ms is connected as shown in Figure. The output of the multiplexer is tied to its own select input S . The input which gets selected when $S = 0$ is tied to 1 and the input that gets selected when $S = 1$ is tied to 0. The output V_0 will be

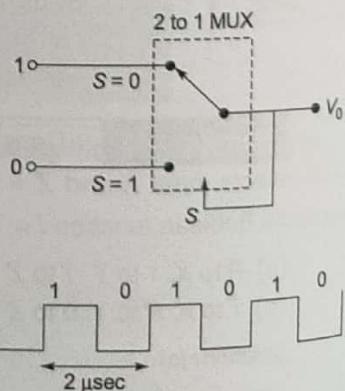- (a) 0
 (b) 1
 (c) pulse train of frequency 0.5 MHz
 (d) pulse train of frequency 1.0 MHz

Solution: (c)

When output is 1, then S will be also 1 and switch will go to 1 after 1 msec and output become zero, again S becomes 0 and switch will go to 0 after 1 msec and output goes to 1 this will continue and we will get the waveform at output as



so,

$$T = 2 \mu\text{sec}$$

then,

$$f = \frac{1}{T} = \frac{1}{2 \times 10^{-6}} = 0.5 \times 10^6 = 0.5 \text{ MHz}$$

Example - 4.18 The logic function $F = AC + ABD + ACD$ is to be realized using an 8 to 1 multiplexer shown in the Figure, using A , C and D as control inputs.


- (i) Indicate the inputs to be applied at the terminals 0 to 7.
- (ii) Can the function be realized using a 4 to 1 multiplexer?

Solution:

$$(i) F = AC + ABD + ACD$$

$$\begin{aligned} &= ACB + AC\bar{B} + ABDC + AB\bar{D} + ACD\bar{B} \\ &= ABC\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD + ABCD + AB\bar{C}\bar{D} \\ &= AC\bar{D}(\bar{B} + B) + ACD(B + \bar{B}) + A\bar{C}DB \\ &= \underbrace{\bar{D}CA}_{3^{\text{rd}} \text{ line}}(B + \bar{B}) + \underbrace{DCA}_{7^{\text{th}} \text{ line}}(B + \bar{B}) + \underbrace{D\bar{C}A}_{5^{\text{th}} \text{ line}}B \\ &= \bar{D}CA(1) + DCA(1) + D\bar{C}A \cdot (B) \end{aligned}$$

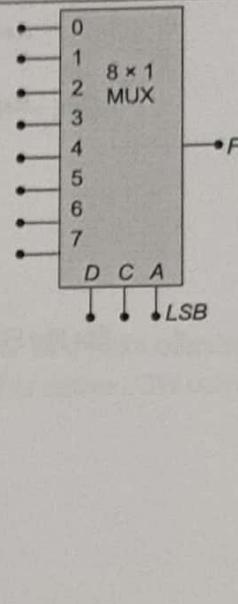- (ii) It can not be realized with a 4 to 1 multiplexer as 5th and 7th lines are being used.



4.3.4 Decoders

- A decoder has many inputs and many outputs.
- It is a combinational logic circuit that converts binary information from ' n ' bit input lines to a maximum ' 2^n ' unique output lines such that only one output line is activated for each one of possible combinations of input.
- Decoders are used to identify or convert a particular code for example:
 1. Binary to Octal (3-8 line decoders)
 2. Binary to Hexadecimal (4-16 line decoders)
 3. BCD to decimal (4-10 line decoders)
 4. BCD to 7-segment display
- If the n -bit decoded information has unused or don't care combinations, the decoder output will have less than 2^n outputs.
i.e. if, n = total number of input lines.

$$m = \text{total number of output lines.}$$

then,

$$m \leq 2^n$$

- Decoders are widely used in memory system of computers.

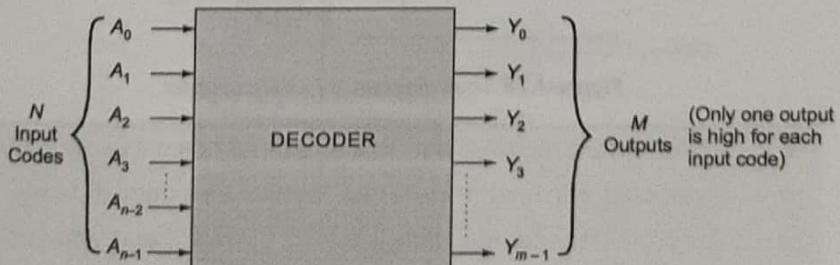
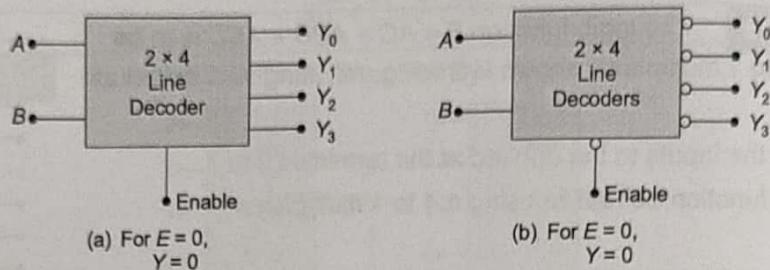


Figure-4.26 General block diagram of a decoder

The 2×4 Line Decoder

- 2×4 decoders are minimum possible decoders.
- Let A and B are the two inputs and Y_0, Y_1, Y_2 and Y_3 are the four outputs.


**Figure-4.27** Two to four line decoder with enable input

- For the Figure 4.27(b), we have,

E	A	B	Y_0	Y_1	Y_2	Y_3
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

Table-4.11 Truth table for 2×4 line decoder

- Some decoders are constructed with NAND gates. Since a NAND gate produces the AND operation with an inverted output, it becomes more economical to generate the decoder minterms in their complemented form. Furthermore, decoders include one or more enable inputs to control the circuit operation. Figure 4.28 shows a 2×4 line decoder with an enable input using NAND gates. The circuit operated with complemented outputs and complemented enable input.

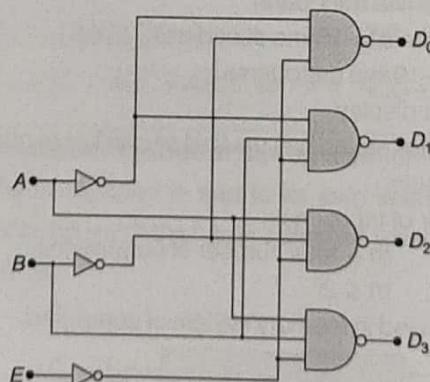
**Figure-4.28** Logic diagram of 2×4 line decoder**Remember**

- The internal circuitry of decoder and DEMUX are exactly same.
- A decoder with enable input can function as a demultiplexer.
- 2×4 line decoder may acts like a $1 : 4$ DEMUX and vice-versa.
- Decoder contains AND-gates or NAND-gates

- A half adder or a half subtractor circuit can be implemented by 2×4 decoder and OR gate. For example: Implementation of half adder using 2×4 line decoder As we know, for half adder

$$S = A \oplus B \quad \text{and} \quad C = AB$$


\therefore from 2×4 line decoder

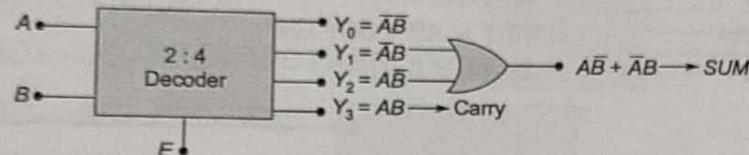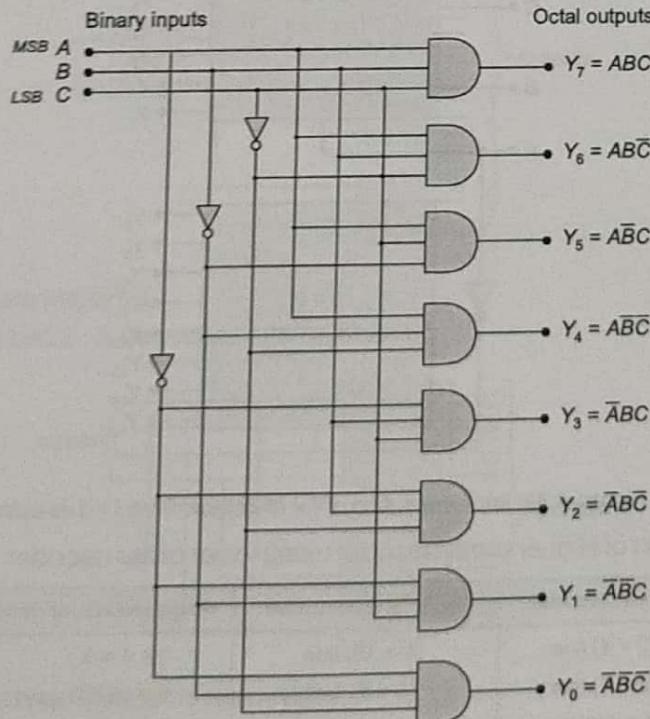Figure 4.29 Half Adder using 2×4 line decoder

The 3×8 Line Decoder

- Figure 4.30 shows the circuitry for a decoder with three inputs A , B and C and eight outputs Y_0 , Y_1 , ..., Y_7 . It uses all AND gates, and therefore the output are active HIGH. For active LOW outputs. NAND gates are used. The truth table is shown in Table 4.12.
- Truth Table:

A	B	C	Y_0	Y_1	Y_2	Y_3	Y_4	Y_5	Y_6	Y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Table 4.12 Truth table for 3×8 line decoderFigure 4.30 Logic diagram of 3×8 line decoder

- To implement a full adder or a full subtractor 3×8 decoder and two OR gates are required.
- For example:* Implementation of full adder circuit using 3×8 line decoder:

As we know, for full adder circuit

$$\text{SUM} = A \oplus B \oplus C$$

or

$$\Sigma m(1, 2, 4, 7)$$

and

$$\text{CARRY} = AB + BC + CA$$

or

$$\Sigma m(3, 5, 6, 7)$$

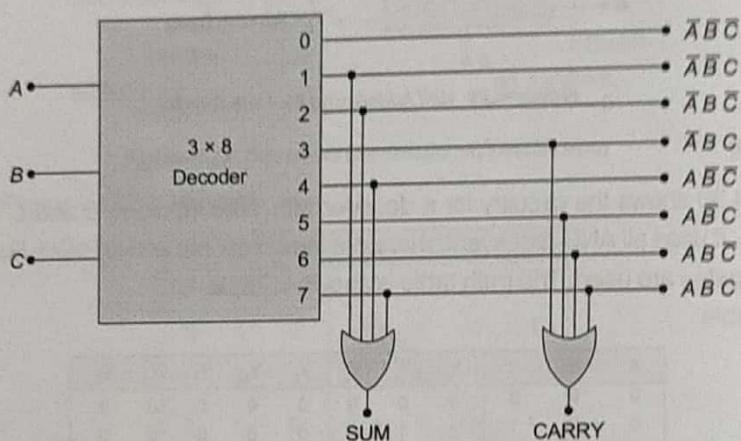


Figure-4.31 Full adder using 3×8 line decoder

- Implementation of 4×16 decoder using 3×8 decoder:

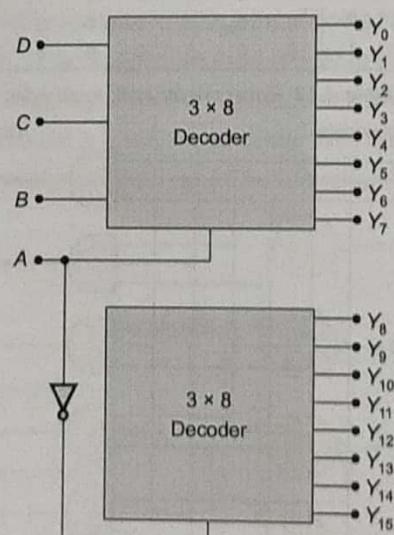


Figure-4.32 Implementation of 4×16 decoder from 3×8 decoder


- Implementation of Higher order decoder using lower order decoder

Given Decoder	To be Implemented	Required no. of decoders
(2 × 4) line	(4 × 16) line	$1 + 4 = 5$
(2 × 4) line	(3 × 8) line	$2 + 1$ NOT gate
(4 × 16) line	(8 × 256) line	$1 + 16 = 17$

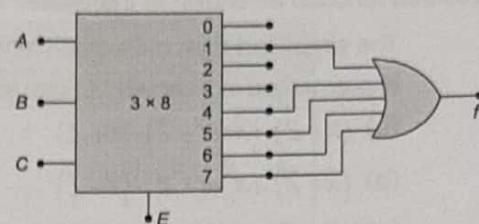Example-4.19 Implement $A + \bar{B}\bar{C}$ by using 3×8 line decoder.

Solution:

$$\begin{aligned} \text{Given, } f &= A + \bar{B}\bar{C} \\ &= A \cdot (B + \bar{B})(C + \bar{C}) + \bar{B}\bar{C}(A + \bar{A}) \\ &= ABC + A\bar{B}C + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C \\ &= ABC + A\bar{B}C + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}BC \end{aligned}$$



Example-4.20 Consider the following statements:

A 4 : 16 decoder can be constructed (with enable input) by:


1. using four 2:4 decoders (each with an enable input) only.
2. using five 2:4 decoders (each with an enable input) only.
3. using two 3:8 decoders (each with an enable input) only.
4. using two 3:8 decoders (each with an enable input) and an inverter.

Which of the statements given above is/are correct

- | | |
|-------------|-----------------------|
| (a) 2 and 3 | (b) 1 only |
| (c) 2 and 4 | (d) None of the above |


Solution:(c)

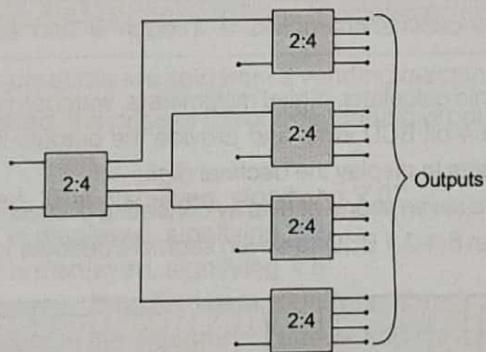4 : 16 decoder using only 2 : 4 decoders:



Five 2 \times 4 decoders are required

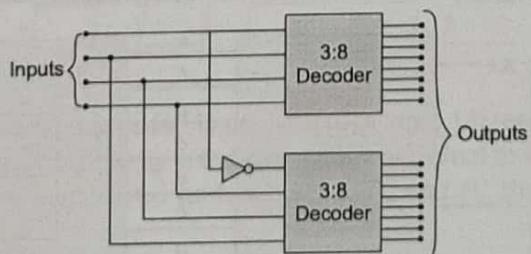4 : 16 decoder using two 3 : 8 decoders and an inverter:




Two 3 \times 8 decoder and one inverter is required.

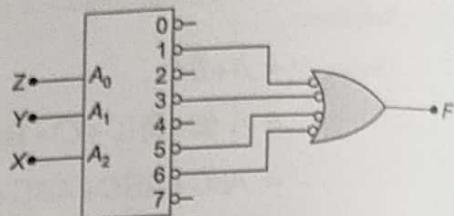Example - 4.21 A 3 to 8 line decoder, with active low outputs, is used to implement a 3 variable Boolean function as shown in the figure.

The simplified form of Boolean function $F(A, B, C)$ implemented in 'Product of Sum' form will be

- $(X + Z) \cdot (\bar{X} + \bar{Y} + \bar{Z}) \cdot (Y + Z)$
- $(\bar{X} + \bar{Z}) \cdot (X + Y + Z) \cdot (\bar{Y} + \bar{Z})$
- $(\bar{X} + \bar{Y} + Z) \cdot (\bar{X} + Y + Z) \cdot (X + \bar{Y} + Z) \cdot (X + Y + \bar{Z}) \cdot (X + Y + \bar{Z})$
- $(\bar{X} + \bar{Y} + Z) \cdot (\bar{X} + Y + \bar{Z}) \cdot (X + \bar{Y} + Z) \cdot (X + \bar{Y} + \bar{Z})$



Solution : (a)

Let us consider active high input

X\YZ	00	01	11	10
0	0	1	1	0
1	0	1	0	1

$$F = \Sigma(1, 3, 5, 6) = \Pi M(0, 2, 4, 7) = (Y + Z) \cdot (X + Z) \cdot (\bar{X} + \bar{Y} + \bar{Z})$$

BCD to Seven Segment Display Decoder

- One of the most popular and simplest methods for displaying numerical digits is a "7-segment display" to form the decimal characters '0' through '9' and sometimes the HEX-characters 'A' through 'F'.
- It is used in electronic calculators, digital multimeters, watches (wrist and railways).
- It is used to take a 4-bit BCD input and provide the outputs that will pass current through the appropriate segments to display the decimal digit.
- Figure 4.33, shows a seven segment display consisting of seven light emitting segments. However the logic circuit of an 8-4-2-1 BCD-to-seven segment decoder is shown in Figure 4.34.

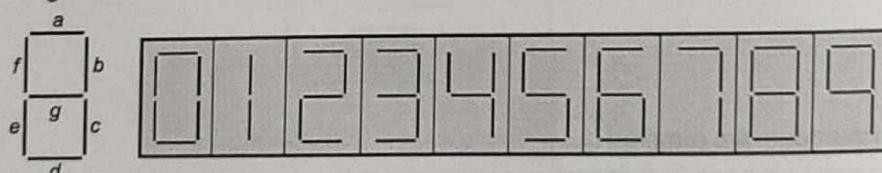


Figure-4.33 Letters and Numerals used to designate the segments

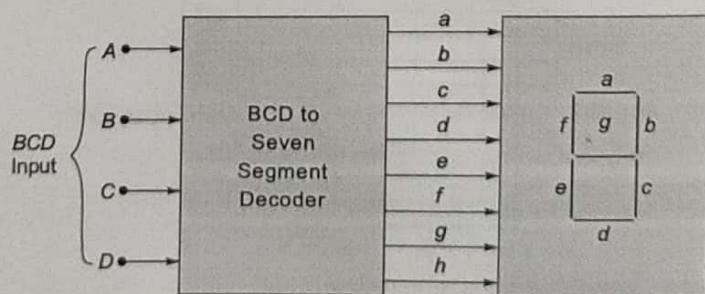


Figure-4.34 Logic Circuit of BCD 7-segment Display Decoder

- Truth Table:

Table-4.13 Truth table of BCD-to-7-segment decoder

Decimal digit displayed	Input				Output						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

- Minimization of Boolean function (after using K-map):

$$a = \bar{B}\bar{D} + BD + CD + A; \quad b = \bar{B} + \bar{C}\bar{D} + CD$$

$$c = B + \bar{C} + D = \overline{\bar{B}C\bar{D}}; \quad d = \bar{B}\bar{D} + C\bar{D} + \bar{B}C + B\bar{C}D$$

$$e = \bar{B}\bar{D} + C\bar{D}; \quad f = A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$


$$g = A + B\bar{C} + \bar{B}C + C\bar{D}$$

NOTE: The outputs of display has AND-OR logic, so it can be implemented by '24' NAND gates.

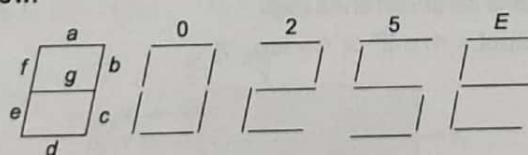Example-4.22 Two products are sold from a vending machine, which has two push buttons P_1 and P_2 . When a button is pressed, the price of the corresponding product is displayed in a 7-segment display.

If no buttons are pressed, '0' is displayed, signifying ₹ 0'
 If only P_1 is pressed, '2' is displayed, signifying ₹ 2'
 If only P_2 is pressed, '5' is displayed, signifying ₹ 5'
 If both P_1 and P_2 are pressed, 'E' is displayed, signifying 'Error'

The names of the segments in the 7-segment display, and the glow of the display for '0', '2', '5' and 'E' are shown below.



Consider:

- push button pressed/not pressed is equivalent to logic 1/0 respectively,
 - a segment glowing/not glowing in the display is equivalent to logic 1/0 respectively
- If segments a to g are considered as functions of P_1 and P_2 , then which of the following is correct?

(a) $g = \bar{P}_1 + P_2, d = c + e$

(b) $g = P_1 + P_2, d = c + e$

(c) $g = \bar{P}_1 + P_2, e = b + c$

(d) $g = P_1 + P_2, e = b + c$


Solution : (b)

We have two input variables here as P_1 and P_2 . Firstly we draw a truth table according to statement of problem.

Inputs		Outputs						
P_1	P_2	a	b	c	d	e	f	g
0	0	1	1	1	1	1	1	0
0	1	1	0	1	1	0	1	1
1	0	1	1	0	1	1	0	1
1	1	1	0	0	1	1	1	1

- display '0'
- display '5'
- display '2'
- display 'E'

K-map for 'g':

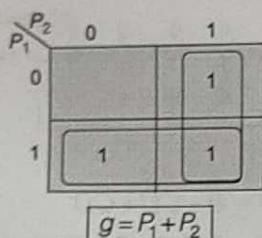

also, we have

$$a = 1, b = \bar{P}_2, c = \bar{P}_1, d = 1, e = P_1 + \bar{P}_2, f = \bar{P}_1 + P_2$$

since,

but,

$$e \neq b + c$$

$$d = c + e$$

$$= P_1 + \bar{P}_2 + \bar{P}_1 = 1 + \bar{P}_2 = 1$$

so,

$$g = P_1 + P_2 \text{ and } d = c + e$$

4.3.5 Demultiplexer

- A demultiplexer is a combinational circuit that receives information on a single line and transmits this on one of " 2^n " possible output lines. However the selection of a specific output line is controlled by the bit values of ' n ' selection lines.
- A 'decoder' with an enable input can function as a 'demultiplexer'.
- Demultiplexer is also known as:
 - (i) Data distributor
 - (ii) Serial to parallel converter
 - (iii) One to many circuit
- It is used to perform the reverse operation of MUX.

NOTE: DEMUX can not be used as an universal gate

- If ' n ' be the number of selection lines then,
Total number of output = $m = 2^n$ or $n = \log_2 m$

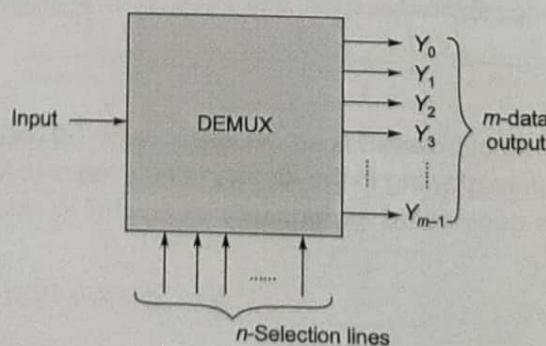
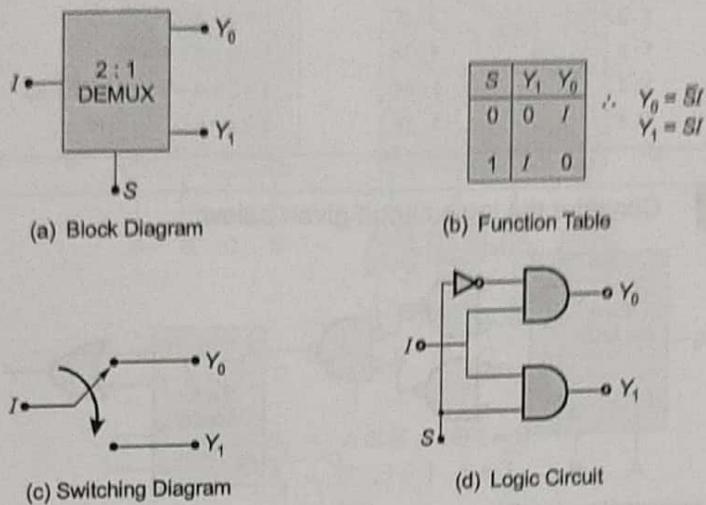



Figure-4.35 Functional diagram of a digital DEMUX

The 1 to 2 Line Demultiplexer


Figure 4.36 shows the logic circuitry and function table for 1 : 2 line DEMUX. It has an input 'I' for which output Y_0 and Y_1 are obtained. The selection line S is used to select the specific output.

**Figure-4.36** 1:2 Line Demultiplexer**The 1 to 4 Line Demultiplexer**

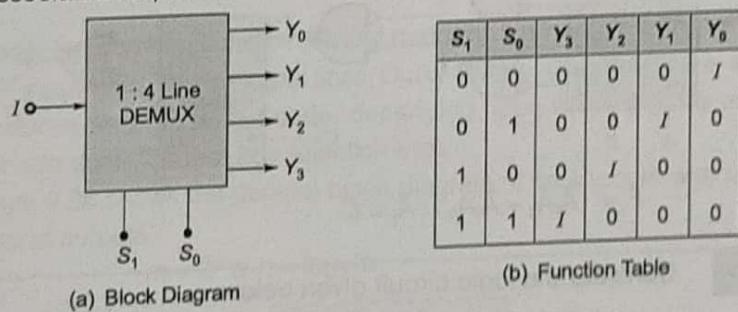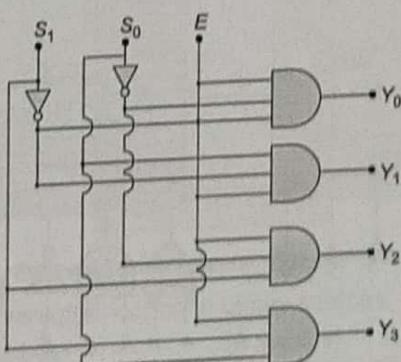A 1 : 4 line DEMUX is shown in Figure 4.37. The input data line goes to all of the AND gates. The two select lines S_0 and S_1 enable only one gate at a time and the data appearing on the input line will pass through the selected gate to the associated output line. The function table is shown in Figure 4.37(b).




where, $Y_0 = \bar{S}_1\bar{S}_0I$; $Y_1 = \bar{S}_1S_0I$; $Y_2 = S_1\bar{S}_0I$ and $Y_3 = S_1S_0I$

**Figure-4.37** 1:4 Line Demultiplexer

- Implementation of higher order DEMUX using lower order DEMUX

Given DEMUX	To be implemented	Required
1:2	1:4	$1+2=3$
1:2	1:8	$1+2+4=7$
1:2	1:16	$1+2+4+8=15$
1:2	1:64	$1+2+4+8+16+32=63$
1:4	1:16	$1+4=5$

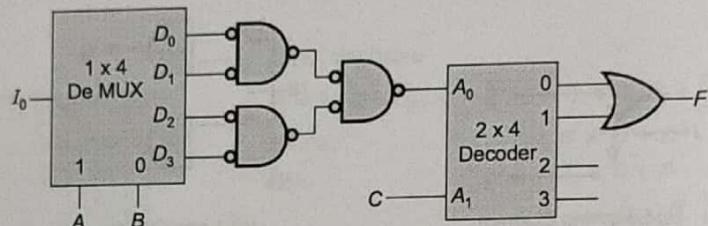
Example-4.23 Consider the logic circuit given below:



The minimized expression for F is


- (a) \bar{C}
 (b) I_0
 (c) C
 (d) \bar{I}_0

Solution: (a)

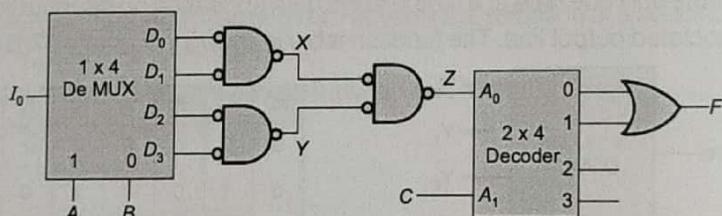


$$F = \bar{A}_1 \bar{A}_0 + \bar{A}_1 A_0 = \bar{A}_1 = \bar{C}$$

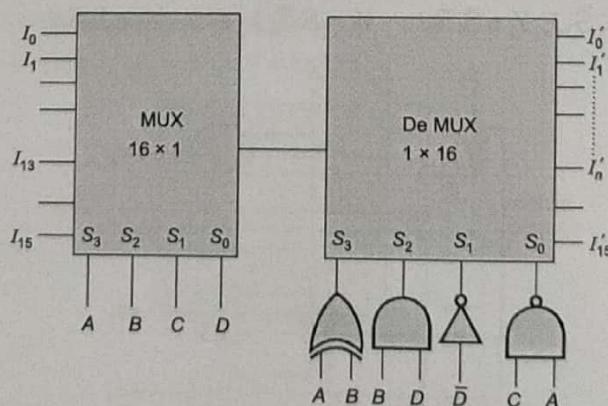Example-4.24 Consider the logic circuit given below:



Input at line I₁₃ in 16x1 MUX corresponds to output at line I'_n of 1x16 De MUX. The value of 'n' is

Solution:

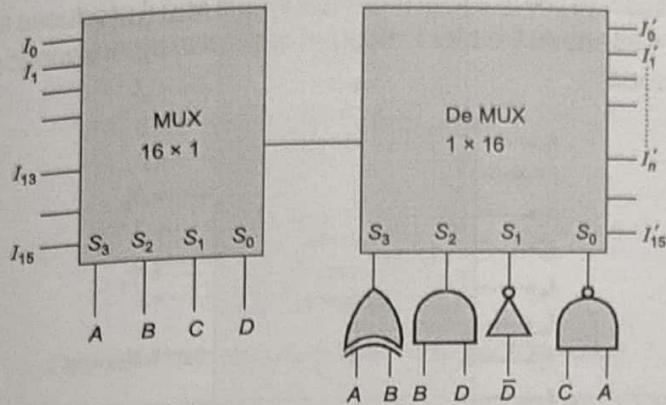

$$I_{13} \rightarrow A \ B \ C \ D \\ 1 \ 1 \ 0 \ 1$$

$$S_3 = A \oplus B = 1 \oplus 1 = 0$$

$$S_2 = B \cdot D = 1 \cdot 1 = 1$$

$$S_1 = \overline{\overline{D}} = D = 1$$

$$S_0 = \overline{CA} = \overline{0 \cdot 1} = 1$$

$$I_n \rightarrow S_3 \ S_2 \ S_1 \ S_0 \\ 0 \ 1 \ 1 \ 1$$

$$(A' \ B' \ C' \ D') = 7 \Rightarrow n = 7$$

4.3.6 Encoders

- An encoder is a combinational circuit that performs the inverse operation of a decoder.
- It has ' 2^n ' input lines, and 'n' output lines. Out of 2^n input lines only one is activated at a given time and produces an n bit output code, depending upon which input is activated. Like decoder, encoder also does not have any selection lines.
- The Figure 4.38 shows the general block diagram of an encoder with m number of inputs and n -number of outputs.

Where,

$$m = 2^n \text{ or } n = \log_2 m$$

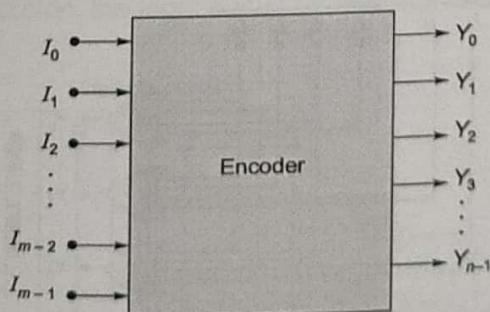


Figure-4.38 Block diagram of an encoder

Encoder is used to convert other codes to binary such as,

- Octal to binary encoder (8×3 line)
- Decimal to BCD encoder (10×4 line)
- Hexadecimal to binary encoder (16×4 line)

Octal to Binary Encoder

An octal to binary encoder (8 line to 3 line) has eight inputs and it produces three outputs corresponding to the activated input. Figure 4.39 shows the block diagram of octal to binary encoder and Table 4.14 shows the truth table for octal binary encoder.

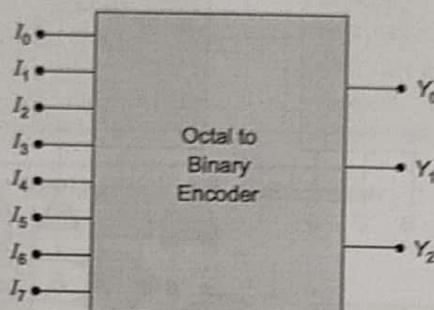


Figure-4.39 Block diagram of octal to binary encoder

I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Table-4.14 Truth table for 8 line to 3 line encoder

from the truth table, it is clear that Y_2 is '1' if any of the digits I_4 or I_5 or I_6 or I_7 is a '1'. Therefore,

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

Similarly,

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

and

$$Y_0 = I_1 + I_3 + I_5 + I_7$$

As we see that I_0 is not present in any of the expression. So, I_0 is a don't care.

- From the logical expression a logic circuit for 8 line to 3 line encoder can be constructed as shown in Figure 4.40.

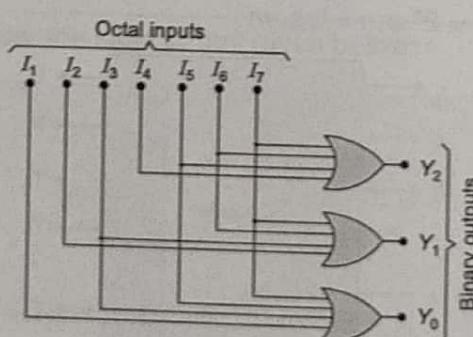


Figure-4.40 Logic diagram of 8 line to 3 line encoder

NOTE: The encoder contains OR gate.

Decimal to BCD Encoder

This encoder has ten inputs (0 to 9), and four outputs corresponding to BCD codes. The Figure 4.41(a) shows a basic 10 line to 4 line encoder. However the truth table is shown in Table 4.15.

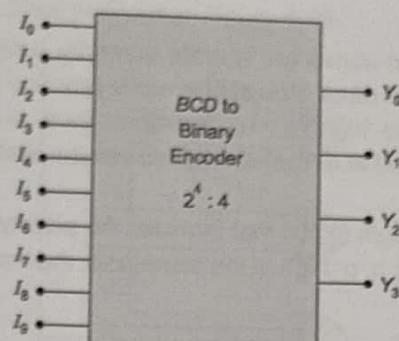


Figure-4.41(a) Block diagram of Decimal to BCD encoder

I_9	I_8	I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	0
0	0	0	0	0	1	0	0	0	0	0	0	1	0
0	0	0	0	1	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	1	0	0	0	0	0	0	0	0	0	1	1
0	1	0	0	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

Table-4.15 Truth Table decimal to BCD encoder

from the truth table we can determine the expression for outputs as.

$$\begin{aligned}
 Y_3 &= I_8 + I_9; & Y_2 &= I_4 + I_5 + I_6 + I_7 \\
 Y_1 &= I_2 + I_3 + I_6 + I_7; & Y_0 &= I_1 + I_3 + I_5 + I_7 + I_9
 \end{aligned}$$

It is clear that, there is no explicit input for a decimal '0'. The BCD outputs are 0000 when the BCD inputs 1–9 are all '0'.

Based on the logical expression, the logic circuit for Decimal to BCD encoder can be constructed as shown in Figure 4.41(b).

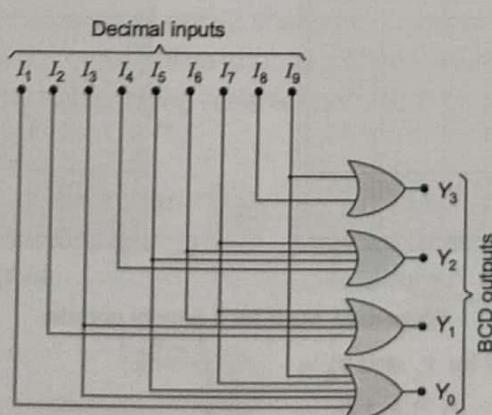


Figure-4.41(b) Logic diagram for decimal to BCD encoder

4.3.7 Priority Encoder

- The encoders discussed above will operate correctly, provided that one and only one decimal input is 'high' at any given time. However in some practical systems, two or more decimal inputs may inadvertently become 'high' at the same time. Thus, to eliminate this drawback (when more than one input is activated at a time) a modified version of simple encoder is used called "priority encoder".
- A priority encoder is a logic circuit that includes the priority functions to ensure that when two or more inputs are equal to '1' or high at the same time, the input having the highest priority will take precedence.

Four Input Priority Encoder


The truth table of a 4-bit priority encoder is given in Table 4.16. The inputs are designated as I_0, I_1, I_2 , and I_3 and in addition to the two outputs Y_1 and Y_0 the circuit has a third output designated as X ; this is activated when one or more inputs are 'high'. If all the inputs are '0' or 'low' there are no valid input and $X=0$. The other two outputs are not inspected when $X=0$ and are specified as don't care condition.

Table-4.16 Truth table for four input priority encoder


I_0	I_1	I_2	I_3	Y_1	Y_0	X
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

According to the truth table shown in Table 4.16 the higher the subscript numbers, the higher the priority of the input. Input I_3 has the highest priority. So regardless of the values of other inputs, when the input is high the output for $Y_1 Y_0 = 11$. Now I_2 has the next priority thus, when $I_3 = 0$ and $I_2 = 1$ regardless of other lower priority inputs shown as don't care, the outputs $Y_1 Y_0 = 10$ similarly for I_1 it is required that I_2 and I_3 should be 'low' and I_0 is don't care and outputs $Y_1 Y_0 = 01$ and lastly for I_0 (lowest priority) all the other inputs are 'low' and outputs $Y_1 Y_0 = 00$.

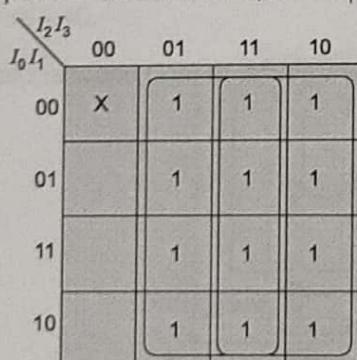With the help of truth table the maps for Y_1 and Y_0 are shown in Figure.



$$(a) Y_1 = I_2 + I_3$$

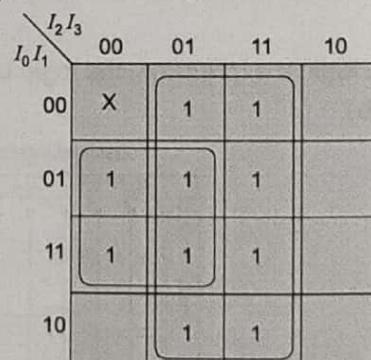

$$(b) Y_0 = I_0 + I_1 \bar{I}_2$$

Figure-4.42 Maps for a priority encoder

The simplified expressions for Y_1 and Y_0 is

$$Y_1 = I_2 + I_3$$

$$Y_0 = I_0 + I_1 \bar{I}_2 \quad \text{and} \quad X = I_0 + I_1 + I_2 + I_3$$

The implementation of logic circuit is shown in Figure 4.43.

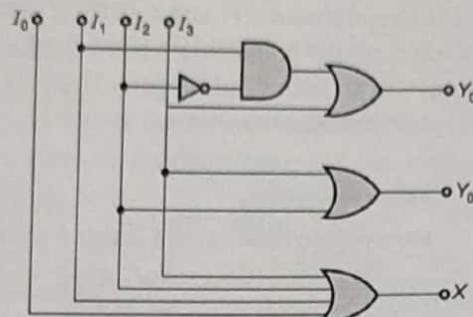


Figure-4.43 Logic Diagram of Four Input Priority Encoder

4.4 Hazards

- Hazard is a phenomenon that may cause the digital circuit to malfunction. These are unwanted switching transients that may appear at the output of a circuit because different paths exhibit different propagation delays. Such a transient is also called a 'glitch' or a false 'spike', which is caused by hazardous behaviour of the logic circuit.
- Hazards occurs in combinational as well as sequential circuits. In combinational circuits they may cause a temporary false output value, whereas in sequential circuits they may result in a transition to a wrong stable state. It is therefore necessary to check for possible hazards, determine whether they can cause improper operation so that step can be taken to eliminate their effect.
- Hazards are classified as:
 - (i) Static hazard
 - (ii) Dynamic hazard
 - (iii) Essential hazard

Static Hazard

Static hazard occur in combinational circuits and can be eliminated by using redundant gates. Static hazard is further classified as:

1. Static -1 hazard
2. Static -0 hazard

The circuit in Figure 4.46 (a) shows the occurrence of hazard. Assume that all the three inputs initially equal to '1'. Now consider a change in B from '1' to '0'. Then the output of gate-1 changes to '0' and that of gate-2 changes to '1', leaving the output $Y = 1$ regardless of the changing variable, the output may momentarily go to '0' if the propagation delay of the inverter is taken into account. The delay in the inverter may cause the output of gate-1 to change to '0' before the output of gate-2 change to 1. In that case, both input of the gate-3 are momentarily equals to '0', causing the output Y to go to '0', for a short interval. Such a condition where the output is expected to be at '1', regardless of the changing variable, the false '0' level for a short interval will cause static-1 hazard.

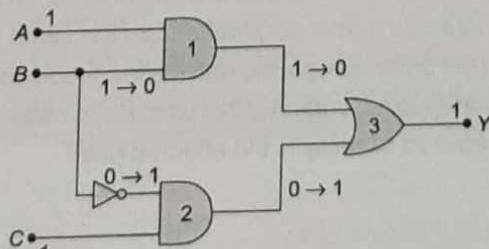


Figure-4.46(a) AND-OR circuit containing static hazard

If the output is expected to be '0' regardless of the changing variable, the false '1' level for the short interval is called a static '0' hazard. The circuit shown in Figure 4.46 (b) is a NAND implementation. Here gate-1 and 2 are NAND gates and their outputs are the complement of the outputs of corresponding AND gates in Figure 4.46 (a). When B changes from '1' to '0', both inputs of gate-3 may be equal to '1', causing the output to produce a momentary change to '0', when it should have stayed to '1'.

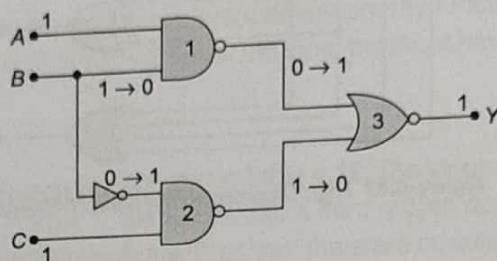


Figure-4.46 (b) NAND circuit containing static Hazard

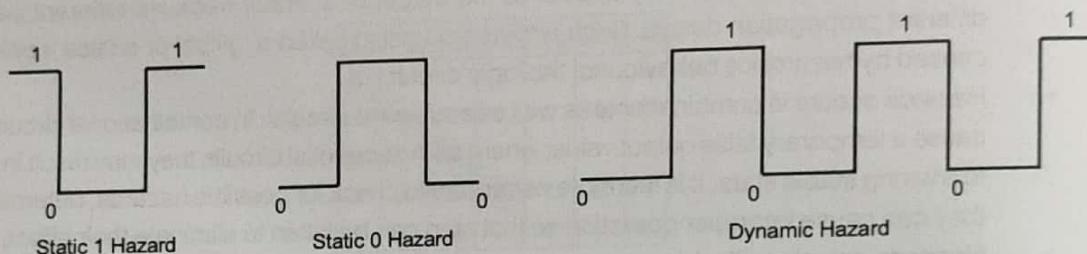


Figure-4.46 (c) Types of Hazards

Dynamic Hazard

When the output changes several times then it should change from $1 \rightarrow 0$ or $0 \rightarrow 1$ only once, it is called dynamic hazard.

Dynamic hazard occur when the output changes for two adjacent input combinations while changing, the output should change only once; but it may change three or more times in short intervals because of different delays in several paths. Dynamic hazards occur only in multilevel circuit.

Figure 4.46 (c) illustrates three types of hazards. When a circuit is implemented in SOP form with AND-OR gates or with NAND gates, the removal of static-1 hazard guarantees that no static-0 hazard OR dynamic hazards will occur.

Essential Hazard

Essential hazard is the another type of hazard occur in asynchronous sequential circuit. It is called by unequal delays along two or more paths, that originated from the same input. An excessive delay through an inverter circuit in comparison to the delay associated with the feedback path may cause such a hazard. Essential hazard cannot be corrected by adding redundant gates as in static hazards. However the problem that they can be corrected by adjusting the amount of delay in the effected path.



Summary

- BCD code is used in calculators, counters, digital voltmeters, digital clocks etc.
- Minimum number of NAND/NOR gate required for the implementation of H.A/H.S is '5'.
- Minimum number of 2×1 MUX required for the implementation of a H.A/H.S is '3'.
- Minimum number of decoders required for the implementation of H.A/H.S is a (2 : 4 line) plus an OR gate.
- Half Adder + Inverter = Half Subtractor
- Full Adder = 2 Half Adder + OR gate
- Full subtractor = 2 Half subtractor + OR gate
- Minimum number of NAND/NOR gates required for the implementation of F.A./F.S. is '9'.
- Number of AND gates required for an N bit look ahead carry circuit is $\frac{N(N+1)}{2}$, and number of OR gates required for look ahead carry circuit is N .
- A look ahead carry adder is the fastest adder.
- To implement $2^n : 1$ MUX by using $2 : 1$ MUX, the total number $2 : 1$ MUX required is $(2^n - 1)$.
- A 'decoder' with an enable input can function as a DEMUX.
- DEMUX contains AND gates.
- 2×4 decoder may act like a $1 : 4$ DEMUX and vice-versa.
- Decoder and DEMUX circuits are almost same.
- Decoder contains AND gates or NAND gates.
- In priority encoder more than one input line can be high but only for the highest priority input line, binary output is available at output.
- Encoder contains OR gates
- Relation between the parity (check) bits and information bits.

$$2^C - 1 \geq C + I$$

where, C = Number of check bits

I = Information bits

$C + I$ = Word length

- Hamming codes are used for error detection and correction for a single bit only.
- If the minimum Hamming code distance is m , then the number of errors to be corrected is less than $m/2$.
- The type of display used in calculators is a 7 segment LED/LCD display.
- Static-1 hazard with contact networks is called a tie set hazard.
- Static-0 hazard with contact networks is called a cut set hazard.

Student's
Assignments

1


Q.1 Implement the function

$$f(A, B, C, D) = \Sigma(0, 1, 5, 7, 10, 14, 15)$$


using an appropriate multiplexer.

Q.2 Write the truth table for the following in Boolean expression, and realize it using only an 8 : 1 multiplexer, $f = \overline{AB} + BD + A\overline{BC}$ Student's
Assignments

2

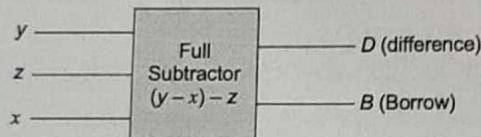
Q.1 Find the Boolean expression 'B' for the digital circuit below

- (a) $xy + yz + zx$ (b) $\bar{x}y + yz + z\bar{x}$
 (c) $x\bar{y} + \bar{y}z + zx$ (d) $xy + y\bar{z} + \bar{z}x$

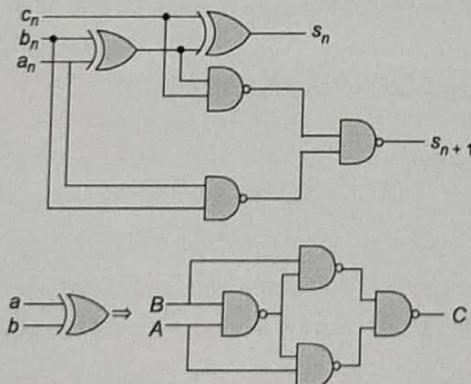
Q.2 A full adder circuit is shown below:

The propagation time for each NAND GATE is 15 nsec then the time required for each addition is given by

- (a) 45 nsec (b) 90 nsec
 (c) 125 nsec (d) 180 nsec

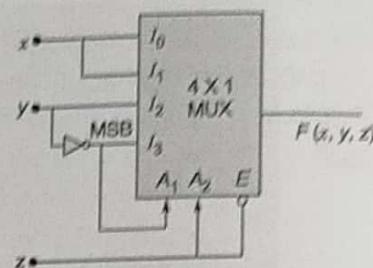Q.3 For the 4×1 MUX shown below the Boolean expression $F(x, y, z)$ is


- (a) $xy\bar{z}$ (b) $(xy\bar{z} + xyz + z\bar{y})$
 (c) $xy\bar{z} + xyz$ (d) None of these

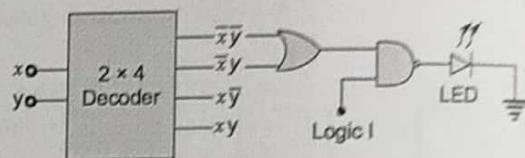Q.4 A LED is connected to a combinational circuit as shown below:

A LED emits light when its positive terminal is connected to a higher potential (equivalent to logic 1) and its negative terminal is connected to a lower potential (equivalent to logic 0).


For what values of input x and y , the LED will emit light?

- (a) $x = 1$ and $y = 0$
 (b) $x = 0$ and $y = 1$
 (c) $x = 1$ and independent of the value of y
 (d) $y = 1$ and independent of the value of x

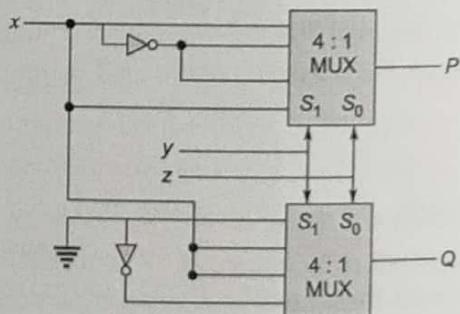Q.5 The multiplexer circuit functions as

- (a) Full adder
 (b) Full subtractor
 (c) Two output comparator
 (d) Non arithmetic combinational logic


Q.6 Consider the 8×3 ROM shown below:

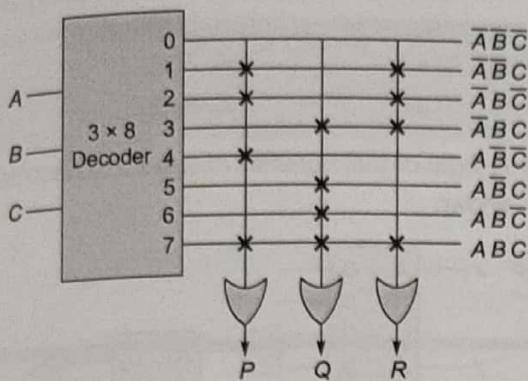

Which of the following statement is correct?

- The ROM can be used as full subtractor with R as the Difference and P as the Borrow.
- The ROM can be used as a full subtractor with P as the Difference and Q as the Borrow.
- The ROM can be used as a full adder with R as the Sum and Q as the Carry.
- The ROM can be used as full adder with P as the Sum and Q as the Carry.


Q.7 Consider the following circuit:

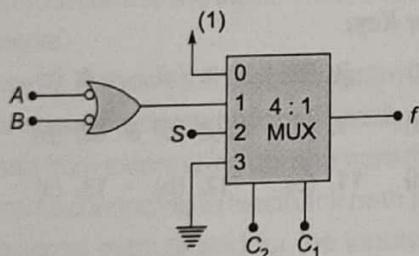

Which one of the following gives the function implemented by the MUX-based digital circuit?

- $f = C_2 \cdot \bar{C}_1 \cdot S + \bar{C}_2 \cdot C_1 \cdot (\bar{A} + \bar{B})$
- $f = \bar{C}_2 \cdot \bar{C}_1 + C_2 \cdot C_1 + C_2 \cdot \bar{C}_1 \cdot S + \bar{C}_2 \cdot C_1 \cdot \bar{A}\bar{B}$
- $f = \bar{A}\bar{B} + S$
- $f = \bar{C}_2 \cdot \bar{C}_1 + C_2 \cdot \bar{C}_1 \cdot S + \bar{C}_2 \cdot C_1 \cdot \bar{A}\bar{B}$

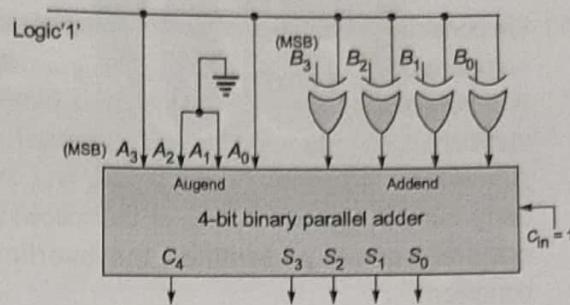
Q.8 Consider the digital circuit shown below. A single digit decimal number (B) is converted into its 4 bit binary equivalent ($B_3 B_2 B_1 B_0$) and then applied to the addend bits of the adder as shown below:



(i). The output $S_3 S_2 S_1 S_0$ is the

- 8's complement of B
- 9's complement of B
- 10's complement of B
- 11's complement of B

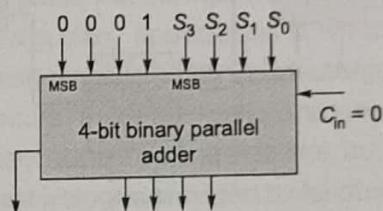(ii). If $C_4 = 1$ and the outputs $S_3 S_2 S_1 S_0$ are given to the addend bits of the 4-bit binary parallel adder as shown below:




Then output of the circuit is

- 9's complement of B
- 10's complement of B
- 11's complement of B
- 12's complement of B

Q.9 The number of select lines required in a single input and '256' output DEMUX is

- 8
- 16
- 32
- 64

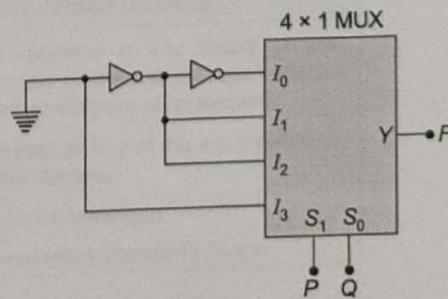Q.10 The logic function implemented by the circuit below is (ground implies a logic "0")




- $F = \text{AND}(P, Q)$
- $F = \text{OR}(P, Q)$
- $F = \text{XNOR}(P, Q)$
- $F = \text{XOR}(P, Q)$

Q.11 We consider the addition of two 2's complement numbers $b_{n-1} b_{n-2} \dots b_0$ and $a_{n-1} a_{n-2} \dots a_0$. A binary adder for adding unsigned binary numbers is used to add the two numbers. The sum is denoted by $c_{n-1} c_{n-2} \dots c_0$ and the carry out by c_{out} , which one of the following options correctly identifies the overflow condition?

- (a) $c_{\text{out}} (\overline{a_{n-1}} \oplus \overline{b_{n-1}})$
- (b) $\overline{a_{n-1}} b_{n-1} \overline{c_{n-1}} + \overline{a_{n-1}} \overline{b_{n-1}} c_{n-1}$
- (c) $c_{\text{out}} \oplus c_{n-1}$
- (d) $a_{n-1} \oplus b_{n-1} \oplus c_{n-1}$

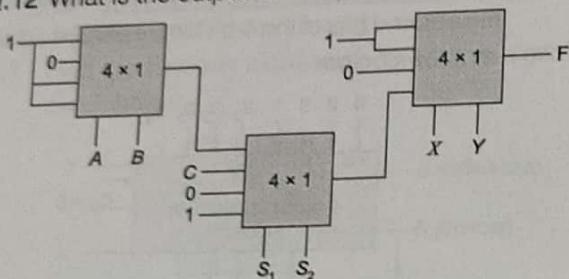
Q.12 What is the output of multiplexer shown below:



- (a) $\overline{X}\overline{Y} + \overline{X}Y + XY S_1 S_2 A\bar{B} + XY S_1 S_2 A\bar{B} + XY S_1 \overline{S_2} AB$
- (b) $\overline{X}\overline{Y} + XY\overline{S_1} \overline{S_2} A\bar{B} + XY\overline{S_1} \overline{S_2} AB + XY + \overline{S_1} \overline{S_2} AB + \overline{S_1} S_2 C + XY S_1 S_2 + \overline{X}Y$
- (c) $\overline{X}\overline{Y} + XY\overline{S_1} S_2 C + XY\overline{S_1} \overline{S_2} A\bar{B} + XY\overline{S_1}$
- (d) $S_1 \overline{S_2} + A\bar{B}\bar{C} + \overline{X}\overline{Y} + XY\overline{S_1} S_2 C$

Q.13 If carry propagation delay is 5Δ in full adder, then multiplication of 8 bit numbers using array co-multiplier takes (Assume AND gate delay = 2Δ)
 (a) 72Δ (b) 74Δ
 (c) 70Δ (d) 82Δ

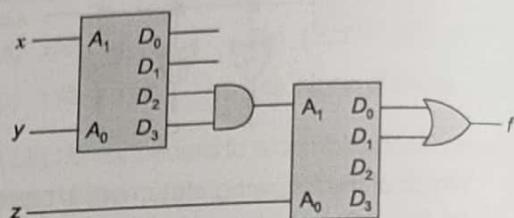Q.14 A logic circuit consists of two 2×4 decoder as shown



The output of the decoder are as follows

$D_0 = 1$ when $A_0 = 0, A_1 = 0$

$D_1 = 1$ when $A_0 = 1, A_1 = 0$

$D_2 = 1$ when $A_0 = 0, A_1 = 1$

$D_3 = 1$ when $A_0 = 1, A_1 = 1$

The value of $f(x, y, z)$ is

- (a) 0 (b) Z
- (c) \overline{Z} (d) 1

Answer Key:

- | | | | | |
|---------|---------|-----------------------|---------|---------|
| 1. (c) | 2. (b) | 3. (a) | 4. (c) | 5. (a) |
| 6. (d) | 7. (d) | 8. (i) (b) & (ii) (b) | | 9. (a) |
| 10. (d) | 11. (b) | 12. (b) | 13. (a) | 14. (d) |

